

Performance-based assessments for network analysis competencies

This worksheet and all related files are licensed under the Creative Commons Attribution License, version 1.0. To view a copy of this license, visit <http://creativecommons.org/licenses/by/1.0/>, or send a letter to Creative Commons, 559 Nathan Abbott Way, Stanford, California 94305, USA. The terms and conditions of this license allow for free copying, distribution, and/or modification of all licensed works by the general public.

The purpose of these assessments is for instructors to accurately measure the learning of their electronics students, in a way that melds theoretical knowledge with hands-on application. In each assessment, students are asked to predict the behavior of a circuit from a schematic diagram and component values, then they build that circuit and measure its real behavior. If the behavior matches the predictions, the student then simulates the circuit on computer and presents the three sets of values to the instructor. If not, then the student then must correct the error(s) and once again compare measurements to predictions. Grades are based on the number of attempts required before all predictions match their respective measurements.

You will notice that no component values are given in this worksheet. The *instructor* chooses component values suitable for the students' parts collections, and ideally chooses different values for each student so that no two students are analyzing and building the exact same circuit. These component values may be hand-written on the assessment sheet, printed on a separate page, or incorporated into the document by editing the graphic image.

This is the procedure I envision for managing such assessments:

1. The instructor hands out individualized assessment sheets to each student.
2. Each student predicts their circuit's behavior at their desks using pencil, paper, and calculator (if appropriate).
3. Each student builds their circuit at their desk, under such conditions that it is impossible for them to verify their predictions using test equipment. Usually this will mean the use of a multimeter only (for measuring component values), but in some cases even the use of a multimeter would not be appropriate.
4. When ready, each student brings their predictions and completed circuit up to the instructor's desk, where any necessary test equipment is already set up to operate and test the circuit. There, the student sets up their circuit and takes measurements to compare with predictions.
5. If any measurement fails to match its corresponding prediction, the student goes back to their own desk with their circuit and their predictions in hand. There, the student tries to figure out where the error is and how to correct it.
6. Students repeat these steps as many times as necessary to achieve correlation between all predictions and measurements. The instructor's task is to count the number of attempts necessary to achieve this, which will become the basis for a percentage grade.
7. (OPTIONAL) As a final verification, each student simulates the same circuit on computer, using circuit simulation software (Spice, Multisim, etc.) and presenting the results to the instructor as a final pass/fail check.



These assessments more closely mimic real-world work conditions than traditional written exams:

- Students cannot pass such assessments only knowing circuit theory or only having hands-on construction and testing skills – they must be proficient at both.
- Students do not receive the “authoritative answers” from the instructor. Rather, they learn to validate their answers through real circuit measurements.
- Just as on the job, the work isn't complete until *all errors* are corrected.
- Students must recognize and correct their own errors, rather than having someone else do it for them.
- Students must be fully prepared on exam days, bringing not only their calculator and notes, but also their tools, breadboard, and circuit components.

Instructors may elect to reveal the assessments before test day, and even use them as preparatory labwork and/or discussion questions. Remember that there is absolutely nothing wrong with “teaching to

the test” *so long as the test is valid*. Normally, it is bad to reveal test material in detail prior to test day, lest students merely memorize responses in advance. With performance-based assessments, however, there is no way to pass without truly understanding the subject(s).

Question 1

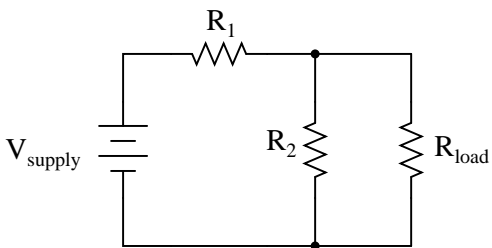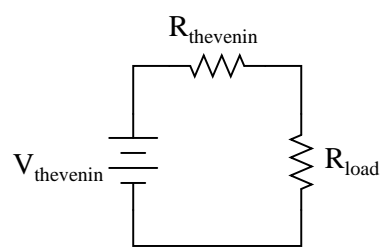Competency: Thevenin's theorem		Version:																					
Schematic																							
<i>Original circuit</i> 		<i>Thevenin equivalent circuit</i> 																					
Given conditions																							
$V_{\text{supply}} =$	$R_1 =$	$R_2 =$	$R_{\text{load}} =$																				
Parameters																							
<table style="width: 100%; border-collapse: collapse;"> <tr> <td colspan="4" style="text-align: center; padding-bottom: 10px;">Predicted</td> </tr> <tr> <td style="text-align: right; padding-right: 10px;">V_{thevenin}</td> <td colspan="3" style="border: 1px solid black; height: 25px;"></td> </tr> <tr> <td style="text-align: right; padding-right: 10px;">R_{thevenin}</td> <td colspan="3" style="border: 1px solid black; height: 25px;"></td> </tr> <tr> <td colspan="2" style="text-align: center; padding-top: 20px;">Measured (in original circuit)</td> <td colspan="2" style="text-align: center; padding-top: 20px;">Measured (in Thevenin equivalent circuit)</td> </tr> <tr> <td style="text-align: right; padding-right: 10px;">V_{load}</td> <td style="border: 1px solid black; width: 100px; height: 25px;"></td> <td style="border: 1px solid black; width: 100px; height: 25px;"></td> <td></td> </tr> </table>				Predicted				V_{thevenin}				R_{thevenin}				Measured (in original circuit)		Measured (in Thevenin equivalent circuit)		V_{load}			
Predicted																							
V_{thevenin}																							
R_{thevenin}																							
Measured (in original circuit)		Measured (in Thevenin equivalent circuit)																					
V_{load}																							

file 03225

Answer 1

Use circuit simulation software to verify your predicted and measured parameter values.



Notes 1

Use a variable-voltage, regulated power supply for $V_{thevenin}$, and a fixed-voltage supply for V_{source} . Specify standard resistor values, all between $1\text{ k}\Omega$ and $100\text{ k}\Omega$ (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k, 47k, 68k, etc.) for resistors in the original circuit. A decade box or potentiometer will suffice for $R_{thevenin}$.

In case it is not already crystal-clear, I want students to build *two different circuits* for this exercise: the "original" circuit and also a "Thevenin equivalent" circuit, then plug the exact same load resistor into both circuits (one at a time) to see that the voltage across it is the same in both cases. Many students seem to struggle with the basic concept of equivalent circuits, and I have found this exercise (once successfully completed) to be excellent for "making it real" to these students.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Question 2

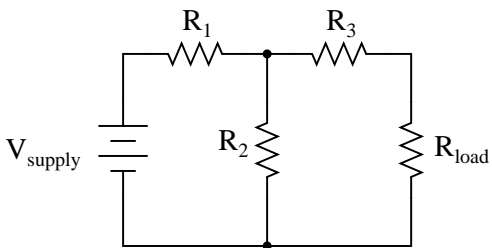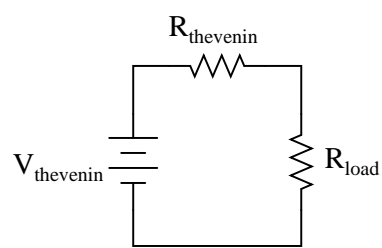Competency: Thevenin's theorem		Version:
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="display: flex; justify-content: space-around; align-items: flex-start; padding: 10px;"> <div style="text-align: center;"> <p><i>Original circuit</i></p>  </div> <div style="text-align: center;"> <p><i>Thevenin equivalent circuit</i></p>  </div> </div>		
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <div style="display: flex; justify-content: space-between; align-items: flex-start; padding: 10px;"> <div style="width: 30%;"> $V_{\text{supply}} =$ </div> <div style="width: 30%;"> $R_1 =$ $R_2 =$ </div> <div style="width: 30%;"> $R_3 =$ $R_{\text{load}} =$ </div> </div>		
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <div style="padding: 10px;"> <div style="text-align: center; margin-bottom: 20px;"> Predicted </div> <div style="display: flex; justify-content: space-between;"> <div style="width: 45%;"> V_{thevenin} <input style="width: 100%;" type="text"/> </div> <div style="width: 45%;"> R_{thevenin} <input style="width: 100%;" type="text"/> </div> </div> <div style="display: flex; justify-content: space-between;"> <div style="width: 45%;"> <div style="text-align: center; margin-bottom: 5px;"> Measured <small>(in original circuit)</small> </div> <div style="display: flex;"> V_{load} <input style="width: 100%;" type="text"/> </div> </div> <div style="width: 45%;"> <div style="text-align: center; margin-bottom: 5px;"> Measured <small>(in Thevenin equivalent circuit)</small> </div> <div style="display: flex;"> <input style="width: 100%;" type="text"/> </div> </div> </div> </div>		

file 03469

Answer 2

Use circuit simulation software to verify your predicted and measured parameter values.



Notes 2

Use a variable-voltage, regulated power supply for $V_{thevenin}$, and a fixed-voltage supply for V_{source} . Specify standard resistor values, all between $1\text{ k}\Omega$ and $100\text{ k}\Omega$ (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k, 47k, 68k, etc.) for resistors in the original circuit. A decade box or potentiometer will suffice for $R_{thevenin}$.

In case it is not already crystal-clear, I want students to build *two different circuits* for this exercise: the "original" circuit and also a "Thevenin equivalent" circuit, then plug the exact same load resistor into both circuits (one at a time) to see that the voltage across it is the same in both cases. Many students seem to struggle with the basic concept of equivalent circuits, and I have found this exercise (once successfully completed) to be excellent for "making it real" to these students.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Question 3

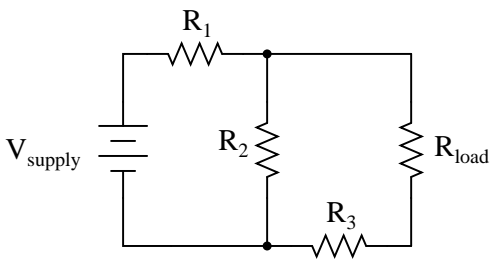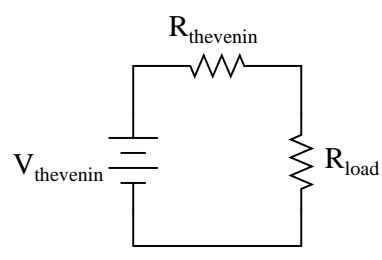Competency: Thevenin's theorem		Version:																
Schematic																		
<p><i>Original circuit</i></p> 	<p><i>Thevenin equivalent circuit</i></p> 																	
Given conditions																		
$V_{\text{supply}} =$	$R_1 =$ $R_3 =$	$R_2 =$ $R_{\text{load}} =$																
Parameters																		
<table style="width: 100%; border-collapse: collapse;"> <tr> <td colspan="3" style="text-align: center; padding-bottom: 10px;">Predicted</td> </tr> <tr> <td style="width: 15%; padding-right: 10px;">V_{thevenin}</td> <td colspan="2" style="border: 1px solid black; height: 25px;"></td> </tr> <tr> <td style="padding-right: 10px;">R_{thevenin}</td> <td colspan="2" style="border: 1px solid black; height: 25px;"></td> </tr> <tr> <td colspan="3" style="padding-top: 20px;"> <table style="width: 100%; border-collapse: collapse;"> <tr> <td style="width: 50%; text-align: center; padding-bottom: 5px;">Measured (in original circuit)</td> <td style="width: 50%; text-align: center; padding-bottom: 5px;">Measured (in Thevenin equivalent circuit)</td> </tr> <tr> <td style="padding-right: 20px;">V_{load}</td> <td style="border: 1px solid black; height: 25px;"></td> </tr> </table> </td> </tr> </table>			Predicted			V_{thevenin}			R_{thevenin}			<table style="width: 100%; border-collapse: collapse;"> <tr> <td style="width: 50%; text-align: center; padding-bottom: 5px;">Measured (in original circuit)</td> <td style="width: 50%; text-align: center; padding-bottom: 5px;">Measured (in Thevenin equivalent circuit)</td> </tr> <tr> <td style="padding-right: 20px;">V_{load}</td> <td style="border: 1px solid black; height: 25px;"></td> </tr> </table>			Measured (in original circuit)	Measured (in Thevenin equivalent circuit)	V_{load}	
Predicted																		
V_{thevenin}																		
R_{thevenin}																		
<table style="width: 100%; border-collapse: collapse;"> <tr> <td style="width: 50%; text-align: center; padding-bottom: 5px;">Measured (in original circuit)</td> <td style="width: 50%; text-align: center; padding-bottom: 5px;">Measured (in Thevenin equivalent circuit)</td> </tr> <tr> <td style="padding-right: 20px;">V_{load}</td> <td style="border: 1px solid black; height: 25px;"></td> </tr> </table>			Measured (in original circuit)	Measured (in Thevenin equivalent circuit)	V_{load}													
Measured (in original circuit)	Measured (in Thevenin equivalent circuit)																	
V_{load}																		

file 03471

Answer 3

Use circuit simulation software to verify your predicted and measured parameter values.



Notes 3

Use a variable-voltage, regulated power supply for $V_{thevenin}$, and a fixed-voltage supply for V_{source} . Specify standard resistor values, all between $1\text{ k}\Omega$ and $100\text{ k}\Omega$ (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k, 47k, 68k, etc.) for resistors in the original circuit. A decade box or potentiometer will suffice for $R_{thevenin}$.

In case it is not already crystal-clear, I want students to build *two different circuits* for this exercise: the "original" circuit and also a "Thevenin equivalent" circuit, then plug the exact same load resistor into both circuits (one at a time) to see that the voltage across it is the same in both cases. Many students seem to struggle with the basic concept of equivalent circuits, and I have found this exercise (once successfully completed) to be excellent for "making it real" to these students.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Question 4

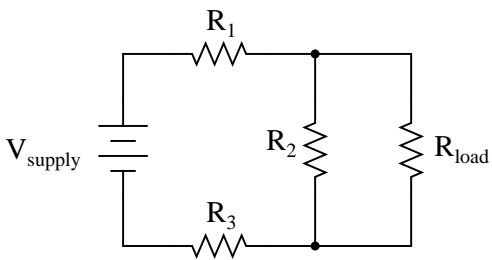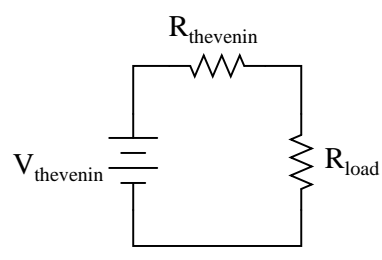Competency: Thevenin's theorem		Version:												
Schematic														
<p><i>Original circuit</i></p> 	<p><i>Thevenin equivalent circuit</i></p> 													
Given conditions														
$V_{\text{supply}} =$	$R_1 =$	$R_2 =$												
	$R_3 =$	$R_{\text{load}} =$												
Parameters														
<table style="width: 100%; border-collapse: collapse;"> <tr> <td colspan="2" style="text-align: center; padding-bottom: 5px;">Predicted</td> </tr> <tr> <td style="width: 15%; padding-right: 10px;">V_{thevenin}</td> <td><input style="width: 100%;" type="text"/></td> </tr> <tr> <td style="padding-right: 10px;">R_{thevenin}</td> <td><input style="width: 100%;" type="text"/></td> </tr> <tr> <td colspan="2" style="padding-top: 20px;"> <table style="width: 100%; border-collapse: collapse;"> <tr> <td style="width: 50%; text-align: center; padding-bottom: 5px;">Measured (in original circuit)</td> <td style="width: 50%; text-align: center; padding-bottom: 5px;">Measured (in Thevenin equivalent circuit)</td> </tr> <tr> <td style="padding-right: 10px;">V_{load}</td> <td><input style="width: 100%;" type="text"/></td> </tr> </table> </td> </tr> </table>			Predicted		V_{thevenin}	<input style="width: 100%;" type="text"/>	R_{thevenin}	<input style="width: 100%;" type="text"/>	<table style="width: 100%; border-collapse: collapse;"> <tr> <td style="width: 50%; text-align: center; padding-bottom: 5px;">Measured (in original circuit)</td> <td style="width: 50%; text-align: center; padding-bottom: 5px;">Measured (in Thevenin equivalent circuit)</td> </tr> <tr> <td style="padding-right: 10px;">V_{load}</td> <td><input style="width: 100%;" type="text"/></td> </tr> </table>		Measured (in original circuit)	Measured (in Thevenin equivalent circuit)	V_{load}	<input style="width: 100%;" type="text"/>
Predicted														
V_{thevenin}	<input style="width: 100%;" type="text"/>													
R_{thevenin}	<input style="width: 100%;" type="text"/>													
<table style="width: 100%; border-collapse: collapse;"> <tr> <td style="width: 50%; text-align: center; padding-bottom: 5px;">Measured (in original circuit)</td> <td style="width: 50%; text-align: center; padding-bottom: 5px;">Measured (in Thevenin equivalent circuit)</td> </tr> <tr> <td style="padding-right: 10px;">V_{load}</td> <td><input style="width: 100%;" type="text"/></td> </tr> </table>		Measured (in original circuit)	Measured (in Thevenin equivalent circuit)	V_{load}	<input style="width: 100%;" type="text"/>									
Measured (in original circuit)	Measured (in Thevenin equivalent circuit)													
V_{load}	<input style="width: 100%;" type="text"/>													

file 03470

Answer 4

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 4

Use a variable-voltage, regulated power supply for $V_{thevenin}$, and a fixed-voltage supply for V_{source} . Specify standard resistor values, all between $1\text{ k}\Omega$ and $100\text{ k}\Omega$ (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k, 47k, 68k, etc.) for resistors in the original circuit. A decade box or potentiometer will suffice for $R_{thevenin}$.

In case it is not already crystal-clear, I want students to build *two different circuits* for this exercise: the "original" circuit and also a "Thevenin equivalent" circuit, then plug the exact same load resistor into both circuits (one at a time) to see that the voltage across it is the same in both cases. Many students seem to struggle with the basic concept of equivalent circuits, and I have found this exercise (once successfully completed) to be excellent for "making it real" to these students.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Question 5

Competency: Thevenin's theorem		Version:
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="display: flex; justify-content: space-around; align-items: flex-start; padding: 10px;"> <div style="text-align: center;"> <p><i>Original circuit</i></p> </div> <div style="text-align: center;"> <p><i>Thevenin equivalent circuit</i></p> </div> </div>		
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <div style="display: flex; justify-content: space-around; align-items: flex-start; padding: 10px;"> <div style="text-align: right; padding-right: 20px;">$V_{\text{supply}} =$</div> <div style="text-align: right; padding-right: 20px;">$R_1 =$</div> <div style="text-align: right; padding-right: 20px;">$R_2 =$</div> <div style="text-align: right; padding-right: 20px;">$R_{\text{load}} =$</div> <div style="text-align: right; padding-right: 20px;">$R_3 =$</div> <div style="text-align: right; padding-right: 20px;">$R_4 =$</div> </div>		
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <div style="display: flex; justify-content: space-between; align-items: flex-start; padding: 10px;"> <div style="width: 45%;"> <p style="text-align: center; margin-bottom: 10px;">Predicted</p> <div style="display: flex; align-items: center; margin-bottom: 10px;"> V_{thevenin} <input style="width: 100px; height: 25px; margin-left: 10px;" type="text"/> </div> <div style="display: flex; align-items: center;"> R_{thevenin} <input style="width: 100px; height: 25px; margin-left: 10px;" type="text"/> </div> </div> <div style="width: 50%;"> <div style="display: flex; justify-content: space-around; margin-bottom: 10px;"> <div style="text-align: center;"> <p>Measured (in original circuit)</p> </div> <div style="text-align: center;"> <p>Measured (in Thevenin equivalent circuit)</p> </div> </div> <div style="display: flex; align-items: center;"> <div style="display: flex; align-items: center; margin-right: 20px;"> V_{load} <input style="width: 100px; height: 25px; margin-left: 10px;" type="text"/> </div> <input style="width: 100px; height: 25px;" type="text"/> </div> </div> </div>		

file 01933

Answer 5

Use circuit simulation software to verify your predicted and measured parameter values.



Notes 5

Use a variable-voltage, regulated power supply for $V_{thevenin}$, and a fixed-voltage supply for V_{source} . Specify standard resistor values, all between $1\text{ k}\Omega$ and $100\text{ k}\Omega$ (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k, 47k, 68k, etc.) for resistors in the original circuit. A decade box or potentiometer will suffice for $R_{thevenin}$.

In case it is not already crystal-clear, I want students to build *two different circuits* for this exercise: the "original" circuit and also a "Thevenin equivalent" circuit, then plug the exact same load resistor into both circuits (one at a time) to see that the voltage across it is the same in both cases. Many students seem to struggle with the basic concept of equivalent circuits, and I have found this exercise (once successfully completed) to be excellent for "making it real" to these students.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Question 6

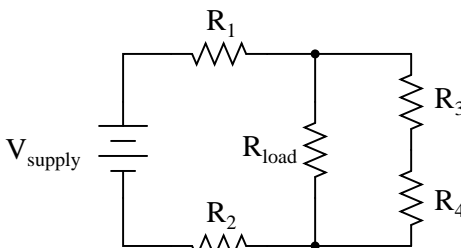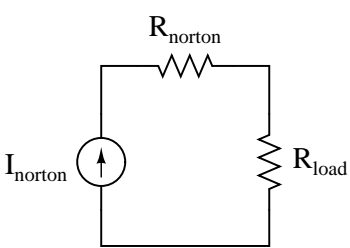Competency: Norton's theorem		Version:
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="display: flex; justify-content: space-around; align-items: flex-start; padding: 10px;"> <div style="text-align: center;"> <p><i>Original circuit</i></p>  </div> <div style="text-align: center;"> <p><i>Norton equivalent circuit</i></p>  </div> </div>		
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <div style="display: flex; justify-content: space-between; align-items: flex-start; padding: 10px;"> <div style="text-align: right; width: 20%;"> $V_{\text{supply}} =$ </div> <div style="text-align: right; width: 15%;"> $R_1 =$ $R_3 =$ </div> <div style="text-align: right; width: 15%;"> $R_2 =$ $R_4 =$ </div> <div style="text-align: right; width: 50%;"> $R_{\text{load}} =$ </div> </div>		
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <div style="display: flex; flex-direction: column; align-items: flex-start; padding: 10px;"> <div style="margin-bottom: 20px;"> <p style="text-align: center; margin-bottom: 5px;">Predicted</p> <div style="display: flex; align-items: center; margin-bottom: 10px;"> I_{norton} <div style="border: 1px solid black; width: 100px; height: 25px; margin-left: 10px;"></div> </div> <div style="display: flex; align-items: center;"> R_{thevenin} <div style="border: 1px solid black; width: 100px; height: 25px; margin-left: 10px;"></div> </div> </div> <div> <div style="display: flex; justify-content: space-around; width: 100%;"> <div style="text-align: center; width: 45%;"> <p>Measured (in original circuit)</p> <div style="display: flex; align-items: center;"> V_{load} <div style="border: 1px solid black; width: 100px; height: 25px; margin-left: 10px;"></div> </div> </div> <div style="text-align: center; width: 45%;"> <p>Measured (in Norton equivalent)</p> <div style="border: 1px solid black; width: 100px; height: 25px; margin-left: 10px;"></div> </div> </div> </div> </div>		

file 01934


Answer 6

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 6

Use a variable-voltage, regulated power supply for I_{norton} , and a fixed-voltage supply for V_{source} . Specify standard resistor values, all between $1\text{ k}\Omega$ and $100\text{ k}\Omega$ (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k, 47k, 68k, etc.) for resistors in the original circuit. A decade box or potentiometer will suffice for R_{norton} .

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

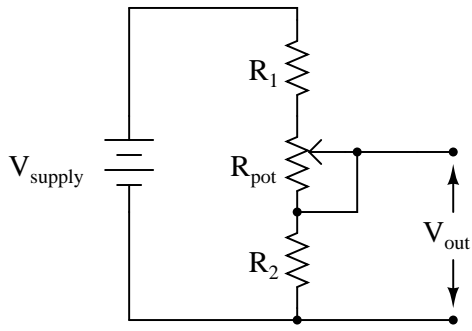Competency: Voltage divider with limited range		Version:												
<div style="border: 1px solid black; padding: 2px; margin-bottom: 10px;">Description</div> <p style="text-align: center;">Use simultaneous equations to calculate values for resistors R_1 and R_2 that will limit the range of voltage adjustment to the specified minimum and maximum values.</p>														
<div style="border: 1px solid black; padding: 2px; margin-bottom: 10px;">Schematic</div> 														
<div style="border: 1px solid black; padding: 2px; margin-bottom: 10px;">Given conditions</div> <div style="display: flex; justify-content: space-between; align-items: flex-start;"> <div style="width: 30%;"> $V_{\text{supply}} =$ </div> <div style="width: 30%;"> $R_{\text{pot}} =$ </div> <div style="width: 30%; text-align: right;"> $V_{\text{out}} (\text{max}) =$ $V_{\text{out}} (\text{min}) =$ </div> </div>														
<div style="border: 1px solid black; padding: 2px; margin-bottom: 10px;">Parameters</div> <table style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="width: 10%;"></th> <th style="width: 40%; text-align: center;">Calculated</th> <th style="width: 10%;"></th> <th style="width: 40%; text-align: center;">Measured</th> </tr> </thead> <tbody> <tr> <td style="text-align: right;">R_1</td> <td style="border: 1px solid black; width: 100px; height: 25px;"></td> <td style="text-align: right;">$V_{\text{out}} (\text{min})$</td> <td style="border: 1px solid black; width: 100px; height: 25px;"></td> </tr> <tr> <td style="text-align: right;">R_2</td> <td style="border: 1px solid black; width: 100px; height: 25px;"></td> <td style="text-align: right;">$V_{\text{out}} (\text{max})$</td> <td style="border: 1px solid black; width: 100px; height: 25px;"></td> </tr> </tbody> </table>				Calculated		Measured	R_1		$V_{\text{out}} (\text{min})$		R_2		$V_{\text{out}} (\text{max})$	
	Calculated		Measured											
R_1		$V_{\text{out}} (\text{min})$												
R_2		$V_{\text{out}} (\text{max})$												
<div style="border: 1px solid black; padding: 2px; margin-bottom: 10px;">Equations</div> <div style="height: 150px;"></div>														

Answer 7

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 7

The purpose of this exercise is for students to use simultaneous equations to arrive at values for fixed resistors R_1 and R_2 that will limit output voltage adjustment to the limits specified.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.