

## Performance-based assessments for DC circuit competencies

This worksheet and all related files are licensed under the Creative Commons Attribution License, version 1.0. To view a copy of this license, visit <http://creativecommons.org/licenses/by/1.0/>, or send a letter to Creative Commons, 559 Nathan Abbott Way, Stanford, California 94305, USA. The terms and conditions of this license allow for free copying, distribution, and/or modification of all licensed works by the general public.

---

The purpose of these assessments is for instructors to accurately measure the learning of their electronics students, in a way that melds theoretical knowledge with hands-on application. In each assessment, students are asked to predict the behavior of a circuit from a schematic diagram and component values, then they build that circuit and measure its real behavior. If the behavior matches the predictions, the student then simulates the circuit on computer and presents the three sets of values to the instructor. If not, then the student then must correct the error(s) and once again compare measurements to predictions. Grades are based on the number of attempts required before all predictions match their respective measurements.

You will notice that no component values are given in this worksheet. The *instructor* chooses component values suitable for the students' parts collections, and ideally chooses different values for each student so that no two students are analyzing and building the exact same circuit. These component values may be hand-written on the assessment sheet, printed on a separate page, or incorporated into the document by editing the graphic image.

This is the procedure I envision for managing such assessments:

1. The instructor hands out individualized assessment sheets to each student.
2. Each student predicts their circuit's behavior at their desks using pencil, paper, and calculator (if appropriate).
3. Each student builds their circuit at their desk, under such conditions that it is impossible for them to verify their predictions using test equipment. Usually this will mean the use of a multimeter only (for measuring component values), but in some cases even the use of a multimeter would not be appropriate.
4. When ready, each student brings their predictions and completed circuit up to the instructor's desk, where any necessary test equipment is already set up to operate and test the circuit. There, the student sets up their circuit and takes measurements to compare with predictions.
5. If any measurement fails to match its corresponding prediction, the student goes back to their own desk with their circuit and their predictions in hand. There, the student tries to figure out where the error is and how to correct it.
6. Students repeat these steps as many times as necessary to achieve correlation between all predictions and measurements. The instructor's task is to count the number of attempts necessary to achieve this, which will become the basis for a percentage grade.
7. (OPTIONAL) As a final verification, each student simulates the same circuit on computer, using circuit simulation software (Spice, Multisim, etc.) and presenting the results to the instructor as a final pass/fail check.

These assessments more closely mimic real-world work conditions than traditional written exams:

- Students cannot pass such assessments only knowing circuit theory or only having hands-on construction and testing skills – they must be proficient at both.
- Students do not receive the “authoritative answers” from the instructor. Rather, they learn to validate their answers through real circuit measurements.
- Just as on the job, the work isn't complete until *all errors* are corrected.
- Students must recognize and correct their own errors, rather than having someone else do it for them.
- Students must be fully prepared on exam days, bringing not only their calculator and notes, but also their tools, breadboard, and circuit components.

Instructors may elect to reveal the assessments before test day, and even use them as preparatory labwork and/or discussion questions. Remember that there is absolutely nothing wrong with “teaching to

the test” *so long as the test is valid*. Normally, it is bad to reveal test material in detail prior to test day, lest students merely memorize responses in advance. With performance-based assessments, however, there is no way to pass without truly understanding the subject(s).

Question 1

Competency: <b>Voltage divider circuit</b>		Version:	
Schematic			
Given conditions			
$V_{\text{supply}} =$		$V_{\text{out}} =$	
Parameters			
	Predicted	Measured	
$I_{\text{supply}}$			
$V_{R1}$			
$V_{R2}$			
			Predicted      Measured
			$I_{R1}$
			$I_{R2}$
$\frac{V_{\text{out}}}{V_{\text{supply}}}$ (Ratio)		Predicted	Calculated (from measurements)
Fault analysis			
Suppose component <span style="border: 1px solid black; display: inline-block; width: 50px; height: 20px; vertical-align: middle;"></span> fails <div style="display: inline-block; vertical-align: middle; margin-left: 10px;"> <input type="checkbox"/> open    <input type="checkbox"/> other _____  <input type="checkbox"/> shorted         </div>			
<i>What will happen in the circuit?</i>			

file 03176

---

#### Answer 1

Use circuit simulation software to verify your predicted and measured parameter values.

---

#### Notes 1

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Students will have to choose resistor values appropriate to the task.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Question 2

Competency: <b>Current divider circuit</b>		Version:	
Schematic			
Given conditions			
$I_{\text{supply}} =$		$I_{\text{out}} =$	
Parameters			
	Predicted	Measured	
$V_{\text{supply}}$			
$I_{R1}$			$V_{R1}$
$I_{R2}$			$V_{R2}$
$\frac{I_{\text{out}}}{I_{\text{supply}}}$ (Ratio)		Predicted	Calculated (from measurements)
Fault analysis			
Suppose component <span style="border: 1px solid black; display: inline-block; width: 50px; height: 20px; vertical-align: middle;"></span> fails <div style="display: inline-block; vertical-align: middle; margin-left: 10px;"> <input type="checkbox"/> open    <input type="checkbox"/> other _____  <input type="checkbox"/> shorted         </div>			
<i>What will happen in the circuit?</i>			

file 03177

---

#### Answer 2

Use circuit simulation software to verify your predicted and measured parameter values.

---

#### Notes 2

Use a variable-current, regulated power supply to supply any amount of DC current below a few milliamps. Students will have to choose resistor values appropriate to the task. I recommend low-value resistors so as to keep the voltage drop (and power dissipation!) low.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Question 3

Competency: <b>Series-parallel DC resistor circuit</b>		Version:	
Schematic			
Given conditions			
$V_{\text{supply}} =$	$R_1 =$	$R_2 =$	$R_3 =$
Parameters			
	Predicted	Measured	
$I_{\text{supply}}$			
$V_{R1}$			$I_{R1}$
$V_{R2}$			$I_{R2}$
$V_{R3}$			$I_{R3}$
Fault analysis			
Suppose component <span style="border: 1px solid black; display: inline-block; width: 50px; height: 20px; vertical-align: middle;"></span> fails <div style="display: inline-block; vertical-align: middle; margin-left: 10px;"> <input type="checkbox"/> open    <input type="checkbox"/> other _____  <input type="checkbox"/> shorted         </div>			
<i>What will happen in the circuit?</i>			

file 01633

---

### Answer 3

Use circuit simulation software to verify your predicted and measured parameter values.

---

### Notes 3

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k $\Omega$  and 100 k $\Omega$  (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k 47k, 68k, etc.).

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.



Question 4

Competency: <b>Series-parallel DC resistor circuit</b>		Version:	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Schematic</div>			
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Given conditions</div>			
$V_{\text{supply}} =$	$R_1 =$	$R_2 =$	$R_3 =$
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Parameters</div>			
	Predicted	Measured	
$I_{\text{supply}}$			$I_{R1}$
$V_{R1}$			$I_{R2}$
$V_{R2}$			$I_{R3}$
$V_{R3}$			
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Fault analysis</div>			
Suppose component <span style="border: 1px solid black; display: inline-block; width: 50px; height: 20px; vertical-align: middle;"></span> fails <div style="display: inline-block; vertical-align: middle; margin-left: 10px;"> <input type="checkbox"/> open    <input type="checkbox"/> other _____  <input type="checkbox"/> shorted         </div>			
<i>What will happen in the circuit?</i>			

file 01631

---

#### Answer 4

Use circuit simulation software to verify your predicted and measured parameter values.

---

#### Notes 4

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k $\Omega$  and 100 k $\Omega$  (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k 47k, 68k, etc.).

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: <b>Series-parallel DC resistor circuit</b>		Version:	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Schematic</div>			
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Given conditions</div>			
$V_{\text{supply}} =$	$R_1 =$	$R_2 =$	$R_3 =$
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Parameters</div>			
	Predicted	Measured	
$I_{\text{supply}}$			$I_{R1}$
$V_{R1}$			$I_{R2}$
$V_{R2}$			$I_{R3}$
$V_{R3}$			
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Fault analysis</div>			
Suppose component <span style="border: 1px solid black; display: inline-block; width: 50px; height: 20px; vertical-align: middle;"></span> fails <div style="display: inline-block; vertical-align: middle; margin-left: 10px;"> <input type="checkbox"/> open    <input type="checkbox"/> other _____  <input type="checkbox"/> shorted         </div>			
<i>What will happen in the circuit?</i>			

---

#### Answer 5

Use circuit simulation software to verify your predicted and measured parameter values.

---

#### Notes 5

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k $\Omega$  and 100 k $\Omega$  (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k 47k, 68k, etc.).

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Question 6

Competency: <b>Series-parallel DC resistor circuit</b>		Version:	
Schematic			
Given conditions			
$V_{\text{supply}} =$	$R_1 =$	$R_2 =$	$R_3 =$
Parameters			
	Predicted	Measured	
$I_{\text{supply}}$	<input type="text"/>	<input type="text"/>	
$V_{R1}$	<input type="text"/>	<input type="text"/>	
$V_{R2}$	<input type="text"/>	<input type="text"/>	
$V_{R3}$	<input type="text"/>	<input type="text"/>	
	Predicted	Measured	
$I_{R1}$	<input type="text"/>	<input type="text"/>	
$I_{R2}$	<input type="text"/>	<input type="text"/>	
$I_{R3}$	<input type="text"/>	<input type="text"/>	
Fault analysis			
Suppose component <input style="width: 50px;" type="text"/> fails <input type="checkbox"/> open <input type="checkbox"/> other _____ <input type="checkbox"/> shorted What will happen in the circuit?     			

file 01630

---

#### Answer 6

Use circuit simulation software to verify your predicted and measured parameter values.


---

#### Notes 6

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k $\Omega$  and 100 k $\Omega$  (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k 47k, 68k, etc.).

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Question 7

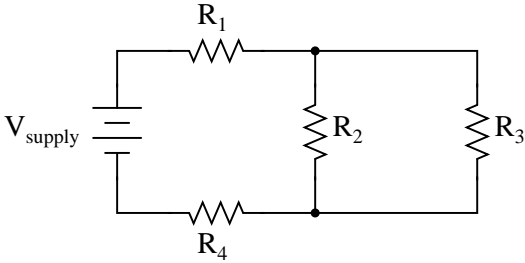Competency: <b>Series-parallel DC resistor circuit</b>		Version:	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Schematic</div>			
			
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Given conditions</div>			
$V_{\text{supply}} =$	$R_1 =$	$R_2 =$	$R_3 =$
$R_4 =$			
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Parameters</div>			
	Predicted	Measured	
$I_{\text{supply}}$			$I_{R1}$
$V_{R1}$			$I_{R2}$
$V_{R2}$			$I_{R3}$
$V_{R3}$			$I_{R4}$
$V_{R4}$			
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Fault analysis</div>			
Suppose component <span style="border: 1px solid black; display: inline-block; width: 40px; height: 15px; vertical-align: middle;"></span> fails <div style="display: inline-block; vertical-align: middle; margin-left: 10px;"> <input type="checkbox"/> open    <input type="checkbox"/> other _____  <input type="checkbox"/> shorted         </div>			
<i>What will happen in the circuit?</i>			

file 01606

---

#### Answer 7

Use circuit simulation software to verify your predicted and measured parameter values.

---


#### Notes 7

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k $\Omega$  and 100 k $\Omega$  (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 8k2, 10k, 22k, 33k, 39k, 47k, 68k, 82k, etc.).

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.



Question 8

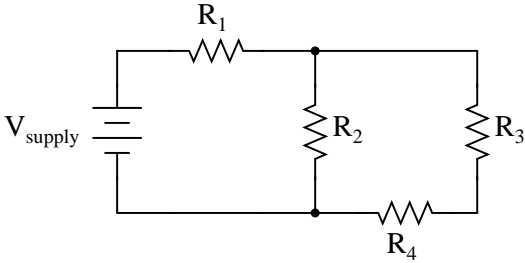Competency: <b>Series-parallel DC resistor circuit</b>		Version:	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Schematic</div>			
			
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Given conditions</div>			
$V_{\text{supply}} =$	$R_1 =$	$R_2 =$	$R_3 =$
$R_4 =$			
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Parameters</div>			
	Predicted	Measured	
$I_{\text{supply}}$			$I_{R1}$
$V_{R1}$			$I_{R2}$
$V_{R2}$			$I_{R3}$
$V_{R3}$			$I_{R4}$
$V_{R4}$			
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Fault analysis</div>			
Suppose component <span style="border: 1px solid black; display: inline-block; width: 40px; height: 15px; vertical-align: middle;"></span> fails <div style="display: inline-block; vertical-align: middle; margin-left: 10px;"> <input type="checkbox"/> open    <input type="checkbox"/> other _____  <input type="checkbox"/> shorted         </div>			
<i>What will happen in the circuit?</i>			

file 01607

---

#### Answer 8

Use circuit simulation software to verify your predicted and measured parameter values.

---

#### Notes 8

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k $\Omega$  and 100 k $\Omega$  (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 8k2, 10k, 22k, 33k, 39k, 47k, 68k, 82k, etc.).

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Question 9

Competency: <b>Series-parallel DC resistor circuit</b>		Version:	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Schematic</div>			
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Given conditions</div>			
$V_{\text{supply}} =$	$R_1 =$	$R_2 =$	$R_3 =$
$R_4 =$			
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Parameters</div>			
	Predicted	Measured	
$I_{\text{supply}}$			$I_{R1}$
$V_{R1}$			$I_{R2}$
$V_{R2}$			$I_{R3}$
$V_{R3}$			$I_{R4}$
$V_{R4}$			
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Fault analysis</div>			
Suppose component <span style="border: 1px solid black; display: inline-block; width: 40px; height: 15px; vertical-align: middle;"></span> fails <div style="display: inline-block; vertical-align: middle; margin-left: 10px;"> <input type="checkbox"/> open    <input type="checkbox"/> other _____  <input type="checkbox"/> shorted         </div>			
<i>What will happen in the circuit?</i>			

file 01608

---

#### Answer 9

Use circuit simulation software to verify your predicted and measured parameter values.

---

#### Notes 9

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k $\Omega$  and 100 k $\Omega$  (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 8k2, 10k, 22k, 33k, 39k, 47k, 68k, 82k, etc.).

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: <b>Custom rheostat range</b>		Version:																							
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="text-align: center; margin: 10px 0;"> </div>																									
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <div style="display: flex; justify-content: space-between; margin-top: 10px;"> <div> <math>R_{\text{total}}</math> (minimum) =   <math>R_{\text{pot}}</math> = </div> <div> <math>R_{\text{total}}</math> (maximum) = </div> </div>																									
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; border-collapse: collapse; margin-top: 10px;"> <thead> <tr> <th style="width: 10%;"></th> <th style="width: 15%; text-align: center;">Ideal</th> <th style="width: 15%; text-align: center;">Attained</th> <th style="width: 60%;"></th> </tr> </thead> <tbody> <tr> <td><math>R_1</math></td> <td><div style="border: 1px solid black; width: 100px; height: 25px;"></div></td> <td><div style="border: 1px solid black; width: 100px; height: 25px;"></div></td> <td rowspan="2" style="vertical-align: middle; padding-left: 10px;">           Resistors <math>R_1</math> and <math>R_2</math> may need to be series-parallel networks in order to achieve the necessary values.         </td> </tr> <tr> <td><math>R_2</math></td> <td><div style="border: 1px solid black; width: 100px; height: 25px;"></div></td> <td><div style="border: 1px solid black; width: 100px; height: 25px;"></div></td> </tr> <tr> <td></td> <td></td> <td style="text-align: center;">Measured</td> <td></td> </tr> <tr> <td><math>R_{\text{total}}</math> (minimum)</td> <td></td> <td><div style="border: 1px solid black; width: 100px; height: 25px;"></div></td> <td></td> </tr> <tr> <td><math>R_{\text{total}}</math> (maximum)</td> <td></td> <td><div style="border: 1px solid black; width: 100px; height: 25px;"></div></td> <td></td> </tr> </tbody> </table>				Ideal	Attained		$R_1$	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>	Resistors $R_1$ and $R_2$ may need to be series-parallel networks in order to achieve the necessary values.	$R_2$	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>			Measured		$R_{\text{total}}$ (minimum)		<div style="border: 1px solid black; width: 100px; height: 25px;"></div>		$R_{\text{total}}$ (maximum)		<div style="border: 1px solid black; width: 100px; height: 25px;"></div>	
	Ideal	Attained																							
$R_1$	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>	Resistors $R_1$ and $R_2$ may need to be series-parallel networks in order to achieve the necessary values.																						
$R_2$	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>																							
		Measured																							
$R_{\text{total}}$ (minimum)		<div style="border: 1px solid black; width: 100px; height: 25px;"></div>																							
$R_{\text{total}}$ (maximum)		<div style="border: 1px solid black; width: 100px; height: 25px;"></div>																							
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Fault analysis</div> <div style="margin-top: 10px;">       Suppose component <div style="border: 1px solid black; width: 50px; height: 20px; display: inline-block;"></div> fails       <div style="display: inline-block; vertical-align: middle; margin-left: 10px;"> <input type="checkbox"/> open    <input type="checkbox"/> other _____  <input type="checkbox"/> shorted       </div> </div> <p style="margin-top: 10px;"><i>What will happen in the circuit?</i></p> <div style="height: 150px; border: 1px solid black; margin-top: 10px;"></div>																									

---


Answer 10

Use circuit simulation software to verify your predicted and measured parameter values.

---

Notes 10

Be sure to remind your students that resistances  $R_1$  and  $R_2$  may need to be series-parallel networks in themselves, to achieve the necessary values. An alternative you may wish to permit is the use of 10-turn (precision) potentiometers connected as rheostats for  $R_1$  and  $R_2$ . This way the circuit's minimum and maximum values may be precisely calibrated. The main potentiometer,  $R_{pot1}$ , should be a 3/4 turn unit, to allow fast checking of minimum and maximum total resistance, and it should be some common value such as 1 k $\Omega$  or 10 k $\Omega$ .

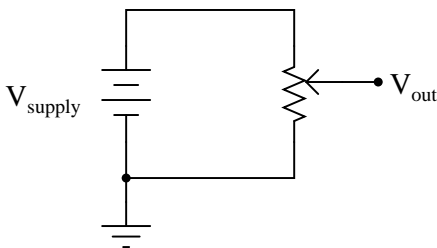Competency: <b>Potentiometer as voltage divider</b>	Version:
<div style="border: 1px solid black; padding: 2px; margin-bottom: 5px;">Description</div> <p style="text-align: center;">You must set the potentiometer to the correct position to achieve <math>V_{out}</math> given <math>V_{supply}</math> <i>before</i> it is connected to <math>V_{supply}</math> for testing.</p>	
<div style="border: 1px solid black; padding: 2px; margin-bottom: 5px;">Schematic</div> <div style="text-align: center; margin-top: 20px;">  </div>	
<div style="border: 1px solid black; padding: 2px; margin-bottom: 5px;">Given conditions</div> <div style="display: flex; justify-content: space-around; margin-top: 20px;"> <div><math>V_{supply} =</math></div> <div><math>V_{out} =</math></div> </div>	
<div style="border: 1px solid black; padding: 2px; margin-bottom: 5px;">Parameters</div> <div style="margin-top: 20px;"> <div style="display: flex; justify-content: space-between; align-items: flex-start;"> <div style="text-align: right; margin-right: 10px;"><math>V_{out}</math></div> <div style="text-align: center;"> <p>Measured</p> <input style="width: 100px; height: 25px;" type="text"/> </div> </div> <div style="display: flex; justify-content: space-between; align-items: flex-start; margin-top: 20px;"> <div style="text-align: right; margin-right: 10px;">Error (%)</div> <div style="text-align: center;"> <p>Calculated</p> <input style="width: 100px; height: 25px;" type="text"/> </div> <div style="text-align: left; margin-left: 20px;"> <math display="block">\frac{V_{out(actual)} - V_{out(ideal)}}{V_{out(ideal)}} \times 100\%</math> </div> </div> </div>	

---

Answer 11

Use circuit simulation software to verify your predicted and measured parameter values.


---

Notes 11

Students need not measure potentiometer shaft angles in order to do this exercise. Rather, all they need to do is measure resistance between the wiper and the two outer terminals to set the potentiometer to a position where it will produce the specified division of voltage.

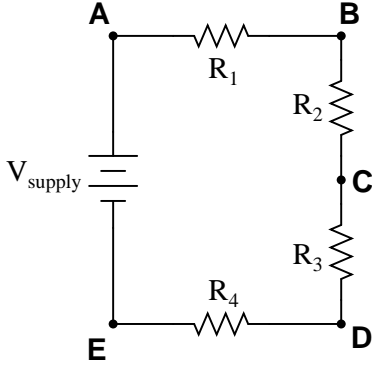An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.



Competency: <b>Kirchhoff's Voltage Law</b>	Version:																																				
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="text-align: center; margin: 10px 0;">  </div>																																					
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <p style="margin-top: 10px;"><math>V_{\text{supply}} = \text{Any whole-number value evenly divisible by 4}</math></p> <p><math>R_1 = R_2 = R_3 = R_4 =</math></p>																																					
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="width: 15%;"></th> <th style="width: 15%; text-align: center;">Predicted</th> <th style="width: 15%; text-align: center;">Measured</th> <th style="width: 15%;"></th> <th style="width: 15%; text-align: center;">Predicted</th> <th style="width: 15%; text-align: center;">Measured</th> </tr> </thead> <tbody> <tr> <td><math>V_{R1}</math></td> <td><input style="width: 80%;" type="text"/></td> <td><input style="width: 80%;" type="text"/></td> <td><math>V_{R3}</math></td> <td><input style="width: 80%;" type="text"/></td> <td><input style="width: 80%;" type="text"/></td> </tr> <tr> <td><math>V_{R2}</math></td> <td><input style="width: 80%;" type="text"/></td> <td><input style="width: 80%;" type="text"/></td> <td><math>V_{R4}</math></td> <td><input style="width: 80%;" type="text"/></td> <td><input style="width: 80%;" type="text"/></td> </tr> <tr> <td><math>V_{BD}</math></td> <td><input style="width: 80%;" type="text"/></td> <td><input style="width: 80%;" type="text"/></td> <td><math>V_{DA}</math></td> <td><input style="width: 80%;" type="text"/></td> <td><input style="width: 80%;" type="text"/></td> </tr> <tr> <td><math>V_{BE}</math></td> <td><input style="width: 80%;" type="text"/></td> <td><input style="width: 80%;" type="text"/></td> <td><math>V_{DC}</math></td> <td><input style="width: 80%;" type="text"/></td> <td><input style="width: 80%;" type="text"/></td> </tr> <tr> <td><math>V_{AC}</math></td> <td><input style="width: 80%;" type="text"/></td> <td><input style="width: 80%;" type="text"/></td> <td><math>V_{CE}</math></td> <td><input style="width: 80%;" type="text"/></td> <td><input style="width: 80%;" type="text"/></td> </tr> </tbody> </table> <p style="text-align: center; margin-top: 20px;"><i>Note: "<math>V_{BD}</math>" means voltage measured with the red lead touching <b>B</b> and the black lead touching <b>D</b>.</i></p>			Predicted	Measured		Predicted	Measured	$V_{R1}$	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>	$V_{R3}$	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>	$V_{R2}$	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>	$V_{R4}$	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>	$V_{BD}$	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>	$V_{DA}$	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>	$V_{BE}$	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>	$V_{DC}$	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>	$V_{AC}$	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>	$V_{CE}$	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>
	Predicted	Measured		Predicted	Measured																																
$V_{R1}$	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>	$V_{R3}$	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>																																
$V_{R2}$	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>	$V_{R4}$	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>																																
$V_{BD}$	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>	$V_{DA}$	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>																																
$V_{BE}$	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>	$V_{DC}$	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>																																
$V_{AC}$	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>	$V_{CE}$	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>																																

---

#### Answer 12

Use circuit simulation software to verify your predicted and measured parameter values.

---

#### Notes 12

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: <b>Kirchhoff's Current Law</b>		Version:																			
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="text-align: center; margin: 10px 0;"> </div>																					
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <p style="margin-top: 10px;"><math>I_{\text{supply}} = \text{Any whole-number milliamp value evenly divisible by 4}</math></p> <p><math>R_1 = R_2 = R_3 = R_4 = R_5 =</math></p>																					
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; margin-top: 10px;"> <thead> <tr> <th></th> <th style="text-align: center;">Predicted</th> <th style="text-align: center;">Measured</th> <th></th> <th style="text-align: center;">Predicted</th> <th style="text-align: center;">Measured</th> </tr> </thead> <tbody> <tr> <td><math>I_{R1}</math></td> <td><input style="width: 80px;" type="text"/></td> <td><input style="width: 80px;" type="text"/></td> <td><math>I_{R3}</math></td> <td><input style="width: 80px;" type="text"/></td> <td><input style="width: 80px;" type="text"/></td> </tr> <tr> <td><math>I_{R2}</math></td> <td><input style="width: 80px;" type="text"/></td> <td><input style="width: 80px;" type="text"/></td> <td><math>I_{R4}</math></td> <td><input style="width: 80px;" type="text"/></td> <td><input style="width: 80px;" type="text"/></td> </tr> </tbody> </table> <p style="margin-top: 20px; text-align: center;">Sketch directions and magnitudes of currents at these nodes:</p> <div style="display: flex; justify-content: space-around; align-items: flex-end; margin-top: 10px;"> <div style="text-align: center;"> <p><b>A</b></p> </div> <div style="text-align: center;"> <p><b>B</b></p> </div> <div style="text-align: center;"> <p><b>C</b></p> </div> <div style="text-align: center;"> <p><b>D</b></p> </div> </div>					Predicted	Measured		Predicted	Measured	$I_{R1}$	<input style="width: 80px;" type="text"/>	<input style="width: 80px;" type="text"/>	$I_{R3}$	<input style="width: 80px;" type="text"/>	<input style="width: 80px;" type="text"/>	$I_{R2}$	<input style="width: 80px;" type="text"/>	<input style="width: 80px;" type="text"/>	$I_{R4}$	<input style="width: 80px;" type="text"/>	<input style="width: 80px;" type="text"/>
	Predicted	Measured		Predicted	Measured																
$I_{R1}$	<input style="width: 80px;" type="text"/>	<input style="width: 80px;" type="text"/>	$I_{R3}$	<input style="width: 80px;" type="text"/>	<input style="width: 80px;" type="text"/>																
$I_{R2}$	<input style="width: 80px;" type="text"/>	<input style="width: 80px;" type="text"/>	$I_{R4}$	<input style="width: 80px;" type="text"/>	<input style="width: 80px;" type="text"/>																

---

#### Answer 13

Use circuit simulation software to verify your predicted and measured parameter values.

---

#### Notes 13

I recommend students use a normal regulated (voltage) power supply, adjusting the output voltage until the output current is at 4 mA. 1 k $\Omega$  resistors work well for this circuit, requiring only 6.4 volts from the power supply to achieve 4 mA total current.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: <b>Loaded voltage divider</b>		Version:																								
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="text-align: center; margin-top: 20px;"> </div>																										
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <div style="display: flex; justify-content: space-around; margin-top: 10px;"> <math>V_{\text{supply}} =</math> <math>R_1 =</math> <math>R_2 =</math> <math>R_3 =</math> <math>R_{\text{load1}} =</math> <math>R_{\text{load2}} =</math> </div>																										
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; border-collapse: collapse; margin-top: 10px;"> <thead> <tr> <th></th> <th style="text-align: center; padding: 5px;">Predicted</th> <th style="text-align: center; padding: 5px;">Measured</th> <th></th> <th style="text-align: center; padding: 5px;">Predicted</th> <th style="text-align: center; padding: 5px;">Measured</th> </tr> </thead> <tbody> <tr> <td style="padding: 5px;"><math>I_{\text{supply}}</math></td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> <td style="padding: 5px;"><math>I_{\text{load1}}</math></td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> </tr> <tr> <td style="padding: 5px;"><math>V_A</math></td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> <td style="padding: 5px;"><math>I_{\text{load2}}</math></td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> </tr> <tr> <td style="padding: 5px;"><math>V_B</math></td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> <td style="padding: 5px;"><math>I_{\text{bleed}}</math></td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> </tr> </tbody> </table>				Predicted	Measured		Predicted	Measured	$I_{\text{supply}}$			$I_{\text{load1}}$			$V_A$			$I_{\text{load2}}$			$V_B$			$I_{\text{bleed}}$		
	Predicted	Measured		Predicted	Measured																					
$I_{\text{supply}}$			$I_{\text{load1}}$																							
$V_A$			$I_{\text{load2}}$																							
$V_B$			$I_{\text{bleed}}$																							
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Fault analysis</div> <div style="margin-top: 10px;"> <p>Suppose component <span style="border: 1px solid black; display: inline-block; width: 50px; height: 25px; vertical-align: middle;"></span> fails <span style="margin-left: 10px;"><input type="checkbox"/> open</span> <span style="margin-left: 10px;"><input type="checkbox"/> other _____</span></p> <p><span style="margin-left: 10px;"><input type="checkbox"/> shorted</span></p> <p>What will happen in the circuit?</p> </div>																										

---

Answer 14

Use circuit simulation software to verify your predicted and measured parameter values.

---

Notes 14

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k $\Omega$  and 100 k $\Omega$  (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 8k2, 10k, 22k, 33k, 39k 47k, 68k, 82k, etc.).

I have used this circuit as both a "quick" lab exercise and a troubleshooting exercise, using values of 10 k $\Omega$  for R1, R2, and R3; 15 k $\Omega$  for R(load1); 22 k $\Omega$  for R(load2); and 6 volts for the power supply. Of course, these component values are not critical, but they do provide easy-to-measure voltages and currents without incurring excessive impedances that would cause significant voltmeter loading problems.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: <b>Loaded voltage divider</b>		Version:	
Schematic			
Given conditions			
$V_{\text{supply}} =$	$R_1 =$	$R_2 =$	$R_3 =$
$R_{\text{load1}} =$	$R_{\text{load2}} =$	$R_{\text{load3}} =$	
Parameters			
	Predicted	Measured	
$I_{\text{supply}}$			$I_{\text{load1}}$
$V_A$			$I_{\text{load2}}$
$V_B$			$I_{\text{load3}}$
			$I_{\text{bleed}}$
Fault analysis			
Suppose component <span style="border: 1px solid black; display: inline-block; width: 50px; height: 20px; vertical-align: middle;"></span> fails <div style="display: inline-block; vertical-align: middle; margin-left: 10px;"> <input type="checkbox"/> open    <input type="checkbox"/> other _____  <input type="checkbox"/> shorted         </div>			
<i>What will happen in the circuit?</i>			

---

Answer 15

Use circuit simulation software to verify your predicted and measured parameter values.

---

Notes 15

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k $\Omega$  and 100 k $\Omega$  (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k 47k, 68k, etc.).

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.



<b>Competency: Potentiometer as loaded voltage divider</b> Version:	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Description</div> <p style="margin-top: 10px;">You must set the potentiometer to the correct position to achieve <math>V_{out}</math> given <math>V_{supply}</math> <i>before</i> it is connected to <math>V_{supply}</math> for testing.</p>	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Schematic</div> <div style="text-align: center; margin-top: 20px;"> </div>	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Given conditions</div> <div style="margin-top: 10px;"> <math>V_{supply} =</math>      <math>V_{out} =</math>      <math>R_{pot} =</math>      <math>R_{load} =</math> </div>	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Parameters</div> <div style="margin-top: 10px;"> <div style="display: flex; justify-content: space-between; align-items: flex-start;"> <div style="text-align: right;">Measured</div> <div style="text-align: center;"> <math>V_{out}</math> <input style="width: 100px; height: 30px; border: 1px solid black;" type="text"/> </div> </div> <div style="display: flex; justify-content: space-between; align-items: flex-start; margin-top: 20px;"> <div style="text-align: right;">Error (%)</div> <div style="text-align: center;"> <div style="display: flex; align-items: center;"> <div style="margin-right: 10px;">Calculated</div> <input style="width: 100px; height: 30px; border: 1px solid black;" type="text"/> </div> <math display="block">\frac{V_{out(actual)} - V_{out(ideal)}}{V_{out(ideal)}} \times 100\%</math> </div> </div> </div>	

---

Answer 16

Use circuit simulation software to verify your predicted and measured parameter values.

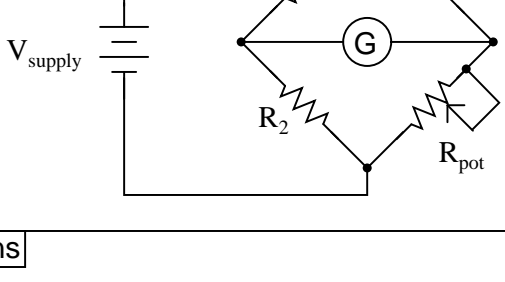
---

Notes 16

Students need not measure potentiometer shaft angles in order to do this exercise. Rather, all they need to do is measure resistance between the wiper and the two outer terminals to set the potentiometer to a position where it will produce the specified division of voltage.

$R_{pot}$  refers to the potentiometer's nominal full-range value (for example, 1 k $\Omega$  or 5 k $\Omega$ ), and not to its particular setting. The setting is what the student must figure out to achieve  $V_{out}$ .

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: <b>Wheatstone bridge</b>	Version:									
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="text-align: center; margin-top: 20px;">  </div>										
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <div style="display: flex; justify-content: space-around; margin-top: 10px;"> <div><math>V_{\text{supply}} =</math></div> <div><math>R_1 =</math></div> <div><math>R_2 =</math></div> <div><math>R_3 =</math></div> </div>										
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; margin-top: 10px;"> <thead> <tr> <th></th> <th style="text-align: center;">Predicted</th> <th style="text-align: center;">Measured</th> </tr> </thead> <tbody> <tr> <td style="width: 20%;"><math>R_{\text{pot}}</math> (balance)</td> <td style="width: 30%; border: 1px solid black; height: 30px;"></td> <td style="width: 30%; border: 1px solid black; height: 30px;"></td> </tr> <tr> <td><math>I_{\text{supply}}</math></td> <td style="border: 1px solid black; height: 30px;"></td> <td style="border: 1px solid black; height: 30px;"></td> </tr> </tbody> </table>			Predicted	Measured	$R_{\text{pot}}$ (balance)			$I_{\text{supply}}$		
	Predicted	Measured								
$R_{\text{pot}}$ (balance)										
$I_{\text{supply}}$										
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Fault analysis</div> <div style="margin-top: 10px;">       Suppose component <span style="border: 1px solid black; display: inline-block; width: 50px; height: 25px; vertical-align: middle;"></span> fails       <div style="display: inline-block; vertical-align: middle; margin-left: 10px;"> <input type="checkbox"/> open  <input type="checkbox"/> shorted       </div> <div style="display: inline-block; vertical-align: middle; margin-left: 10px;"> <input type="checkbox"/> other _____       </div> </div> <p style="margin-top: 10px;"><i>What will happen in the circuit?</i></p>										

---

#### Answer 17


Use circuit simulation software to verify your predicted and measured parameter values.

---

#### Notes 17

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k $\Omega$  and 100 k $\Omega$  (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k 47k, 68k, etc.), and be sure to specify a potentiometer value in excess of the amount required to balance the bridge.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.
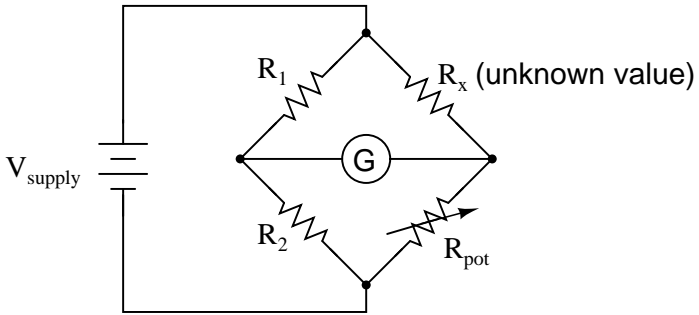
<b>Competency: Bridge resistance measurement</b>		Version:
<b>Schematic</b>		
		
<b>Given conditions</b>		
$V_{\text{supply}} =$	$R_1 =$	$R_2 =$
$R_{\text{pot}} =$ Decade resistance box		
<b>Parameters</b>		
$R_x$	Measured by bridge <div style="border: 1px solid black; width: 100px; height: 20px; margin: 0 auto;"></div>	Measured by ohmmeter <div style="border: 1px solid black; width: 100px; height: 20px; margin: 0 auto;"></div>
<b>Calculations</b>		

---

Answer 18


The ohmmeter's indication is the "final word" on resistance.

---

Notes 18

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Use precision resistors for  $R_1$  and  $R_2$ , and use any standard resistor value for  $R_x$  between 1 k $\Omega$  and 100 k $\Omega$ .

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

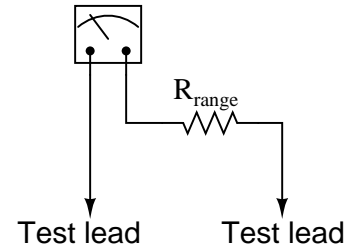Competency: <b>DC voltmeter circuit</b>	Version:												
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="text-align: center; margin-top: 20px;"> <p>Meter movement</p>  <p>Test lead      Test lead</p> </div>													
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <div style="margin-top: 20px;"> <math>I_{F.S.} =</math>      <math>R_{movement} =</math>      Full-scale range =         </div>													
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <div style="margin-top: 20px; text-align: center;"> <table style="margin: auto;"> <tr> <td></td> <td>Predicted</td> <td></td> </tr> <tr> <td><math>R_{range}</math></td> <td><div style="border: 1px solid black; width: 100px; height: 20px;"></div></td> <td></td> </tr> <tr> <td></td> <td>Predicted</td> <td>Measured</td> </tr> <tr> <td>Meter indication with full-scale voltage applied</td> <td><div style="border: 1px solid black; width: 100px; height: 20px;"></div></td> <td><div style="border: 1px solid black; width: 100px; height: 20px;"></div></td> </tr> </table> </div>			Predicted		$R_{range}$	<div style="border: 1px solid black; width: 100px; height: 20px;"></div>			Predicted	Measured	Meter indication with full-scale voltage applied	<div style="border: 1px solid black; width: 100px; height: 20px;"></div>	<div style="border: 1px solid black; width: 100px; height: 20px;"></div>
	Predicted												
$R_{range}$	<div style="border: 1px solid black; width: 100px; height: 20px;"></div>												
	Predicted	Measured											
Meter indication with full-scale voltage applied	<div style="border: 1px solid black; width: 100px; height: 20px;"></div>	<div style="border: 1px solid black; width: 100px; height: 20px;"></div>											
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Calculations</div> <div style="height: 150px; margin-top: 10px;"></div>													

---

Answer 19

Use circuit simulation software to verify your predicted and measured parameter values.


---

Notes 19

Students may use potentiometers in their range resistance networks to achieve precise values. However, they are not allowed to adjust those potentiometers after connecting them to the meter movement – they must set their potentiometer(s) during the "prediction" step of the assessment before the circuit is completely built.

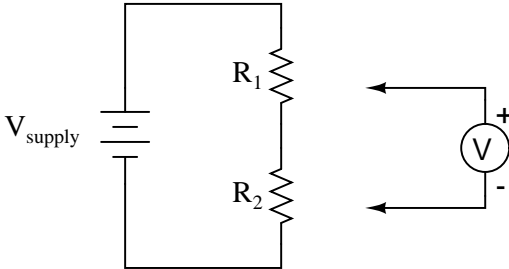An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.



<b>Competency: Voltmeter loading</b>	<b>Version:</b>
<b>Schematic</b>	
	
<b>Given conditions</b>	
$V_{\text{supply}} =$ $R_1 =$ $R_2 =$	
<b>Explanation</b>	
<p>Due to the effects of the voltmeter "loading" the voltage divider circuit, there will be a significant difference between <math>V_{R2}</math> predicted and <math>V_{R2}</math> measured.</p>	
<b>Parameters</b>	
<div style="display: flex; justify-content: space-between; align-items: flex-start;"> <div style="text-align: right; width: 15%;"> <math>V_{R2}</math> </div> <div style="width: 40%;"> <div style="text-align: center; margin-bottom: 10px;"> <b>Predicted</b>  <input style="width: 100px; height: 30px; border: 1px solid black;" type="text"/> </div> <div style="text-align: center; margin-bottom: 10px;"> <b>Measured</b>  <input style="width: 100px; height: 30px; border: 1px solid black;" type="text"/> </div> <div style="display: flex; justify-content: space-around;"> <div style="text-align: center;"> <b>Calculated</b>  <input style="width: 80px; height: 30px; border: 1px solid black;" type="text"/> </div> <div style="text-align: center;"> <b>Advertised</b>  <input style="width: 80px; height: 30px; border: 1px solid black;" type="text"/> </div> </div> </div> <div style="text-align: right; width: 15%;"> <p>(Ideal, with no meter connected)</p> <p>(Real measurement with voltmeter)</p> </div> </div> <div style="margin-top: 20px;"> <div style="display: flex; justify-content: space-between; align-items: flex-start;"> <div style="text-align: right; width: 15%;"> <math>R_{\text{input}}</math> (Meter)         </div> <div style="width: 40%;"> <div style="text-align: center; margin-bottom: 10px;"> <b>Calculated</b>  <input style="width: 100px; height: 30px; border: 1px solid black;" type="text"/> </div> <div style="text-align: center;"> <b>Advertised</b>  <input style="width: 100px; height: 30px; border: 1px solid black;" type="text"/> </div> </div> </div> </div>	

---

## Answer 20

Use circuit simulation software to verify your predicted and measured parameter values.

---

## Notes 20

Be sure to specify resistor values for the voltage divider that will show a marked impact when measured with the type of voltmeter you expect your students to use. If you size the resistors for a modest impact measured with an analog voltmeter ( $20,000\ \Omega/\text{Volt}$ ), your students may not see much of an impact when using a modern digital voltmeter ( $Z_{in} > 10\ \text{M}\Omega$ ).

New students often have a difficult time grasping the main idea of this activity, due to the assumption of the voltmeter's indication always being taken as true. The purpose of this activity is to shatter that assumption: to teach students that electrical measurements are never truly passive – rather, they invariably impact the circuit being measured in some way. Usually, the impact is so small it may be safely ignored. Here, due to the large resistor values used in the divider circuit, the impact of voltmeter usage on the circuit is non-trivial.

Another aspect of this activity that escapes some students' attention is that the circuit must be analyzed twice: once with the meter connected and once without. The point here is that the meter *becomes a component of the circuit when it is connected across  $R_2$ , and thus changes all the voltages and currents.*

Competency: <b>Self-induction</b>	Version:																								
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="text-align: center; padding: 20px;"> <p style="margin: 0;">Pushbutton switch</p> <p style="margin: 0;"><math>V_{\text{supply}}</math></p> <p style="margin: 0;"><math>L_1</math></p> <p style="margin: 0;">Neon lamp</p> </div>																									
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <p style="margin: 10px 0;"><math>V_{\text{supply}} =</math></p>																									
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; margin-top: 10px;"> <thead> <tr> <th></th> <th colspan="2" style="text-align: center;"><i>Yes/no answers only</i></th> </tr> <tr> <th></th> <th style="text-align: center;">Predicted</th> <th style="text-align: center;">Tested</th> </tr> </thead> <tbody> <tr> <td>Lamp across <math>L_1</math></td> <td></td> <td></td> </tr> <tr> <td>Lamp flashes?</td> <td></td> <td></td> </tr> <tr> <td>Lamp across switch</td> <td></td> <td></td> </tr> <tr> <td>Lamp flashes?</td> <td></td> <td></td> </tr> <tr> <td>Lamp across battery</td> <td></td> <td></td> </tr> <tr> <td>Lamp flashes?</td> <td></td> <td></td> </tr> </tbody> </table>			<i>Yes/no answers only</i>			Predicted	Tested	Lamp across $L_1$			Lamp flashes?			Lamp across switch			Lamp flashes?			Lamp across battery			Lamp flashes?		
	<i>Yes/no answers only</i>																								
	Predicted	Tested																							
Lamp across $L_1$																									
Lamp flashes?																									
Lamp across switch																									
Lamp flashes?																									
Lamp across battery																									
Lamp flashes?																									

---


Answer 21

The neon bulb will likely give you more reliable confirmation of your predictions than simulation software.

---

Notes 21

Students may either use ready-made inductors for this experiment (the larger the value, the more impressive the light flash!) or inductors of their own making (using old solenoid valve coils, or hand-wound coils around steel bolts). Power transformer primary windings also work well for this.

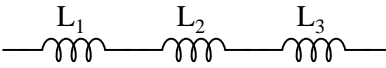Competency: <b>Series inductances</b>	Version:						
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="text-align: center; margin-top: 20px;">  </div>							
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <div style="text-align: center; margin-top: 20px;"> <math>L_1 =</math>                      <math>L_2 =</math>                      <math>L_3 =</math> </div>							
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; margin-top: 20px;"> <thead> <tr> <th style="width: 10%;"></th> <th style="width: 40%; text-align: center;">Predicted</th> <th style="width: 50%; text-align: center;">Measured</th> </tr> </thead> <tbody> <tr> <td style="vertical-align: middle;"><math>L_{\text{total}}</math></td> <td style="text-align: center; border: 1px solid black; height: 30px;"></td> <td style="text-align: center; border: 1px solid black; height: 30px;"></td> </tr> </tbody> </table>			Predicted	Measured	$L_{\text{total}}$		
	Predicted	Measured					
$L_{\text{total}}$							
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Analysis</div> <div style="text-align: center; margin-top: 20px;">             Equation used to calculate <math>L_{\text{total}}</math> :           </div> <div style="height: 150px; margin-top: 10px;"></div>							

---


Answer 22

Use circuit simulation software to verify your predicted and measured parameter values.

---

Notes 22

You will need an inductance meter in your lab to do this exercise. If you don't have one, you should get one right away!
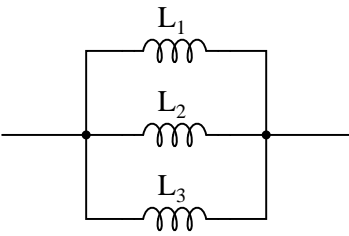
<b>Competency: Parallel inductances</b>		Version:
<b>Schematic</b>		
		
<b>Given conditions</b>		
$L_1 =$	$L_2 =$	$L_3 =$
<b>Parameters</b>		
$L_{\text{total}}$	<div>Predicted <input style="width: 80px; height: 25px;" type="text"/></div>	<div>Measured <input style="width: 80px; height: 25px;" type="text"/></div>
<b>Analysis</b>		
Equation used to calculate $L_{\text{total}}$ :		

---

Answer 23

Use circuit simulation software to verify your predicted and measured parameter values.

---

Notes 23

You will need an inductance meter in your lab to do this exercise. If you don't have one, you should get one right away!



Competency: <b>Series coupled inductors</b>		Version:						
<div> <div>Schematic</div> <div> </div> </div>								
<div> <div>Given conditions</div> <div> <math>L_1 =</math> <math>L_2 =</math> </div> </div>								
<div> <div>Parameters</div> <div> <table> <thead> <tr> <th></th> <th>Predicted</th> <th>Measured</th> </tr> </thead> <tbody> <tr> <td><math>L_{total}</math></td> <td><input type="text"/></td> <td><input type="text"/></td> </tr> </tbody> </table> </div> </div>				Predicted	Measured	$L_{total}$	<input type="text"/>	<input type="text"/>
	Predicted	Measured						
$L_{total}$	<input type="text"/>	<input type="text"/>						
<div> <div>Analysis</div> <div> <p>Equation used to calculate <math>L_{total}</math> :</p> </div> </div>								

---

Answer 24


Use circuit simulation software to verify your predicted and measured parameter values.

You might be surprised to find that  $L_{total} \neq L_1 + L_2$ . This is due to the *mutual inductance* between inductors  $L_1$  and  $L_2$ .

---


Notes 24

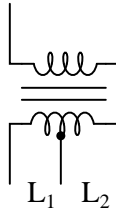In case students don't have access to a pair of inductors on a common core, they may either make their own by winding wire around a long ferromagnetic core, or use a center-tapped inductor (or transformer winding). The latter solution is probably the easiest:



Inexpensive audio output transformers (with center-tapped  $1000\ \Omega$  primary windings) work very well for this. Your students' parts kits should contain at least one of these transformers anyway if they are to do audio coupling experiments later.

You will need an inductance meter in your lab to do this exercise. If you don't have one, you should get one right away!
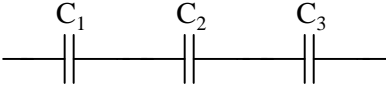
<b>Competency: Series capacitances</b>		Version:
<b>Schematic</b>		
		
<b>Given conditions</b>		
$C_1 =$	$C_2 =$	$C_3 =$
<b>Parameters</b>		
$C_{\text{total}}$	<div style="display: inline-block; text-align: center;">Predicted <div style="border: 1px solid black; width: 100px; height: 30px; margin: 5px auto;"></div></div>	<div style="display: inline-block; text-align: center;">Measured <div style="border: 1px solid black; width: 100px; height: 30px; margin: 5px auto;"></div></div>
<b>Analysis</b>		
Equation used to calculate $C_{\text{total}}$ :		

---


Answer 25

Use circuit simulation software to verify your predicted and measured parameter values.

---

Notes 25

Many modern digital multimeters come equipped with capacitance measurement built-in. If your students do not have these meters, you will either need to provide one for them to use, or provide an LCR meter. If you don't have either one of these instruments, you should get one right away!
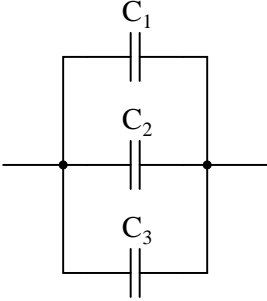
<b>Competency: Parallel capacitances</b>		Version:
<b>Schematic</b>		
		
<b>Given conditions</b>		
$C_1 =$	$C_2 =$	$C_3 =$
<b>Parameters</b>		
$C_{\text{total}}$	Predicted <input style="width: 80px; height: 25px;" type="text"/>	Measured <input style="width: 80px; height: 25px;" type="text"/>
<b>Analysis</b>		
Equation used to calculate $C_{\text{total}}$ :		

---

Answer 26

Use circuit simulation software to verify your predicted and measured parameter values.

---

Notes 26

Many modern digital multimeters come equipped with capacitance measurement built-in. If your students do not have these meters, you will either need to provide one for them to use, or provide an LCR meter. If you don't have either one of these instruments, you should get one right away!

Competency: <b>RC discharge circuit</b>		Version:												
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="text-align: center; padding: 10px;"> </div>														
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <table style="width: 100%; margin-top: 10px;"> <tr> <td style="text-align: center; width: 33%;"><math>V_{\text{supply}} =</math></td> <td style="text-align: center; width: 33%;"><math>C_1 =</math></td> <td style="text-align: center; width: 33%;"><math>R_1 =</math></td> </tr> <tr> <td style="text-align: center;"><math>t_1 =</math></td> <td style="text-align: center;"><math>t_2 =</math></td> <td style="text-align: center;"><math>t_3 =</math></td> </tr> </table>			$V_{\text{supply}} =$	$C_1 =$	$R_1 =$	$t_1 =$	$t_2 =$	$t_3 =$						
$V_{\text{supply}} =$	$C_1 =$	$R_1 =$												
$t_1 =$	$t_2 =$	$t_3 =$												
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; margin-top: 10px;"> <thead> <tr> <th></th> <th style="text-align: center;">Predicted</th> <th style="text-align: center;">Measured</th> </tr> </thead> <tbody> <tr> <td style="text-align: right;"><math>V_{t1}</math></td> <td style="border: 1px solid black; width: 100px; height: 25px;"></td> <td style="border: 1px solid black; width: 100px; height: 25px;"></td> </tr> <tr> <td style="text-align: right;"><math>V_{t2}</math></td> <td style="border: 1px solid black; width: 100px; height: 25px;"></td> <td style="border: 1px solid black; width: 100px; height: 25px;"></td> </tr> <tr> <td style="text-align: right;"><math>V_{t3}</math></td> <td style="border: 1px solid black; width: 100px; height: 25px;"></td> <td style="border: 1px solid black; width: 100px; height: 25px;"></td> </tr> </tbody> </table>				Predicted	Measured	$V_{t1}$			$V_{t2}$			$V_{t3}$		
	Predicted	Measured												
$V_{t1}$														
$V_{t2}$														
$V_{t3}$														
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Calculations</div> <div style="height: 150px; border: 1px solid black; margin-top: 5px;"></div>														

---

Answer 27

Use circuit simulation software to verify your predicted and measured parameter values.

---

Notes 27

I recommend choosing resistor and capacitor values that yield time constants in the range that may be accurately tracked with a stopwatch. I also recommend using resistor values significantly less than the voltmeter's input impedance, so that voltmeter loading does not significantly contribute to the decay rate.

Good time values to use ( $t_1$ ,  $t_2$ ,  $t_3$ ) would be in the range of 5, 10, and 15 seconds, respectively.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.



Competency: <b>Time-delay relay</b>		Version:	
Schematic			
Given conditions			
$V_{\text{supply}} =$	$C_1 =$	$R_{\text{coil}} =$	$V_{\text{dropout}} =$
Parameters			
$t_{\text{delay}}$	<div style="display: inline-block; border: 1px solid black; padding: 5px;">Predicted</div>	<div style="display: inline-block; border: 1px solid black; padding: 5px;">Measured</div>	
Calculations			

file 01647

---

Answer 28

Use circuit simulation software to verify your predicted and measured parameter values.

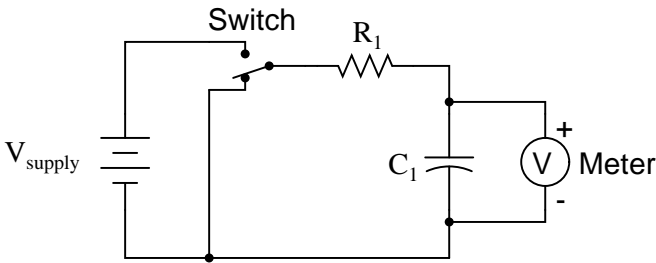
---

Notes 28

Two very important "given" parameters are the relay coil resistance ( $R_{coil}$ ) and the relay dropout voltage ( $V_{dropout}$ ). These are best determined experimentally.

Many students fail to grasp the purpose of this exercise until it is explained. The idea here is to predict *when* the relay will "drop out" after the switch is opened. This means solving for  $t$  in the time-constant (decay) equation given the initial capacitor voltage, time constant ( $\tau$ ), and the capacitor voltage at time  $t$ . Because this involves the use of logarithms, students may be perplexed until given assistance.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: <b>RC charge/discharge circuit</b>		Version:																								
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="text-align: center; margin-top: 20px;">  </div>																										
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <div style="display: flex; justify-content: space-around; margin-top: 10px;"> <div style="text-align: center;"><math>V_{\text{supply}} =</math></div> <div style="text-align: center;"><math>C_1 =</math></div> <div style="text-align: center;"><math>R_1 =</math></div> </div> <div style="display: flex; justify-content: space-around; margin-top: 10px;"> <div style="text-align: center;"><math>t_1 =</math></div> <div style="text-align: center;"><math>t_2 =</math></div> <div style="text-align: center;"><math>t_3 =</math></div> </div>																										
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <div style="display: flex; justify-content: space-between; margin-top: 10px;"> <div style="width: 45%;"> <p style="text-align: center; margin-bottom: 10px;"><i>Charging from 0 volts</i></p> <table style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th></th> <th style="text-align: center; padding: 5px;">Predicted</th> <th style="text-align: center; padding: 5px;">Measured</th> </tr> </thead> <tbody> <tr> <td style="text-align: right; padding-right: 10px;"><math>V_{t1}</math></td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> </tr> <tr> <td style="text-align: right; padding-right: 10px;"><math>V_{t2}</math></td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> </tr> <tr> <td style="text-align: right; padding-right: 10px;"><math>V_{t3}</math></td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> </tr> </tbody> </table> </div> <div style="width: 45%;"> <p style="text-align: center; margin-bottom: 10px;"><i>Discharging from <math>V_{\text{supply}}</math></i></p> <table style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th></th> <th style="text-align: center; padding: 5px;">Predicted</th> <th style="text-align: center; padding: 5px;">Measured</th> </tr> </thead> <tbody> <tr> <td style="text-align: right; padding-right: 10px;"><math>V_{t1}</math></td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> </tr> <tr> <td style="text-align: right; padding-right: 10px;"><math>V_{t2}</math></td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> </tr> <tr> <td style="text-align: right; padding-right: 10px;"><math>V_{t3}</math></td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> </tr> </tbody> </table> </div> </div>				Predicted	Measured	$V_{t1}$			$V_{t2}$			$V_{t3}$				Predicted	Measured	$V_{t1}$			$V_{t2}$			$V_{t3}$		
	Predicted	Measured																								
$V_{t1}$																										
$V_{t2}$																										
$V_{t3}$																										
	Predicted	Measured																								
$V_{t1}$																										
$V_{t2}$																										
$V_{t3}$																										
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Calculations</div> <div style="height: 150px; border: 1px solid black; margin-top: 10px;"></div>																										

---

Answer 29

Use circuit simulation software to verify your predicted and measured parameter values.

---

Notes 29

I recommend choosing resistor and capacitor values that yield time constants in the range that may be accurately tracked with a stopwatch. I also recommend using resistor values significantly less than the voltmeter's input impedance, so that voltmeter loading does not significantly contribute to the decay rate.

Good time values to use ( $t_1$ ,  $t_2$ ,  $t_3$ ) would be in the range of 5, 10, and 15 seconds, respectively.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: <b>Rate of change indicator circuit</b>		Version:
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Schematic</div>		
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Given conditions</div>		
$V_{\text{supply}} =$	$R_{\text{pot}} =$	$C_1 =$
$R_1 =$		
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Parameters</div>		
<i>Qualitative answers only</i>		
	Predicted	Measured
$V_{\text{out}}$ Wiper up, slowly	<input style="width: 80px; height: 25px;" type="text"/>	<input style="width: 80px; height: 25px;" type="text"/>
$V_{\text{out}}$ Wiper down, slowly	<input style="width: 80px; height: 25px;" type="text"/>	<input style="width: 80px; height: 25px;" type="text"/>
$V_{\text{out}}$ Wiper up, rapidly	<input style="width: 80px; height: 25px;" type="text"/>	<input style="width: 80px; height: 25px;" type="text"/>
$V_{\text{out}}$ Wiper down, rapidly	<input style="width: 80px; height: 25px;" type="text"/>	<input style="width: 80px; height: 25px;" type="text"/>
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Analysis</div>		
Explain <i>why</i> the output voltage polarity is related to the wiper motion as measured.		

---

Answer 30

Use circuit simulation software to verify your predicted and measured parameter values.

---

Notes 30

I recommend a supply voltage of 12 volts, a potentiometer value of  $10\text{ k}\Omega$ , a capacitor value of  $0.1\text{ }\mu\text{F}$ , and a loading resistor ( $R_1$ ) of  $1\text{ M}\Omega$ . Use a DMM so as to not load the circuit any more than necessary. If you wish to choose different capacitor/resistor values, I strongly suggest choosing them such that the time constant ( $\tau$ ) of the circuit significantly faster than 1 second.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

(Template)

Competency:	Version:						
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Schematic</div>							
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Given conditions</div>							
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Parameters</div>							
<table style="margin-left: auto; margin-right: auto;"> <thead> <tr> <th style="text-align: center; padding: 5px;">Predicted</th> <th style="text-align: center; padding: 5px;">Measured</th> </tr> </thead> <tbody> <tr> <td style="border: 1px solid black; width: 80px; height: 25px;"></td> <td style="border: 1px solid black; width: 80px; height: 25px;"></td> </tr> <tr> <td style="border: 1px solid black; width: 80px; height: 25px;"></td> <td style="border: 1px solid black; width: 80px; height: 25px;"></td> </tr> </tbody> </table>		Predicted	Measured				
Predicted	Measured						

file 01602

---

Answer 31

Here, you would indicate where or how to obtain answers for the requested parameters, but not actually give the figures. My stock answer here is “use circuit simulation software” (Spice, Multisim, etc.).

---

Notes 31

Any relevant notes for the assessment activity go here.