

## Performance-based assessments for digital circuit competencies

This worksheet and all related files are licensed under the Creative Commons Attribution License, version 1.0. To view a copy of this license, visit <http://creativecommons.org/licenses/by/1.0/>, or send a letter to Creative Commons, 559 Nathan Abbott Way, Stanford, California 94305, USA. The terms and conditions of this license allow for free copying, distribution, and/or modification of all licensed works by the general public.

---

The purpose of these assessments is for instructors to accurately measure the learning of their electronics students, in a way that melds theoretical knowledge with hands-on application. In each assessment, students are asked to predict the behavior of a circuit from a schematic diagram and component values, then they build that circuit and measure its real behavior. If the behavior matches the predictions, the student then simulates the circuit on computer and presents the three sets of values to the instructor. If not, then the student then must correct the error(s) and once again compare measurements to predictions. Grades are based on the number of attempts required before all predictions match their respective measurements.

You will notice that no component values are given in this worksheet. The *instructor* chooses component values suitable for the students' parts collections, and ideally chooses different values for each student so that no two students are analyzing and building the exact same circuit. These component values may be hand-written on the assessment sheet, printed on a separate page, or incorporated into the document by editing the graphic image.

This is the procedure I envision for managing such assessments:

1. The instructor hands out individualized assessment sheets to each student.
2. Each student predicts their circuit's behavior at their desks using pencil, paper, and calculator (if appropriate).
3. Each student builds their circuit at their desk, under such conditions that it is impossible for them to verify their predictions using test equipment. Usually this will mean the use of a multimeter only (for measuring component values), but in some cases even the use of a multimeter would not be appropriate.
4. When ready, each student brings their predictions and completed circuit up to the instructor's desk, where any necessary test equipment is already set up to operate and test the circuit. There, the student sets up their circuit and takes measurements to compare with predictions.
5. If any measurement fails to match its corresponding prediction, the student goes back to their own desk with their circuit and their predictions in hand. There, the student tries to figure out where the error is and how to correct it.
6. Students repeat these steps as many times as necessary to achieve correlation between all predictions and measurements. The instructor's task is to count the number of attempts necessary to achieve this, which will become the basis for a percentage grade.
7. (OPTIONAL) As a final verification, each student simulates the same circuit on computer, using circuit simulation software (Spice, Multisim, etc.) and presenting the results to the instructor as a final pass/fail check.

These assessments more closely mimic real-world work conditions than traditional written exams:

- Students cannot pass such assessments only knowing circuit theory or only having hands-on construction and testing skills – they must be proficient at both.
- Students do not receive the “authoritative answers” from the instructor. Rather, they learn to validate their answers through real circuit measurements.
- Just as on the job, the work isn't complete until *all errors* are corrected.
- Students must recognize and correct their own errors, rather than having someone else do it for them.
- Students must be fully prepared on exam days, bringing not only their calculator and notes, but also their tools, breadboard, and circuit components.

Instructors may elect to reveal the assessments before test day, and even use them as preparatory labwork and/or discussion questions. Remember that there is absolutely nothing wrong with “teaching to

the test” *so long as the test is valid*. Normally, it is bad to reveal test material in detail prior to test day, lest students merely memorize responses in advance. With performance-based assessments, however, there is no way to pass without truly understanding the subject(s).

Question 1

Competency: <b>Logic probe circuit</b>		Version:
Schematic		
Given conditions		
$V_{High} =$	$R_{pot1} = R_{pot2} =$	
$V_{Low} =$	$R_1 = R_2 =$	
Parameters		
	Predicted	Tested
LED status		
	$V_{probe} \geq V_{High}$	
LED status		
	$V_{probe} \leq V_{Low}$	
Fault analysis		
Suppose component <span style="border: 1px solid black; display: inline-block; width: 50px; height: 20px; vertical-align: middle;"></span> fails <div style="display: inline-block; vertical-align: middle; margin-left: 10px;"> <input type="checkbox"/> open    <input type="checkbox"/> other _____  <input type="checkbox"/> shorted         </div>		
<i>What will happen in the circuit?</i>		

file 02851

---

Answer 1

Use circuit simulation software to verify your predicted and measured parameter values.

---

Notes 1

I recommend the use of the LM339 comparator for this circuit.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Question 2

Competency: <b>OR gate, diode-resistor logic</b>		Version:																														
Schematic																																
Given conditions																																
$V_{DD} =$	$R_{pulldown} =$																															
Truth table																																
<div style="display: flex; justify-content: space-around;"> <div style="text-align: center;"> <p>Predicted</p> <table border="1" style="margin: auto;"> <thead> <tr> <th>A</th> <th>B</th> <th>Output</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td></tr> <tr><td>0</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td></td></tr> <tr><td>1</td><td>1</td><td></td></tr> </tbody> </table> </div> <div style="text-align: center;"> <p>Actual</p> <table border="1" style="margin: auto;"> <thead> <tr> <th>A</th> <th>B</th> <th>Output</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td></tr> <tr><td>0</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td></td></tr> <tr><td>1</td><td>1</td><td></td></tr> </tbody> </table> </div> </div>			A	B	Output	0	0		0	1		1	0		1	1		A	B	Output	0	0		0	1		1	0		1	1	
A	B	Output																														
0	0																															
0	1																															
1	0																															
1	1																															
A	B	Output																														
0	0																															
0	1																															
1	0																															
1	1																															
Fault analysis																																
<p>Suppose component <span style="border: 1px solid black; display: inline-block; width: 50px; height: 20px; vertical-align: middle;"></span> fails <span style="margin-left: 20px;"><input type="checkbox"/> open</span> <span style="margin-left: 20px;"><input type="checkbox"/> other _____</span></p> <p style="margin-left: 100px;"><span style="border: 1px solid black; display: inline-block; width: 20px; height: 20px; vertical-align: middle;"></span> shorted</p> <p><i>What will happen in the circuit?</i></p>																																

file 02787

---

#### Answer 2

Use circuit simulation software to verify your predicted and actual truth tables.

---

#### Notes 2

The choice of diodes is not critical in a circuit where the inputs come from manually actuated switches. Neither is the choice of resistor sizes (10 k $\Omega$ ) works just fine, especially when the only thing loading the output is the student's logic probe or voltmeter.

Question 3

Competency: <b>AND gate, diode-resistor logic</b>	Version:																														
Schematic																															
Given conditions																															
$V_{DD} =$	$R_{pullup} =$																														
Truth table																															
Predicted	Actual																														
<table border="1" style="margin: auto;"> <thead> <tr> <th>A</th> <th>B</th> <th>Output</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td></tr> <tr><td>0</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td></td></tr> <tr><td>1</td><td>1</td><td></td></tr> </tbody> </table>	A	B	Output	0	0		0	1		1	0		1	1		<table border="1" style="margin: auto;"> <thead> <tr> <th>A</th> <th>B</th> <th>Output</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td></tr> <tr><td>0</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td></td></tr> <tr><td>1</td><td>1</td><td></td></tr> </tbody> </table>	A	B	Output	0	0		0	1		1	0		1	1	
A	B	Output																													
0	0																														
0	1																														
1	0																														
1	1																														
A	B	Output																													
0	0																														
0	1																														
1	0																														
1	1																														
Fault analysis																															
Suppose component <span style="border: 1px solid black; display: inline-block; width: 50px; height: 20px; vertical-align: middle;"></span> fails <div style="display: inline-block; vertical-align: middle; margin-left: 10px;"> <input type="checkbox"/> open    <input type="checkbox"/> other _____  <input type="checkbox"/> shorted         </div> <p><i>What will happen in the circuit?</i></p>																															

file 02788

---

### Answer 3

Use circuit simulation software to verify your predicted and actual truth tables.

---

### Notes 3

It should be noted that the input states in this circuit are defined by the voltage levels, not by the contact status. In other words, a closed contact equals a "low" (0) logic state.

The choice of diodes is not critical in a circuit where the inputs come from manually actuated switches. Neither is the choice of resistor sizes (10 k $\Omega$ ) works just fine, especially when the only thing loading the output is the student's logic probe or voltmeter.



Question 4

Competency: <b>OR gate, simple BJT logic</b>		Version:																														
Schematic																																
Given conditions																																
$V_{CC} =$	$R_{pulldown} =$																															
Truth table																																
<div style="display: flex; justify-content: space-around;"> <div style="text-align: center;"> <p>Predicted</p> <table border="1" style="margin: auto;"> <thead> <tr> <th>A</th> <th>B</th> <th>Output</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td></tr> <tr><td>0</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td></td></tr> <tr><td>1</td><td>1</td><td></td></tr> </tbody> </table> </div> <div style="text-align: center;"> <p>Actual</p> <table border="1" style="margin: auto;"> <thead> <tr> <th>A</th> <th>B</th> <th>Output</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td></tr> <tr><td>0</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td></td></tr> <tr><td>1</td><td>1</td><td></td></tr> </tbody> </table> </div> </div>			A	B	Output	0	0		0	1		1	0		1	1		A	B	Output	0	0		0	1		1	0		1	1	
A	B	Output																														
0	0																															
0	1																															
1	0																															
1	1																															
A	B	Output																														
0	0																															
0	1																															
1	0																															
1	1																															
Fault analysis																																
<p>Suppose component <span style="border: 1px solid black; display: inline-block; width: 50px; height: 20px; vertical-align: middle;"></span> fails</p> <div style="display: flex; align-items: center; margin-top: 5px;"> <div style="margin-right: 20px;"> <input type="checkbox"/> open  <input type="checkbox"/> shorted         </div> <div> <input type="checkbox"/> other _____         </div> </div> <p><i>What will happen in the circuit?</i></p>																																

file 02794

---

Answer 4

Use circuit simulation software to verify your predicted and actual truth tables.

---

Notes 4

Nothing special to note here!

Competency: <b>AND gate, simple BJT logic</b>		Version:																														
<b>Schematic</b>																																
<b>Given conditions</b>	$V_{EE} =$ $R_{pullup} =$																															
<b>Truth table</b>	<div style="display: flex; justify-content: space-around;"> <div style="text-align: center;"> <p><b>Predicted</b></p> <table border="1" style="margin: auto;"> <thead> <tr><th>A</th><th>B</th><th>Output</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td></tr> <tr><td>0</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td></td></tr> <tr><td>1</td><td>1</td><td></td></tr> </tbody> </table> </div> <div style="text-align: center;"> <p><b>Actual</b></p> <table border="1" style="margin: auto;"> <thead> <tr><th>A</th><th>B</th><th>Output</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td></tr> <tr><td>0</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td></td></tr> <tr><td>1</td><td>1</td><td></td></tr> </tbody> </table> </div> </div>		A	B	Output	0	0		0	1		1	0		1	1		A	B	Output	0	0		0	1		1	0		1	1	
A	B	Output																														
0	0																															
0	1																															
1	0																															
1	1																															
A	B	Output																														
0	0																															
0	1																															
1	0																															
1	1																															
<b>Fault analysis</b>	<p>Suppose component <span style="border: 1px solid black; display: inline-block; width: 50px; height: 20px; vertical-align: middle;"></span> fails    <input type="checkbox"/> open    <input type="checkbox"/> other _____</p> <p style="margin-left: 100px;"><input type="checkbox"/> shorted</p> <p><i>What will happen in the circuit?</i></p>   																															

---

Answer 5

Use circuit simulation software to verify your predicted and actual truth tables.

---

Notes 5

It needs to be understood that this is an AND gate only if you consider the "0" and "1" states as defined by voltage levels with respect to ground, and not by switch actuation. Many students assume an actuated (pushed) switch is a "1" input and a de-actuated (unpushed) switch is a "0" input. Not necessarily so! In this circuit, the switches are connecting inputs to *ground*. This means a closed (actuated) switch provides a low (0) input state, while an open (unactuated) switch provides a high (1) input state.

Question 6

Competency: <b>OR gate, relay logic</b>	Version:																														
Ladder logic diagram																															
Schematic																															
Truth table																															
Predicted	Actual																														
<table border="1" style="margin: auto;"> <thead> <tr> <th>A</th> <th>B</th> <th>Output</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td></tr> <tr><td>0</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td></td></tr> <tr><td>1</td><td>1</td><td></td></tr> </tbody> </table>	A	B	Output	0	0		0	1		1	0		1	1		<table border="1" style="margin: auto;"> <thead> <tr> <th>A</th> <th>B</th> <th>Output</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td></tr> <tr><td>0</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td></td></tr> <tr><td>1</td><td>1</td><td></td></tr> </tbody> </table>	A	B	Output	0	0		0	1		1	0		1	1	
A	B	Output																													
0	0																														
0	1																														
1	0																														
1	1																														
A	B	Output																													
0	0																														
0	1																														
1	0																														
1	1																														

file 02792

---

#### Answer 6

Use circuit simulation software to verify your predicted and actual truth tables.

---

#### Notes 6

The transition from ladder logic diagram to actual relay wiring is a confusing one for many students. This is what I consider to be the most significant learning objective of this exercise: figuring out how to build the circuit, not necessarily understanding the logical function of it.

Question 7

Competency: <b>AND gate, relay logic</b>	Version:																														
Ladder logic diagram																															
Schematic																															
Truth table																															
<b>Predicted</b> <table border="1" style="margin: auto; border-collapse: collapse;"> <thead> <tr> <th>A</th> <th>B</th> <th>Output</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td></tr> <tr><td>0</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td></td></tr> <tr><td>1</td><td>1</td><td></td></tr> </tbody> </table>	A	B	Output	0	0		0	1		1	0		1	1		<b>Actual</b> <table border="1" style="margin: auto; border-collapse: collapse;"> <thead> <tr> <th>A</th> <th>B</th> <th>Output</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td></tr> <tr><td>0</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td></td></tr> <tr><td>1</td><td>1</td><td></td></tr> </tbody> </table>	A	B	Output	0	0		0	1		1	0		1	1	
A	B	Output																													
0	0																														
0	1																														
1	0																														
1	1																														
A	B	Output																													
0	0																														
0	1																														
1	0																														
1	1																														

[file 02791](#)

---

#### Answer 7

Use circuit simulation software to verify your predicted and actual truth tables.

---

#### Notes 7

The transition from ladder logic diagram to actual relay wiring is a confusing one for many students. This is what I consider to be the most significant learning objective of this exercise: figuring out how to build the circuit, not necessarily understanding the logical function of it.



<b>Competency: IC logic gate usage</b>	<b>Version:</b>																														
<div style="border: 1px solid black; padding: 2px; margin-bottom: 5px;"><b>Description</b></div> <p style="text-align: center;">Connect one of the IC's two-input gates to the switches and to the LED, then prove your prediction for that gate's truth table.</p>																															
<div style="border: 1px solid black; padding: 2px; margin-bottom: 5px;"><b>Diagram</b></div>																															
<div style="border: 1px solid black; padding: 2px; margin-bottom: 5px;"><b>Given conditions</b></div> <p style="text-align: center;"><i>(instructor chooses IC part number)</i></p> <p style="text-align: center;"> <math>V_{DD} =</math>      <math>R_{pullup} =</math>      <math>R_{limit} =</math>      <math>U_1 =</math> </p>																															
<div style="border: 1px solid black; padding: 2px; margin-bottom: 5px;"><b>Truth table</b></div> <div style="display: flex; justify-content: space-around; align-items: flex-start;"> <div style="text-align: center;"> <p>Predicted</p> <table border="1" style="margin: auto;"> <thead> <tr> <th>A</th> <th>B</th> <th>Output</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td></tr> <tr><td>0</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td></td></tr> <tr><td>1</td><td>1</td><td></td></tr> </tbody> </table> </div> <div style="text-align: center;"> <p>Actual</p> <table border="1" style="margin: auto;"> <thead> <tr> <th>A</th> <th>B</th> <th>Output</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td></tr> <tr><td>0</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td></td></tr> <tr><td>1</td><td>1</td><td></td></tr> </tbody> </table> </div> </div>		A	B	Output	0	0		0	1		1	0		1	1		A	B	Output	0	0		0	1		1	0		1	1	
A	B	Output																													
0	0																														
0	1																														
1	0																														
1	1																														
A	B	Output																													
0	0																														
0	1																														
1	0																														
1	1																														

---

#### Answer 8

Use circuit simulation software to verify your predicted and actual truth tables.

---

#### Notes 8

The purpose of this exercise is for students to research what type of IC this is (from the given part number for  $U_1$ ), its pinout, and then predict and prove its operation using truth tables to document the results. You, as the instructor, may select any 14-pin CMOS or TTL logic IC that you wish. Students are to draw the logic gate symbol within the rectangle of  $U_1$ , then connect that symbol to the input switches and output LED.

It needs to be understood that the "0" and "1" states are defined by voltage levels with respect to ground, and not by switch actuation. Many students assume an actuated (pushed) switch is a "1" input and a de-actuated (unpushed) switch is a "0" input. Not necessarily so! In this circuit, the switches are connecting inputs to *ground*. This means a closed (actuated) switch provides a low (0) input state, while an open (unactuated) switch provides a high (1) input state.

Competency: <b>Gate-relay interposing</b>		Version:																														
<div style="border: 1px solid black; padding: 2px; display: inline-block; width: 100px;">Schematic</div>																																
<div style="border: 1px solid black; padding: 2px; display: inline-block; width: 100px;">Given conditions</div>																																
$+V =$	$R_1 = R_2 =$	$R_3 =$																														
<div style="border: 1px solid black; padding: 2px; display: inline-block; width: 100px;">Truth table</div>																																
<div style="display: flex; justify-content: space-around;"> <div style="text-align: center;"> <p>Predicted</p> <table border="1" style="margin: auto; border-collapse: collapse;"> <thead> <tr> <th>A</th> <th>B</th> <th>Output</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td></tr> <tr><td>0</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td></td></tr> <tr><td>1</td><td>1</td><td></td></tr> </tbody> </table> </div> <div style="text-align: center;"> <p>Actual</p> <table border="1" style="margin: auto; border-collapse: collapse;"> <thead> <tr> <th>A</th> <th>B</th> <th>Output</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td></tr> <tr><td>0</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td></td></tr> <tr><td>1</td><td>1</td><td></td></tr> </tbody> </table> </div> </div>			A	B	Output	0	0		0	1		1	0		1	1		A	B	Output	0	0		0	1		1	0		1	1	
A	B	Output																														
0	0																															
0	1																															
1	0																															
1	1																															
A	B	Output																														
0	0																															
0	1																															
1	0																															
1	1																															
<div style="border: 1px solid black; padding: 2px; display: inline-block; width: 100px;">Fault analysis</div>																																
<p>Suppose component <span style="border: 1px solid black; display: inline-block; width: 50px; height: 20px; vertical-align: middle;"></span> fails</p> <div style="display: flex; justify-content: flex-end; align-items: center; gap: 10px;"> <div> <input type="checkbox"/> open  <input type="checkbox"/> shorted         </div> <div> <input type="checkbox"/> other _____         </div> </div> <p><i>What will happen in the circuit?</i></p>																																

---

#### Answer 9

Use circuit simulation software to verify your predicted and actual truth tables.


---

#### Notes 9

Something omitted from too many basic digital electronics texts is a thorough discussion on interfacing IC logic gates with high-power devices, usually using relays. This is a very important subject, however, because many devices we wish to control with digital logic circuits are too power-hungry to directly drive with the logic gate outputs! Here, students get the opportunity to experiment with how to make a logic gate (CMOS, preferably) drive an electric motor.

One component value you may wish to have your students size themselves is resistor  $R_3$ , being the base current limiting resistor for transistor  $Q_1$ . It must be sized such that the transistor is saturated with the gate output in the HIGH state, yet not allowing so much base current that the transistor becomes damaged. Figuring out an appropriate size for this resistor is a very practical exercise, forcing students to review transistor theory (calculations with  $\beta$ ) as well as consider characteristics of the load.

It may be advisable (especially if the logic gate is TTL and requires a precise 5.0 volt power supply) to have a separate source of power for the electric motor.

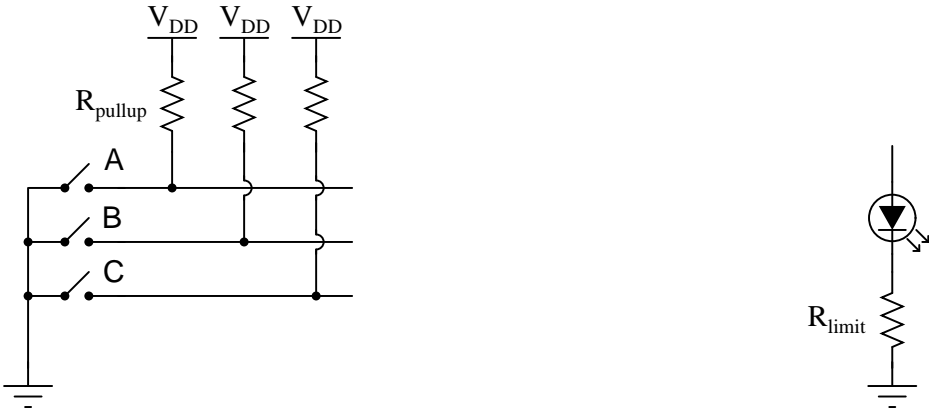Competency: <b>Combinational logic circuit</b>	Version:																																																																								
<div style="border: 1px solid black; padding: 2px; margin-bottom: 5px;">Schematic</div> <div style="display: flex; justify-content: space-around; align-items: center;">  </div>																																																																									
<div style="border: 1px solid black; padding: 2px; margin-bottom: 5px;">Given conditions</div> <div style="display: flex; justify-content: space-around; align-items: center; margin-top: 10px;"> <div><math>V_{DD} =</math></div> <div><math>R_{pullup} =</math></div> <div><math>R_{limit} =</math></div> </div>																																																																									
<div style="border: 1px solid black; padding: 2px; margin-bottom: 5px;">Truth table</div> <div style="display: flex; justify-content: space-around; align-items: flex-start; margin-top: 10px;"> <div style="text-align: center;"> <p>Predicted</p> <table border="1" style="border-collapse: collapse; text-align: center;"> <thead> <tr> <th>A</th><th>B</th><th>C</th><th>Output</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td></td></tr> <tr><td>0</td><td>0</td><td>1</td><td></td></tr> <tr><td>0</td><td>1</td><td>0</td><td></td></tr> <tr><td>0</td><td>1</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td>0</td><td></td></tr> <tr><td>1</td><td>0</td><td>1</td><td></td></tr> <tr><td>1</td><td>1</td><td>0</td><td></td></tr> <tr><td>1</td><td>1</td><td>1</td><td></td></tr> </tbody> </table> </div> <div style="text-align: center;"> <p>Actual</p> <table border="1" style="border-collapse: collapse; text-align: center;"> <thead> <tr> <th>A</th><th>B</th><th>C</th><th>Output</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td></td></tr> <tr><td>0</td><td>0</td><td>1</td><td></td></tr> <tr><td>0</td><td>1</td><td>0</td><td></td></tr> <tr><td>0</td><td>1</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td>0</td><td></td></tr> <tr><td>1</td><td>0</td><td>1</td><td></td></tr> <tr><td>1</td><td>1</td><td>0</td><td></td></tr> <tr><td>1</td><td>1</td><td>1</td><td></td></tr> </tbody> </table> </div> </div>		A	B	C	Output	0	0	0		0	0	1		0	1	0		0	1	1		1	0	0		1	0	1		1	1	0		1	1	1		A	B	C	Output	0	0	0		0	0	1		0	1	0		0	1	1		1	0	0		1	0	1		1	1	0		1	1	1	
A	B	C	Output																																																																						
0	0	0																																																																							
0	0	1																																																																							
0	1	0																																																																							
0	1	1																																																																							
1	0	0																																																																							
1	0	1																																																																							
1	1	0																																																																							
1	1	1																																																																							
A	B	C	Output																																																																						
0	0	0																																																																							
0	0	1																																																																							
0	1	0																																																																							
0	1	1																																																																							
1	0	0																																																																							
1	0	1																																																																							
1	1	0																																																																							
1	1	1																																																																							

---

Answer 10

Use circuit simulation software to verify your predicted and actual truth tables.

---

Notes 10

It should be noted that the input states in this circuit are defined by the voltage levels, not by the contact status. In other words, a closed contact equals a "low" (0) logic state.

I strongly recommend having students build their logic circuits with CMOS chips rather than TTL, because of the less stringent power supply requirements of CMOS. I also recommend drawing a combinational circuit using four gates, because this is the common number of two-input gates found on 14-pin DIP logic chips.

Question 11

Competency: <b>Binary to Gray code converter</b>		Version:																																																																								
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div>																																																																										
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <div style="display: flex; justify-content: space-around; align-items: flex-start; padding-top: 10px;"> <div style="text-align: center;"><math>V_{DD} =</math></div> <div style="text-align: center;"><math>R_{pulldown} =</math></div> <div style="text-align: center;"><math>R_{limit} =</math></div> </div>																																																																										
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Truth table</div> <table style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th colspan="2" style="text-align: center; padding: 5px;">Predicted</th> <th colspan="2" style="text-align: center; padding: 5px;">Actual</th> </tr> <tr> <th style="text-align: center; padding: 5px;"><i>Binary</i></th> <th style="text-align: center; padding: 5px;"><i>Gray</i></th> <th style="text-align: center; padding: 5px;"><i>Binary</i></th> <th style="text-align: center; padding: 5px;"><i>Gray</i></th> </tr> </thead> <tbody> <tr><td>0 0 0 0</td><td></td><td>0 0 0 0</td><td></td></tr> <tr><td>0 0 0 1</td><td></td><td>0 0 0 1</td><td></td></tr> <tr><td>0 0 1 0</td><td></td><td>0 0 1 0</td><td></td></tr> <tr><td>0 0 1 1</td><td></td><td>0 0 1 1</td><td></td></tr> <tr><td>0 1 0 0</td><td></td><td>0 1 0 0</td><td></td></tr> <tr><td>0 1 0 1</td><td></td><td>0 1 0 1</td><td></td></tr> <tr><td>0 1 1 0</td><td></td><td>0 1 1 0</td><td></td></tr> <tr><td>0 1 1 1</td><td></td><td>0 1 1 1</td><td></td></tr> <tr><td>1 0 0 0</td><td></td><td>1 0 0 0</td><td></td></tr> <tr><td>1 0 0 1</td><td></td><td>1 0 0 1</td><td></td></tr> <tr><td>1 0 1 0</td><td></td><td>1 0 1 0</td><td></td></tr> <tr><td>1 0 1 1</td><td></td><td>1 0 1 1</td><td></td></tr> <tr><td>1 1 0 0</td><td></td><td>1 1 0 0</td><td></td></tr> <tr><td>1 1 0 1</td><td></td><td>1 1 0 1</td><td></td></tr> <tr><td>1 1 1 0</td><td></td><td>1 1 1 0</td><td></td></tr> <tr><td>1 1 1 1</td><td></td><td>1 1 1 1</td><td></td></tr> </tbody> </table>			Predicted		Actual		<i>Binary</i>	<i>Gray</i>	<i>Binary</i>	<i>Gray</i>	0 0 0 0		0 0 0 0		0 0 0 1		0 0 0 1		0 0 1 0		0 0 1 0		0 0 1 1		0 0 1 1		0 1 0 0		0 1 0 0		0 1 0 1		0 1 0 1		0 1 1 0		0 1 1 0		0 1 1 1		0 1 1 1		1 0 0 0		1 0 0 0		1 0 0 1		1 0 0 1		1 0 1 0		1 0 1 0		1 0 1 1		1 0 1 1		1 1 0 0		1 1 0 0		1 1 0 1		1 1 0 1		1 1 1 0		1 1 1 0		1 1 1 1		1 1 1 1	
Predicted		Actual																																																																								
<i>Binary</i>	<i>Gray</i>	<i>Binary</i>	<i>Gray</i>																																																																							
0 0 0 0		0 0 0 0																																																																								
0 0 0 1		0 0 0 1																																																																								
0 0 1 0		0 0 1 0																																																																								
0 0 1 1		0 0 1 1																																																																								
0 1 0 0		0 1 0 0																																																																								
0 1 0 1		0 1 0 1																																																																								
0 1 1 0		0 1 1 0																																																																								
0 1 1 1		0 1 1 1																																																																								
1 0 0 0		1 0 0 0																																																																								
1 0 0 1		1 0 0 1																																																																								
1 0 1 0		1 0 1 0																																																																								
1 0 1 1		1 0 1 1																																																																								
1 1 0 0		1 1 0 0																																																																								
1 1 0 1		1 1 0 1																																																																								
1 1 1 0		1 1 1 0																																																																								
1 1 1 1		1 1 1 1																																																																								

file 02855

---

Answer 11

Use circuit simulation software to verify your predicted and actual truth tables.

---

Notes 11

I strongly recommend having students build their logic circuits with CMOS chips rather than TTL, because of the less stringent power supply requirements of CMOS. I also recommend drawing a combinational circuit using four gates, because this is the common number of two-input gates found on 14-pin DIP logic chips.



Question 12

Competency: **Gray to Binary code converter**
Version:

**Schematic**

**Given conditions**

$V_{DD} =$ 
 $R_{pulldown} =$ 
 $R_{limit} =$

**Truth table**

**Predicted**

Gray	Binary
0 0 0 0	
0 0 0 1	
0 0 1 1	
0 0 1 0	
0 1 1 0	
0 1 1 1	
0 1 0 1	
0 1 0 0	
1 1 0 0	
1 1 0 1	
1 1 1 1	
1 1 1 0	
1 0 1 0	
1 0 1 1	
1 0 0 1	
1 0 0 0	

**Actual**

Gray	Binary
0 0 0 0	
0 0 0 1	
0 0 1 1	
0 0 1 0	
0 1 1 0	
0 1 1 1	
0 1 0 1	
0 1 0 0	
1 1 0 0	
1 1 0 1	
1 1 1 1	
1 1 1 0	
1 0 1 0	
1 0 1 1	
1 0 0 1	
1 0 0 0	

file 02856

---

**Answer 12**

Use circuit simulation software to verify your predicted and actual truth tables.

---

**Notes 12**

I strongly recommend having students build their logic circuits with CMOS chips rather than TTL, because of the less stringent power supply requirements of CMOS. I also recommend drawing a combinational circuit using four gates, because this is the common number of two-input gates found on 14-pin DIP logic chips.

<b>Competency: Half adder circuit</b>	<b>Version:</b>																																								
<b>Schematic</b>																																									
<b>Given conditions</b>																																									
$V_{DD} =$	$R_{pullup} =$																																								
$R_{limit} =$																																									
<b>Truth table</b>																																									
<b>Predicted</b> <table border="1" style="margin: auto; border-collapse: collapse;"> <thead> <tr> <th>A</th> <th>B</th> <th><math>C_{out}</math></th> <th><math>\Sigma</math></th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td><td></td></tr> <tr><td>0</td><td>1</td><td></td><td></td></tr> <tr><td>1</td><td>0</td><td></td><td></td></tr> <tr><td>1</td><td>1</td><td></td><td></td></tr> </tbody> </table>	A	B	$C_{out}$	$\Sigma$	0	0			0	1			1	0			1	1			<b>Actual</b> <table border="1" style="margin: auto; border-collapse: collapse;"> <thead> <tr> <th>A</th> <th>B</th> <th><math>C_{out}</math></th> <th><math>\Sigma</math></th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td><td></td></tr> <tr><td>0</td><td>1</td><td></td><td></td></tr> <tr><td>1</td><td>0</td><td></td><td></td></tr> <tr><td>1</td><td>1</td><td></td><td></td></tr> </tbody> </table>	A	B	$C_{out}$	$\Sigma$	0	0			0	1			1	0			1	1		
A	B	$C_{out}$	$\Sigma$																																						
0	0																																								
0	1																																								
1	0																																								
1	1																																								
A	B	$C_{out}$	$\Sigma$																																						
0	0																																								
0	1																																								
1	0																																								
1	1																																								

file 02857

---

#### Answer 13

Use circuit simulation software to verify your predicted and actual truth tables.

---

#### Notes 13

It should be noted that the input states in this circuit are defined by the voltage levels, not by the contact status. In other words, a closed contact equals a "low" (0) logic state.

I strongly recommend having students build their logic circuits with CMOS chips rather than TTL, because of the less stringent power supply requirements of CMOS. I also recommend drawing a combinational circuit using four gates, because this is the common number of two-input gates found on 14-pin DIP logic chips.

Competency: <b>Full adder circuit</b>	Version:																																																																																										
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 10px;">Schematic</div>																																																																																											
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 10px;">Given conditions</div> <div style="display: flex; justify-content: space-around; align-items: flex-start;"> <div style="text-align: center;"><math>V_{DD} =</math></div> <div style="text-align: center;"><math>R_{pullup} =</math></div> <div style="text-align: center;"><math>R_{limit} =</math></div> </div>																																																																																											
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 10px;">Truth table</div> <div style="display: flex; justify-content: space-around; align-items: flex-start;"> <div style="text-align: center;"> <p>Predicted</p> <table border="1" style="border-collapse: collapse; text-align: center;"> <thead> <tr> <th>A</th><th>B</th><th>C<sub>in</sub></th><th>C<sub>out</sub></th><th>Σ</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td></td><td></td></tr> <tr><td>0</td><td>0</td><td>1</td><td></td><td></td></tr> <tr><td>0</td><td>1</td><td>0</td><td></td><td></td></tr> <tr><td>0</td><td>1</td><td>1</td><td></td><td></td></tr> <tr><td>1</td><td>0</td><td>0</td><td></td><td></td></tr> <tr><td>1</td><td>0</td><td>1</td><td></td><td></td></tr> <tr><td>1</td><td>1</td><td>0</td><td></td><td></td></tr> <tr><td>1</td><td>1</td><td>1</td><td></td><td></td></tr> </tbody> </table> </div> <div style="text-align: center;"> <p>Actual</p> <table border="1" style="border-collapse: collapse; text-align: center;"> <thead> <tr> <th>A</th><th>B</th><th>C<sub>in</sub></th><th>C<sub>out</sub></th><th>Σ</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td></td><td></td></tr> <tr><td>0</td><td>0</td><td>1</td><td></td><td></td></tr> <tr><td>0</td><td>1</td><td>0</td><td></td><td></td></tr> <tr><td>0</td><td>1</td><td>1</td><td></td><td></td></tr> <tr><td>1</td><td>0</td><td>0</td><td></td><td></td></tr> <tr><td>1</td><td>0</td><td>1</td><td></td><td></td></tr> <tr><td>1</td><td>1</td><td>0</td><td></td><td></td></tr> <tr><td>1</td><td>1</td><td>1</td><td></td><td></td></tr> </tbody> </table> </div> </div>		A	B	C <sub>in</sub>	C <sub>out</sub>	Σ	0	0	0			0	0	1			0	1	0			0	1	1			1	0	0			1	0	1			1	1	0			1	1	1			A	B	C <sub>in</sub>	C <sub>out</sub>	Σ	0	0	0			0	0	1			0	1	0			0	1	1			1	0	0			1	0	1			1	1	0			1	1	1		
A	B	C <sub>in</sub>	C <sub>out</sub>	Σ																																																																																							
0	0	0																																																																																									
0	0	1																																																																																									
0	1	0																																																																																									
0	1	1																																																																																									
1	0	0																																																																																									
1	0	1																																																																																									
1	1	0																																																																																									
1	1	1																																																																																									
A	B	C <sub>in</sub>	C <sub>out</sub>	Σ																																																																																							
0	0	0																																																																																									
0	0	1																																																																																									
0	1	0																																																																																									
0	1	1																																																																																									
1	0	0																																																																																									
1	0	1																																																																																									
1	1	0																																																																																									
1	1	1																																																																																									

file 02858

---

Answer 14

Use circuit simulation software to verify your predicted and actual truth tables.

---

Notes 14

It should be noted that the input states in this circuit are defined by the voltage levels, not by the contact status. In other words, a closed contact equals a "low" (0) logic state.

I strongly recommend having students build their logic circuits with CMOS chips rather than TTL, because of the less stringent power supply requirements of CMOS. I also recommend drawing a combinational circuit using four gates, because this is the common number of two-input gates found on 14-pin DIP logic chips.

Competency: **Full adder circuit w/ NAND gates**
Version:

Schematic

Given conditions

$V_{DD} =$ 
 $R_{pullup} =$ 
 $R_{limit} =$

Truth table

Predicted

A	B	$C_{in}$	$C_{out}$	$\Sigma$
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

Actual

A	B	$C_{in}$	$C_{out}$	$\Sigma$
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

---

Answer 15

Use circuit simulation software to verify your predicted and actual truth tables.

---

Notes 15

It should be noted that the input states in this circuit are defined by the voltage levels, not by the contact status. In other words, a closed contact equals a "low" (0) logic state.

I strongly recommend having students build their logic circuits with CMOS chips rather than TTL, because of the less stringent power supply requirements of CMOS. I also recommend drawing a combinational circuit using four gates, because this is the common number of two-input gates found on 14-pin DIP logic chips.



Competency: <b>Gate circuit from Boolean expression</b>	Version:																														
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Boolean expression</div>																															
<p>Output =</p>																															
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Schematic</div>																															
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Truth table</div>																															
<div style="display: flex; justify-content: space-around; align-items: flex-start;"> <div style="text-align: center;"> <p>Predicted</p> <table border="1" style="border-collapse: collapse; margin: auto;"> <thead> <tr> <th>A</th> <th>B</th> <th>Output</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td></tr> <tr><td>0</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td></td></tr> <tr><td>1</td><td>1</td><td></td></tr> </tbody> </table> </div> <div style="text-align: center;"> <p>Actual</p> <table border="1" style="border-collapse: collapse; margin: auto;"> <thead> <tr> <th>A</th> <th>B</th> <th>Output</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td></tr> <tr><td>0</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td></td></tr> <tr><td>1</td><td>1</td><td></td></tr> </tbody> </table> </div> </div>		A	B	Output	0	0		0	1		1	0		1	1		A	B	Output	0	0		0	1		1	0		1	1	
A	B	Output																													
0	0																														
0	1																														
1	0																														
1	1																														
A	B	Output																													
0	0																														
0	1																														
1	0																														
1	1																														

file 02809

---

#### Answer 16

Use circuit simulation software to verify your predicted and actual truth tables.


---

#### Notes 16

It should be noted that the input states in this circuit are defined by the voltage levels, not by the contact status. In other words, a closed contact equals a "low" (0) logic state.

Here are some suggested Boolean expressions for your students to build gate circuits from:

- Output =  $AB + A$
- Output =  $\overline{A}B + A$
- Output =  $(A + B)A$
- Output =  $(A + B)B$
- Output =  $\overline{A} + B$
- Output =  $A + \overline{B}$
- Output =  $\overline{A}B$
- Output =  $A\overline{B}$

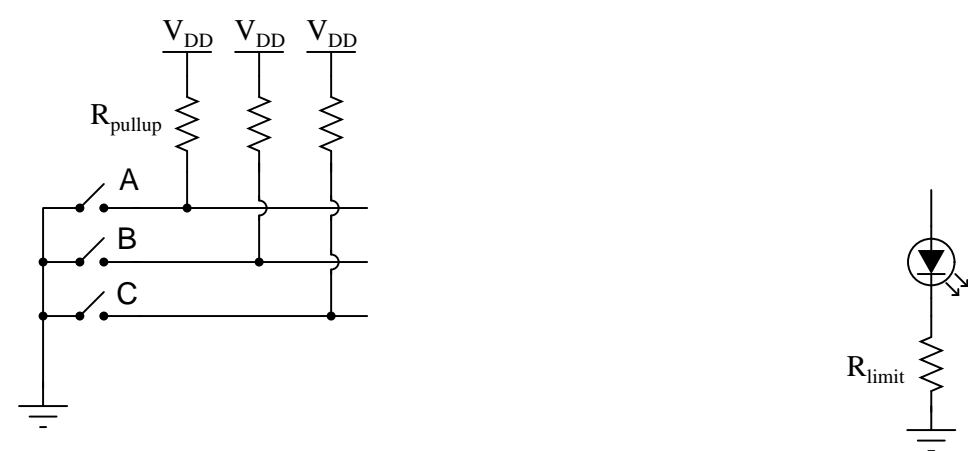Competency: <b>Gate circuit from Boolean expression</b>	Version:																																																																								
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Boolean expression</div>																																																																									
<p style="text-align: center; margin-top: 40px;">Output =</p>																																																																									
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Schematic</div>																																																																									
																																																																									
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Truth table</div>																																																																									
<div style="display: flex; justify-content: space-around; align-items: flex-start;"> <div style="text-align: center;"> <p>Predicted</p> <table border="1" style="border-collapse: collapse; margin: auto;"> <thead> <tr> <th>A</th><th>B</th><th>C</th><th>Output</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td></td></tr> <tr><td>0</td><td>0</td><td>1</td><td></td></tr> <tr><td>0</td><td>1</td><td>0</td><td></td></tr> <tr><td>0</td><td>1</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td>0</td><td></td></tr> <tr><td>1</td><td>0</td><td>1</td><td></td></tr> <tr><td>1</td><td>1</td><td>0</td><td></td></tr> <tr><td>1</td><td>1</td><td>1</td><td></td></tr> </tbody> </table> </div> <div style="text-align: center;"> <p>Actual</p> <table border="1" style="border-collapse: collapse; margin: auto;"> <thead> <tr> <th>A</th><th>B</th><th>C</th><th>Output</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td></td></tr> <tr><td>0</td><td>0</td><td>1</td><td></td></tr> <tr><td>0</td><td>1</td><td>0</td><td></td></tr> <tr><td>0</td><td>1</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td>0</td><td></td></tr> <tr><td>1</td><td>0</td><td>1</td><td></td></tr> <tr><td>1</td><td>1</td><td>0</td><td></td></tr> <tr><td>1</td><td>1</td><td>1</td><td></td></tr> </tbody> </table> </div> </div>		A	B	C	Output	0	0	0		0	0	1		0	1	0		0	1	1		1	0	0		1	0	1		1	1	0		1	1	1		A	B	C	Output	0	0	0		0	0	1		0	1	0		0	1	1		1	0	0		1	0	1		1	1	0		1	1	1	
A	B	C	Output																																																																						
0	0	0																																																																							
0	0	1																																																																							
0	1	0																																																																							
0	1	1																																																																							
1	0	0																																																																							
1	0	1																																																																							
1	1	0																																																																							
1	1	1																																																																							
A	B	C	Output																																																																						
0	0	0																																																																							
0	0	1																																																																							
0	1	0																																																																							
0	1	1																																																																							
1	0	0																																																																							
1	0	1																																																																							
1	1	0																																																																							
1	1	1																																																																							

file 02810

---

#### Answer 17

Use circuit simulation software to verify your predicted and actual truth tables.


---

#### Notes 17

It should be noted that the input states in this circuit are defined by the voltage levels, not by the contact status. In other words, a closed contact equals a "low" (0) logic state.

Here are some suggested Boolean expressions for your students to build gate circuits from:

- Output =  $AB + C$
- Output =  $(A + B)C$
- Output =  $\overline{A} + BC$
- Output =  $\overline{AB} + C$

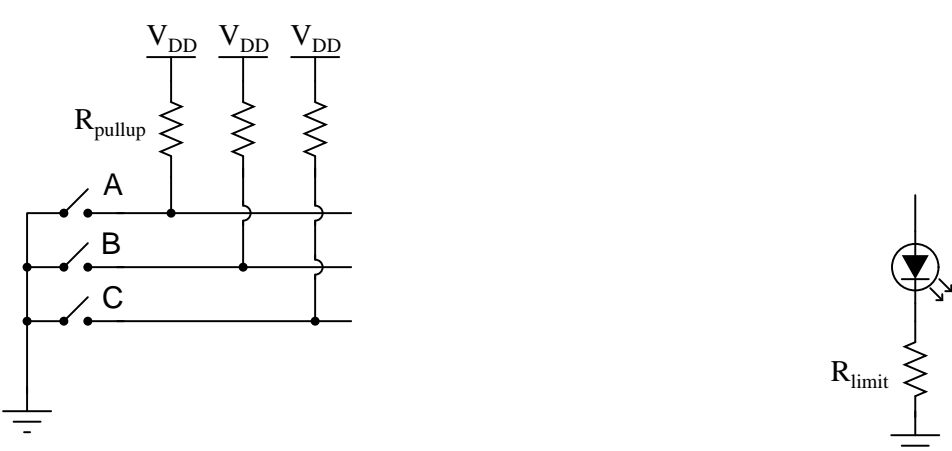Competency: <b>Gate circuit from truth table</b>				Version:																																																																											
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 10px;">Truth table</div> <div style="display: flex; justify-content: space-around; align-items: flex-start;"> <div style="text-align: center;"> <p>Given</p> <table border="1" style="border-collapse: collapse; margin: auto;"> <thead> <tr> <th>A</th> <th>B</th> <th>C</th> <th>Output</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td></td></tr> <tr><td>0</td><td>0</td><td>1</td><td></td></tr> <tr><td>0</td><td>1</td><td>0</td><td></td></tr> <tr><td>0</td><td>1</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td>0</td><td></td></tr> <tr><td>1</td><td>0</td><td>1</td><td></td></tr> <tr><td>1</td><td>1</td><td>0</td><td></td></tr> <tr><td>1</td><td>1</td><td>1</td><td></td></tr> </tbody> </table> </div> <div style="text-align: center;"> <p>Actual</p> <table border="1" style="border-collapse: collapse; margin: auto;"> <thead> <tr> <th>A</th> <th>B</th> <th>C</th> <th>Output</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td></td></tr> <tr><td>0</td><td>0</td><td>1</td><td></td></tr> <tr><td>0</td><td>1</td><td>0</td><td></td></tr> <tr><td>0</td><td>1</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td>0</td><td></td></tr> <tr><td>1</td><td>0</td><td>1</td><td></td></tr> <tr><td>1</td><td>1</td><td>0</td><td></td></tr> <tr><td>1</td><td>1</td><td>1</td><td></td></tr> </tbody> </table> </div> </div>								A	B	C	Output	0	0	0		0	0	1		0	1	0		0	1	1		1	0	0		1	0	1		1	1	0		1	1	1		A	B	C	Output	0	0	0		0	0	1		0	1	0		0	1	1		1	0	0		1	0	1		1	1	0		1	1	1	
A	B	C	Output																																																																												
0	0	0																																																																													
0	0	1																																																																													
0	1	0																																																																													
0	1	1																																																																													
1	0	0																																																																													
1	0	1																																																																													
1	1	0																																																																													
1	1	1																																																																													
A	B	C	Output																																																																												
0	0	0																																																																													
0	0	1																																																																													
0	1	0																																																																													
0	1	1																																																																													
1	0	0																																																																													
1	0	1																																																																													
1	1	0																																																																													
1	1	1																																																																													
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 10px;">Schematic</div> <div style="display: flex; justify-content: space-around; align-items: center;">  </div>																																																																															

file 02134

---

Answer 18

Use circuit simulation software to verify your predicted and actual truth tables.

---

Notes 18

It should be noted that the input states in this circuit are defined by the voltage levels, not by the contact status. In other words, a closed contact equals a "low" (0) logic state.

Suggested truth tables include the following (encoded as Boolean SOP statements):

- $AB\overline{C} + ABC$
- $\overline{A}B\overline{C} + \overline{A}BC$
- $\overline{A}B\overline{C} + \overline{A}BC + \overline{A}\overline{B}\overline{C}$
- $\overline{A}\overline{B}\overline{C} + A\overline{B}\overline{C}$
- $AB\overline{C} + \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}\overline{C}$
- $\overline{A}BC + \overline{A}\overline{B}C + \overline{A}\overline{B}\overline{C}$
- $ABC + \overline{A}BC + AB\overline{C}$
- $\overline{A}BC + \overline{A}\overline{B}C + \overline{A}\overline{B}\overline{C}$
- $ABC + \overline{A}BC + \overline{A}\overline{B}C$

I strongly recommend having students build their logic circuits with CMOS chips rather than TTL, because of the less stringent power supply requirements of CMOS. I also recommend drawing a combinational circuit using four gates, because this is the common number of two-input gates found on 14-pin DIP logic chips.

Competency: 4-line to 16-line decoder IC					Version:														
Truth table																			
D	C	B	A	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
0	0	0	0																
0	0	0	1																
0	0	1	0																
0	0	1	1																
0	1	0	0																
0	1	0	1																
0	1	1	0																
0	1	1	1																
1	0	0	0																
1	0	0	1																
1	0	1	0																
1	0	1	1																
1	1	0	0																
1	1	0	1																
1	1	1	0																
1	1	1	1																

Schematic	

file 03009

---

#### Answer 19

Use circuit simulation software to verify your predicted and actual truth tables.

---

#### Notes 19

It should be noted that the input states in this circuit are defined by the voltage levels, not by the contact status. In other words, a closed contact equals a "low" (0) logic state.

Here, the arrangement of the input letters D, C, B, and A is purposeful: D represents the most significant bit, while A represents the least significant bit, just like the IC datasheets typically order the input lines.

Normally, I draw LEDs in the schematic to give visual indication of output states. Here, due to the sheer number of required LEDs (16), I decided not to. However, students with access to lots of LEDs may choose to add them to their circuits, because visual indicators do make the circuit's function easier to understand.

If the decoder IC has enable inputs, the students must figure out what to do with them to make the circuit function!



<b>Competency: Arbitrary logic function using mux</b>				Version:																																																																											
<b>Truth table</b>																																																																															
<div style="display: flex; justify-content: space-around;"><div style="text-align: center;"><p>Given</p><table border="1" style="border-collapse: collapse; margin: auto;"><thead><tr><th>C</th><th>B</th><th>A</th><th>Output</th></tr></thead><tbody><tr><td>0</td><td>0</td><td>0</td><td></td></tr><tr><td>0</td><td>0</td><td>1</td><td></td></tr><tr><td>0</td><td>1</td><td>0</td><td></td></tr><tr><td>0</td><td>1</td><td>1</td><td></td></tr><tr><td>1</td><td>0</td><td>0</td><td></td></tr><tr><td>1</td><td>0</td><td>1</td><td></td></tr><tr><td>1</td><td>1</td><td>0</td><td></td></tr><tr><td>1</td><td>1</td><td>1</td><td></td></tr></tbody></table></div><div style="text-align: center;"><p>Actual</p><table border="1" style="border-collapse: collapse; margin: auto;"><thead><tr><th>C</th><th>B</th><th>A</th><th>Output</th></tr></thead><tbody><tr><td>0</td><td>0</td><td>0</td><td></td></tr><tr><td>0</td><td>0</td><td>1</td><td></td></tr><tr><td>0</td><td>1</td><td>0</td><td></td></tr><tr><td>0</td><td>1</td><td>1</td><td></td></tr><tr><td>1</td><td>0</td><td>0</td><td></td></tr><tr><td>1</td><td>0</td><td>1</td><td></td></tr><tr><td>1</td><td>1</td><td>0</td><td></td></tr><tr><td>1</td><td>1</td><td>1</td><td></td></tr></tbody></table></div></div>								C	B	A	Output	0	0	0		0	0	1		0	1	0		0	1	1		1	0	0		1	0	1		1	1	0		1	1	1		C	B	A	Output	0	0	0		0	0	1		0	1	0		0	1	1		1	0	0		1	0	1		1	1	0		1	1	1	
C	B	A	Output																																																																												
0	0	0																																																																													
0	0	1																																																																													
0	1	0																																																																													
0	1	1																																																																													
1	0	0																																																																													
1	0	1																																																																													
1	1	0																																																																													
1	1	1																																																																													
C	B	A	Output																																																																												
0	0	0																																																																													
0	0	1																																																																													
0	1	0																																																																													
0	1	1																																																																													
1	0	0																																																																													
1	0	1																																																																													
1	1	0																																																																													
1	1	1																																																																													
<b>Schematic</b>																																																																															
<i>You draw it, in its entirety!</i>																																																																															

---

Answer 20

Use circuit simulation software to verify your predicted and actual truth tables.

---

Notes 20

The purpose of this exercise is for students to connect a multiplexer to fulfill an arbitrary logic function specified by the instructor, thus showing the flexibility of the technique.

Here, the arrangement of the input letters C, B, and A is purposeful: C represents the most significant bit, while A represents the least significant bit, just like the IC datasheets typically order the input lines.

Competency: <b>NAND gate universality</b>	Version:																														
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Description</div>																															
Emulate the specified logic function using nothing but interconnected NAND gates.																															
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Emulated function</div> <span style="margin-left: 10px;"><i>(instructor checks one box)</i></span>																															
<div style="display: flex; justify-content: space-around; align-items: center;"> <div style="text-align: center;"> <input style="width: 30px; height: 20px; border: 1px solid black;" type="checkbox"/> AND         </div> <div style="text-align: center;"> <input style="width: 30px; height: 20px; border: 1px solid black;" type="checkbox"/> OR         </div> <div style="text-align: center;"> <input style="width: 30px; height: 20px; border: 1px solid black;" type="checkbox"/> NOR         </div> </div>																															
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Diagram</div>																															
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Truth table</div>																															
<div style="display: flex; justify-content: space-around; align-items: flex-start;"> <div style="text-align: center;"> <p>Predicted</p> <table border="1" style="border-collapse: collapse; margin: auto;"> <thead> <tr> <th>A</th> <th>B</th> <th>Output</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td></tr> <tr><td>0</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td></td></tr> <tr><td>1</td><td>1</td><td></td></tr> </tbody> </table> </div> <div style="text-align: center;"> <p>Actual</p> <table border="1" style="border-collapse: collapse; margin: auto;"> <thead> <tr> <th>A</th> <th>B</th> <th>Output</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td></tr> <tr><td>0</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td></td></tr> <tr><td>1</td><td>1</td><td></td></tr> </tbody> </table> </div> </div>		A	B	Output	0	0		0	1		1	0		1	1		A	B	Output	0	0		0	1		1	0		1	1	
A	B	Output																													
0	0																														
0	1																														
1	0																														
1	1																														
A	B	Output																													
0	0																														
0	1																														
1	0																														
1	1																														

file 02807

---


Answer 21

Use circuit simulation software to verify your predicted and actual truth tables.

---

Notes 21

Here, I let students choose appropriate values for  $R_{pullup}$  and  $R_{limit}$ , rather than specify them as given conditions.

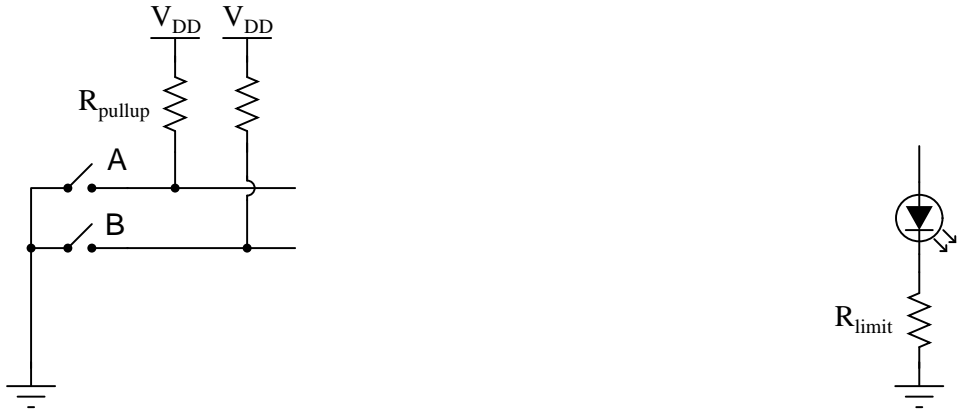Competency: <b>NOR gate universality</b>	Version:																														
<div style="border: 1px solid black; padding: 2px; display: inline-block;">Description</div> <p style="text-align: center; margin-top: 20px;">Emulate the specified logic function using nothing but interconnected NOR gates.</p>																															
<div style="border: 1px solid black; padding: 2px; display: inline-block;">Emulated function</div> <span style="margin-left: 10px;"><i>(instructor checks one box)</i></span>																															
<div style="display: flex; justify-content: space-around; align-items: center;"> <div><input type="checkbox"/> AND</div> <div><input type="checkbox"/> OR</div> <div><input type="checkbox"/> NAND</div> </div>																															
<div style="border: 1px solid black; padding: 2px; display: inline-block;">Diagram</div>																															
																															
<div style="border: 1px solid black; padding: 2px; display: inline-block;">Truth table</div>																															
<div style="display: flex; justify-content: space-around; margin-bottom: 10px;"> <div>Predicted</div> <div>Actual</div> </div> <div style="display: flex; justify-content: space-around;"> <table border="1" style="border-collapse: collapse; text-align: center;"> <thead> <tr> <th>A</th> <th>B</th> <th>Output</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td></tr> <tr><td>0</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td></td></tr> <tr><td>1</td><td>1</td><td></td></tr> </tbody> </table> <table border="1" style="border-collapse: collapse; text-align: center;"> <thead> <tr> <th>A</th> <th>B</th> <th>Output</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td></tr> <tr><td>0</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td></td></tr> <tr><td>1</td><td>1</td><td></td></tr> </tbody> </table> </div>		A	B	Output	0	0		0	1		1	0		1	1		A	B	Output	0	0		0	1		1	0		1	1	
A	B	Output																													
0	0																														
0	1																														
1	0																														
1	1																														
A	B	Output																													
0	0																														
0	1																														
1	0																														
1	1																														

file 02808

---


Answer 22

Use circuit simulation software to verify your predicted and actual truth tables.

---

Notes 22

Here, I let students choose appropriate values for  $R_{pullup}$  and  $R_{limit}$ , rather than specify them as given conditions.

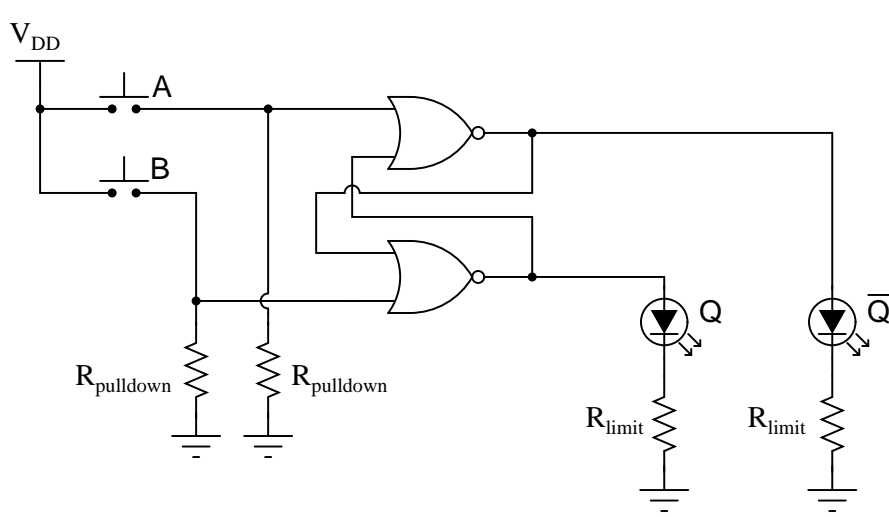Competency: <b>S-R latch using NOR gates</b>	Version:																																								
<div style="border: 1px solid black; padding: 2px; margin-bottom: 5px;">Schematic</div> 																																									
<div style="border: 1px solid black; padding: 2px; margin-bottom: 5px;">Given conditions</div> <div style="display: flex; justify-content: space-around; align-items: flex-start;"> <div style="text-align: center;"><math>V_{DD} =</math></div> <div style="text-align: center;"><math>R_{pulldown} =</math></div> <div style="text-align: center;"><math>R_{limit} =</math></div> </div>																																									
<div style="border: 1px solid black; padding: 2px; margin-bottom: 5px;">Truth table</div> <div style="display: flex; justify-content: space-around; align-items: flex-start;"> <div style="text-align: center;"> <p>Predicted</p> <table border="1" style="border-collapse: collapse; text-align: center;"> <thead> <tr> <th>A</th> <th>B</th> <th>Q</th> <th><math>\overline{Q}</math></th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td><td></td></tr> <tr><td>0</td><td>1</td><td></td><td></td></tr> <tr><td>1</td><td>0</td><td></td><td></td></tr> <tr><td>1</td><td>1</td><td></td><td></td></tr> </tbody> </table> </div> <div style="text-align: center;"> <p>Actual</p> <table border="1" style="border-collapse: collapse; text-align: center;"> <thead> <tr> <th>A</th> <th>B</th> <th>Q</th> <th><math>\overline{Q}</math></th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td><td></td></tr> <tr><td>0</td><td>1</td><td></td><td></td></tr> <tr><td>1</td><td>0</td><td></td><td></td></tr> <tr><td>1</td><td>1</td><td></td><td></td></tr> </tbody> </table> </div> </div>		A	B	Q	$\overline{Q}$	0	0			0	1			1	0			1	1			A	B	Q	$\overline{Q}$	0	0			0	1			1	0			1	1		
A	B	Q	$\overline{Q}$																																						
0	0																																								
0	1																																								
1	0																																								
1	1																																								
A	B	Q	$\overline{Q}$																																						
0	0																																								
0	1																																								
1	0																																								
1	1																																								
<div style="border: 1px solid black; padding: 2px; margin-bottom: 5px;">Experiment</div> <p>What happens when you use different values of <math>R_{limit}</math> resistance?</p> <p><i>Hint: try 10 <math>\Omega</math> versus 1000 <math>\Omega</math> to see the difference it makes!</i></p>																																									

---

#### Answer 23

Use circuit simulation software to verify your predicted and actual truth tables.


---
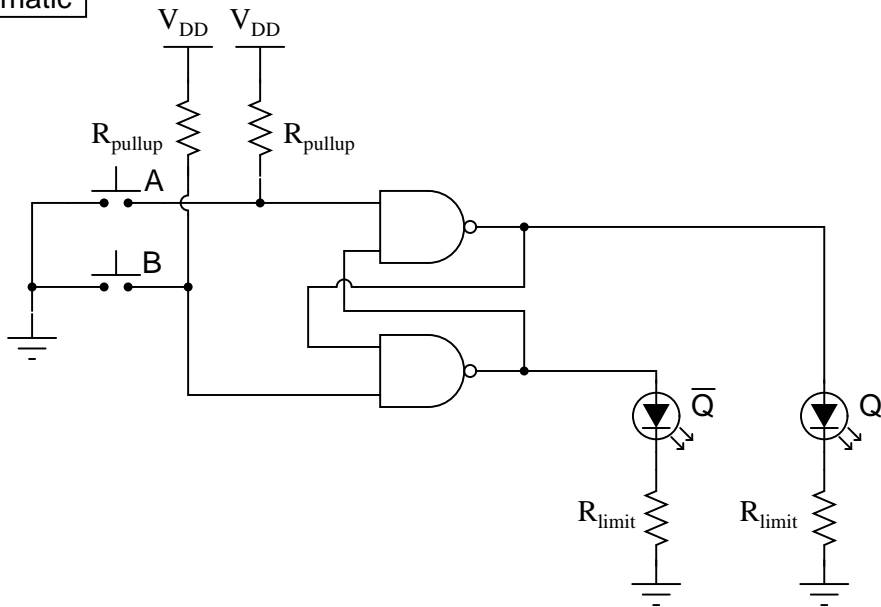
#### Notes 23

Pushbutton switches are recommended over toggle switches for demonstrating a latch circuit. When the contacts are momentary, the latching characteristics of the circuit becomes more evident to see.

I have intentionally requested students try different resistance values for  $R_{limit}$  so they may see the effects of gate output *loading*, and the importance of proper logic level voltages. Students should try undersized resistors (10  $\Omega$ , perhaps) on both LEDs to generate this problem, and then use oversized resistors (1000  $\Omega$ , perhaps) to make the problem go away. Large-valued limiting resistors will cause the LEDs to be dim, but will also restore workable voltage levels so that "high" output states are actually interpreted as "high" when fed back to the gate inputs.



Competency: <b>S-R latch using NAND gates</b>		Version:																																								
<b>Schematic</b>																																										
<b>Given conditions</b>	$V_{DD} =$ $R_{pullup} =$ $R_{limit} =$																																									
<b>Truth table</b>	<div style="display: flex; justify-content: space-around; align-items: flex-start;"> <div style="text-align: center;"> <p>Predicted</p> <table border="1" style="border-collapse: collapse; margin: auto;"> <thead> <tr> <th>A</th> <th>B</th> <th>Q</th> <th><math>\bar{Q}</math></th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td><td></td></tr> <tr><td>0</td><td>1</td><td></td><td></td></tr> <tr><td>1</td><td>0</td><td></td><td></td></tr> <tr><td>1</td><td>1</td><td></td><td></td></tr> </tbody> </table> </div> <div style="text-align: center;"> <p>Actual</p> <table border="1" style="border-collapse: collapse; margin: auto;"> <thead> <tr> <th>A</th> <th>B</th> <th>Q</th> <th><math>\bar{Q}</math></th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td><td></td></tr> <tr><td>0</td><td>1</td><td></td><td></td></tr> <tr><td>1</td><td>0</td><td></td><td></td></tr> <tr><td>1</td><td>1</td><td></td><td></td></tr> </tbody> </table> </div> </div>		A	B	Q	$\bar{Q}$	0	0			0	1			1	0			1	1			A	B	Q	$\bar{Q}$	0	0			0	1			1	0			1	1		
A	B	Q	$\bar{Q}$																																							
0	0																																									
0	1																																									
1	0																																									
1	1																																									
A	B	Q	$\bar{Q}$																																							
0	0																																									
0	1																																									
1	0																																									
1	1																																									
<b>Experiment</b>	<p>What happens when you use different values of <math>R_{limit}</math> resistance?</p> <p><i>Hint: try 10 <math>\Omega</math> versus 1000 <math>\Omega</math> to see the difference it makes!</i></p>																																									

---

#### Answer 24




Use circuit simulation software to verify your predicted and actual truth tables.

---

#### Notes 24

Pushbutton switches are recommended over toggle switches for demonstrating a latch circuit. When the contacts are momentary, the latching characteristics of the circuit becomes more evident to see.

I have intentionally requested students try different resistance values for  $R_{limit}$  so they may see the effects of gate output *loading*, and the importance of proper logic level voltages. Students should try undersized resistors (10  $\Omega$ , perhaps) on both LEDs to generate this problem, and then use oversized resistors (1000  $\Omega$ , perhaps) to make the problem go away. Large-valued limiting resistors will cause the LEDs to be dim, but will also restore workable voltage levels so that "high" output states are actually interpreted as "high" when fed back to the gate inputs.

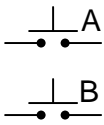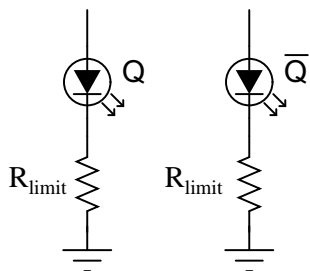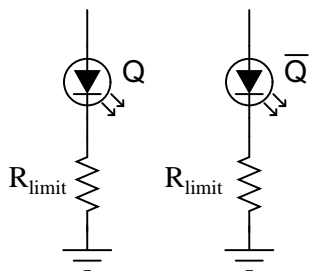Competency: <b>S-R latch circuit</b>	Version:																																								
<div style="border: 1px solid black; padding: 2px; display: inline-block;">Description</div>																																									
<p style="text-align: center;">Build an S-R latch circuit using either NAND or NOR gates</p>																																									
<div style="border: 1px solid black; padding: 2px; display: inline-block;">Schematic</div>																																									
<div style="display: flex; justify-content: space-around; align-items: center;"> <div style="text-align: center;">  <p>A</p> </div> <div style="text-align: center;">  <p>B</p> </div> </div> <div style="text-align: right; margin-top: 100px;">  </div>																																									
<div style="border: 1px solid black; padding: 2px; display: inline-block;">Truth table</div>																																									
<div style="display: flex; justify-content: space-around;"> <div style="text-align: center;"> <p>Predicted</p> <table border="1" style="border-collapse: collapse; text-align: center;"> <thead> <tr> <th>A</th><th>B</th><th>Q</th><th><math>\overline{Q}</math></th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td><td></td></tr> <tr><td>0</td><td>1</td><td></td><td></td></tr> <tr><td>1</td><td>0</td><td></td><td></td></tr> <tr><td>1</td><td>1</td><td></td><td></td></tr> </tbody> </table> </div> <div style="text-align: center;"> <p>Actual</p> <table border="1" style="border-collapse: collapse; text-align: center;"> <thead> <tr> <th>A</th><th>B</th><th>Q</th><th><math>\overline{Q}</math></th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td><td></td></tr> <tr><td>0</td><td>1</td><td></td><td></td></tr> <tr><td>1</td><td>0</td><td></td><td></td></tr> <tr><td>1</td><td>1</td><td></td><td></td></tr> </tbody> </table> </div> </div>		A	B	Q	$\overline{Q}$	0	0			0	1			1	0			1	1			A	B	Q	$\overline{Q}$	0	0			0	1			1	0			1	1		
A	B	Q	$\overline{Q}$																																						
0	0																																								
0	1																																								
1	0																																								
1	1																																								
A	B	Q	$\overline{Q}$																																						
0	0																																								
0	1																																								
1	0																																								
1	1																																								

file 01621

---

Answer 25

Use circuit simulation software to verify your predicted and actual truth tables.

---

Notes 25

Pushbutton switches are recommended over toggle switches for demonstrating a latch circuit. When the contacts are momentary, the latching characteristics of the circuit becomes more evident to see.

If students use LEDs to indicate the  $Q$  and  $\overline{Q}$  output states, they may experience trouble with the circuit not latching as it should. This is an excellent example of gate output *loading*, and the importance of proper logic level voltages. If such problems are encountered, advise the student(s) to use over-sized (too large) LED dropping resistors. This will cause the LEDs to be dim, but restore workable voltage levels so that "high" output states are actually interpreted as "high" when fed back to the gate inputs.

<b>Competency: J-K flip-flop IC</b>	<b>Version:</b>
<div style="border: 1px solid black; padding: 2px; margin-bottom: 5px;"><b>Description</b></div> <p style="text-align: center;">Demonstrate the "set," "reset," and "toggle" modes of a J-K flip-flop integrated circuit.</p>	
<div style="border: 1px solid black; padding: 2px; margin-bottom: 5px;"><b>Schematic</b></div>	
<div style="border: 1px solid black; padding: 2px; margin-bottom: 5px;"><b>Parameters</b></div> <p style="text-align: center;">         "Set" mode demonstrated <input style="width: 40px; height: 20px;" type="checkbox"/> </p> <p style="text-align: center;">         "Reset" mode demonstrated <input style="width: 40px; height: 20px;" type="checkbox"/> </p> <p style="text-align: center;">         "Toggle" mode demonstrated <input style="width: 40px; height: 20px;" type="checkbox"/> </p>	

file 02900

---

#### Answer 26



Use circuit simulation software to verify your predicted and actual truth tables.

---

#### Notes 26

In this activity, students are asked to figure out how to wire the inputs of the J-K flip-flop circuit, and also how to demonstrate the three modes (Set, Reset, and Toggle). Students will have to properly set up their square-wave signal generators to create a workable clock pulse. This not only means a clock pulse at the correct voltage levels, but also one that is slow enough to allow them to clearly see the toggling of the flip-flop.

A great thing to do here is have students use a logic probe to sense the clock pulse and compare that frequency with the blinking of the  $Q$  and  $\overline{Q}$  LEDs.

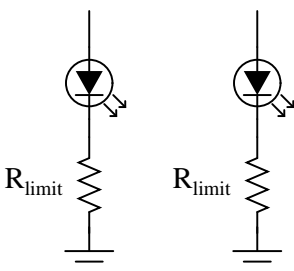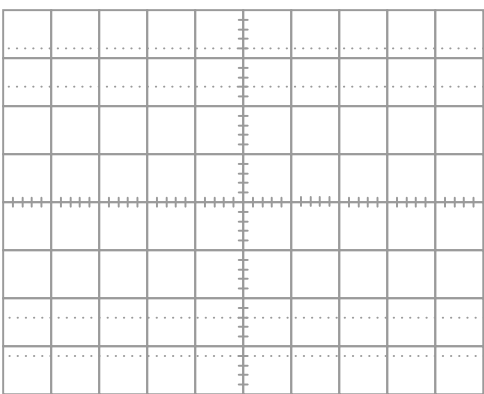Competency: <b>2-bit flip-flop counter circuit</b>	Version:
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Description</div>	
Build a 2-bit counter circuit using individual J-K flip-flops.	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Schematic</div>	
	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Count sequence</div>	
<p style="text-align: right;"><i>Output timing diagram as shown by oscilloscope</i></p> <div style="display: flex; align-items: flex-start;"> <div style="margin-right: 20px;"> <p>Predicted      Actual</p> <div style="display: flex; align-items: center;"> <div style="text-align: center; margin-right: 10px;">             Time ↓           </div> <div style="display: flex; flex-direction: column; gap: 5px;"> <div style="border: 1px solid black; width: 60px; height: 20px;"></div> <div style="border: 1px solid black; width: 60px; height: 20px;"></div> <div style="border: 1px solid black; width: 60px; height: 20px;"></div> <div style="border: 1px solid black; width: 60px; height: 20px;"></div> </div> </div> <div style="display: flex; flex-direction: column; gap: 5px;"> <div style="border: 1px solid black; width: 60px; height: 20px;"></div> <div style="border: 1px solid black; width: 60px; height: 20px;"></div> <div style="border: 1px solid black; width: 60px; height: 20px;"></div> <div style="border: 1px solid black; width: 60px; height: 20px;"></div> </div> </div> </div> <div style="margin-left: 20px;">  </div>	

file 02947

---

Answer 27


Use circuit simulation software to verify your predicted and actual truth tables.

---

Notes 27

One lesson of digital circuits many students learn the hard way is the importance of not leaving CMOS inputs floating. In this case, the lesson is often learned in the form of leaving asynchronous inputs of the J-K flip-flops floating (preset, clear, or both). Be sure to check to see that all chip inputs are accounted for before passing students on this competency. If you see an input floating, touch the chip pin with a pen or pencil and let your students see the effect static has on their circuit!

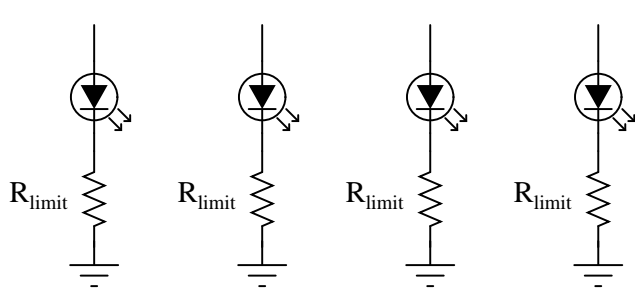

Competency: <b>4-bit flip-flop counter circuit</b>		Version:																																																																																																																																	
Description																																																																																																																																			
Build a 4-bit counter circuit using individual J-K flip-flops																																																																																																																																			
Schematic																																																																																																																																			
																																																																																																																																			
Count sequence																																																																																																																																			
	Predicted	Actual																																																																																																																																	
Time ↓	<table border="1" data-bbox="670 1265 774 1668"><tr><td></td><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td><td></td></tr></table>																																																																	<table border="1" data-bbox="885 1265 989 1668"><tr><td></td><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td><td></td></tr><tr><td></td><td></td><td></td><td></td></tr></table>																																																																	

file 02135

---


Answer 28

Use circuit simulation software to verify your predicted and actual truth tables.

---

Notes 28

I strongly recommend having students build their logic circuits with CMOS chips rather than TTL, because of the less stringent power supply requirements of CMOS.

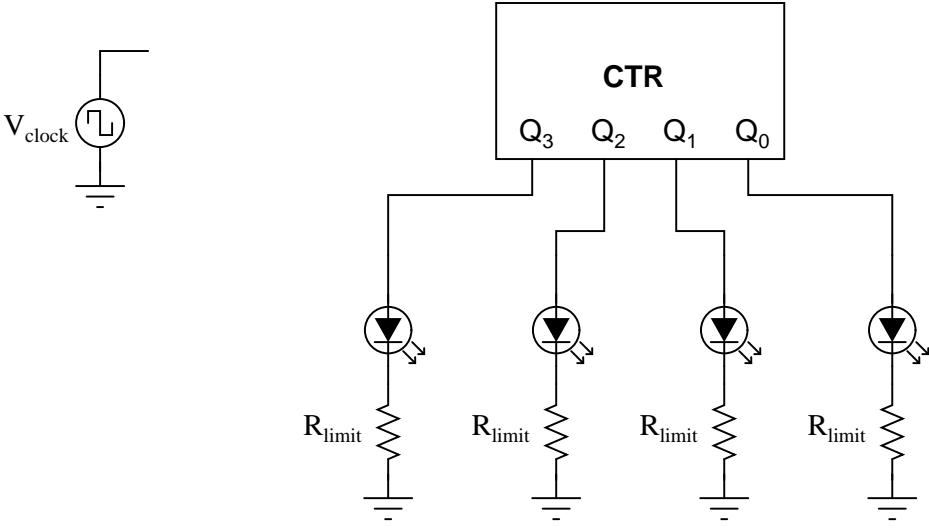Competency: <b>4-bit up/down counter IC</b>	Version:
<b>Description</b>	
Configure a 4-bit counter IC to count either up or down depending on the position of a selector switch. Complete the schematic diagram to show the switch and all other necessary components/connections.	
<b>Schematic</b>	
	
<b>Count sequence</b>	
Counts in the "up" direction	<input type="checkbox"/>
Counts in the "down" direction	<input type="checkbox"/>

file 02957

---

Answer 29

Use circuit simulation software to verify your predicted and actual truth tables.

---

Notes 29

Students are to research the datasheet for their particular IC and figure out from that what connections and timing sequences they need to make the circuit perform as requested. It is very important for students to learn to interpret manufacturers' datasheets!

I recommend a slow clock frequency (1 Hz or so) to allow for easy viewing of the count sequence.

Competency: <b>BCD to 7-segment decoder/driver IC</b> Version:	
Schematic	
Parameters	
All numerals (0 through 9) demonstrated <input style="width: 30px; height: 20px;" type="checkbox"/>	
Fault analysis	
Suppose component <input style="width: 50px; height: 20px;" type="text"/> fails <input style="width: 20px; height: 20px;" type="checkbox"/> open <input style="width: 20px; height: 20px;" type="checkbox"/> other _____ <input style="width: 20px; height: 20px;" type="checkbox"/> shorted What will happen in the circuit?	

file 03010

---


Answer 30

Use circuit simulation software to verify your predicted and actual truth tables.

---

Notes 30

Students are left on their own to figure out what they must do with the other inputs (lamp test, BI, RBI, etc.) to make the decoder/driver chip function properly.

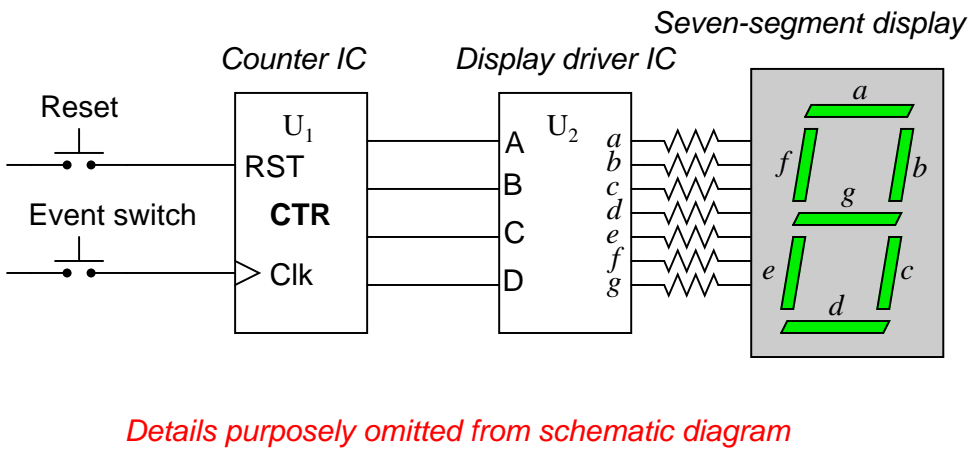Competency: <b>Decade counter circuit</b>	Version:
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 10px;">Schematic</div>  <p style="color: red; text-align: center; margin-top: 10px;"><i>Details purposely omitted from schematic diagram</i></p>	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 10px;">Given conditions</div> <p style="margin-top: 10px;"> <math>U_1 =</math> <span style="margin-left: 150px;"><math>U_2 =</math></span> </p>	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 10px;">Parameters</div> <p style="margin-top: 10px;"> Counter increments with each physical event, counting from 0 to 9 and then resetting back to 0 again. Count sequence exhibits no skipped counts and no missed events. <div style="float: right; margin-top: -20px;"> <input type="checkbox"/> YES  <input type="checkbox"/> NO </div> </p>	

file 03851

---

#### Answer 31

Use circuit simulation software to verify your predicted and measured parameter values.

---


#### Notes 31

I have purposely left the details of the schematic diagram vague, so that students must do a lot of datasheet research on their own to figure out how to make an event counter circuit. You may choose to give your students part numbers for the integrated circuits, or choose not to, depending on how capable your students are. The point is, they must figure out how to make the ICs work based on what they read from the manufacturer.

Something else students will probably have to do is de-bounce the event switch. Some event switches are inherently bounceless, while others are definitely not. Switch debouncing is something your students need to learn about and integrate into this circuit.

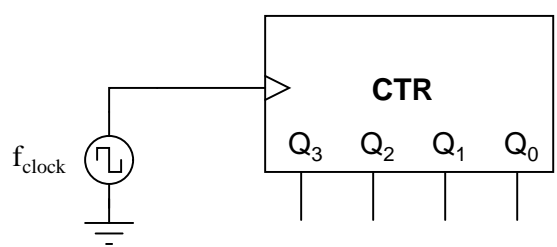An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.



<b>Competency: Binary counter as frequency divider</b>		Version:
<b>Schematic</b>		
		
<b>Given conditions</b>		
$f_{\text{clock}} =$		
<b>Parameters</b>		
	Predicted	Measured
$f_{Q0}$	<input style="width: 100px; height: 30px;" type="text"/>	<input style="width: 100px; height: 30px;" type="text"/>
$f_{Q1}$	<input style="width: 100px; height: 30px;" type="text"/>	<input style="width: 100px; height: 30px;" type="text"/>
$f_{Q2}$	<input style="width: 100px; height: 30px;" type="text"/>	<input style="width: 100px; height: 30px;" type="text"/>
$f_{Q3}$	<input style="width: 100px; height: 30px;" type="text"/>	<input style="width: 100px; height: 30px;" type="text"/>

---

**Answer 32**


Use circuit simulation software to verify your predicted and actual truth tables.

---

**Notes 32**

Students are to research the datasheet for their particular IC and figure out from that what connections and timing sequences they need to make the circuit perform as requested. It is very important for students to learn to interpret manufacturers' datasheets!

I recommend a slow clock frequency (1 Hz or so) to allow for easy viewing of the shift patterns. To conserve the number of necessary input switches, I allow students to hard-wire the data inputs ( $D_0$  through  $D_3$ ). This means they only need switches to control the mode of the shift register (parallel load, shift right, shift left, and shift inhibit).

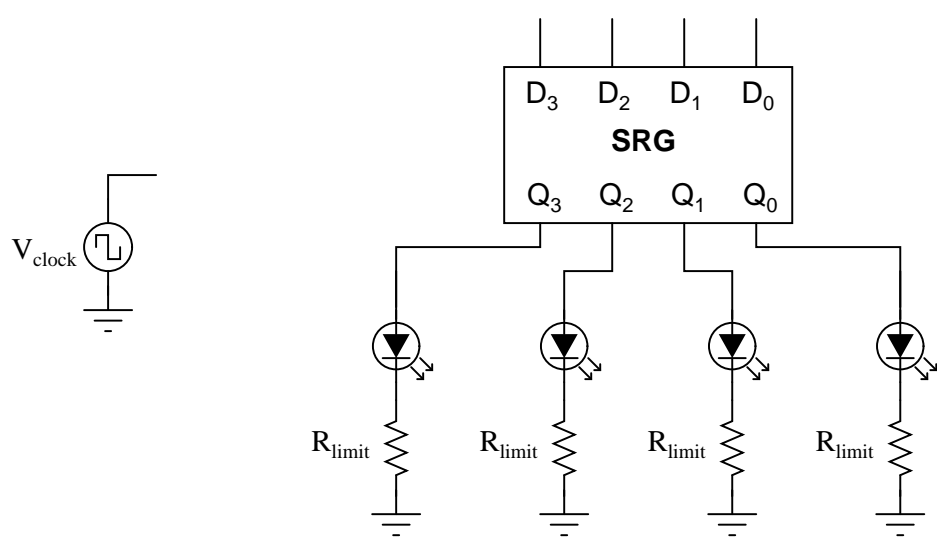Competency: <b>4-bit universal shift register IC</b>	Version:
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 10px;">Description</div> <p>Configure a 4-bit universal shift register IC to load parallel data, then shift in both directions. Complete the schematic diagram to show all switches and other necessary components/connections.</p>	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 10px;">Schematic</div> 	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 10px;">Shift sequence</div> <p>Loads parallel data <input style="margin-left: 10px;" type="checkbox"/></p> <p>Shifts right <input style="margin-left: 10px;" type="checkbox"/></p> <p>Shifts left <input style="margin-left: 10px;" type="checkbox"/></p>	

file 02958

---

### Answer 33

Use circuit simulation software to verify your predicted and actual truth tables.

---

### Notes 33

Students are to research the datasheet for their particular IC and figure out from that what connections and timing sequences they need to make the circuit perform as requested. It is very important for students to learn to interpret manufacturers' datasheets!

I recommend a slow clock frequency (1 Hz or so) to allow for easy viewing of the shift patterns. To conserve the number of necessary input switches, I allow students to hard-wire the data inputs ( $D_0$  through  $D_3$ ). This means they only need switches to control the mode of the shift register (parallel load, shift right, shift left, and shift inhibit).

Competency: <b>Stepper motor drive circuit</b>		Version:
<b>Description</b>		
<p>Design a simple circuit for driving a stepper motor using four pushbutton switches (pushing the switches in the correct sequence will cause the motor to turn).</p>		
<b>Schematic</b>		

file 01619

---

#### Answer 34

The real circuit you build will validate your circuit design.

---

#### Notes 34

Use a four-pole, unipolar stepper motor for this assessment, with a power supply capable of sourcing the required current.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: <b>Relay start/stop motor control circuit</b> Version:																															
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Description</div>																															
Build a start/stop motor control circuit using an electromechanical relay and two pushbutton switches																															
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Schematic</div>																															
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Truth table</div>																															
<div style="display: flex; justify-content: space-around;"> <table border="1" style="border-collapse: collapse; text-align: center;"> <caption>Predicted</caption> <thead> <tr> <th>Start</th> <th>Stop</th> <th>Motor</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td></tr> <tr><td>0</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td></td></tr> <tr><td>1</td><td>1</td><td></td></tr> </tbody> </table> <table border="1" style="border-collapse: collapse; text-align: center;"> <caption>Actual</caption> <thead> <tr> <th>Start</th> <th>Stop</th> <th>Motor</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td></td></tr> <tr><td>0</td><td>1</td><td></td></tr> <tr><td>1</td><td>0</td><td></td></tr> <tr><td>1</td><td>1</td><td></td></tr> </tbody> </table> </div>		Start	Stop	Motor	0	0		0	1		1	0		1	1		Start	Stop	Motor	0	0		0	1		1	0		1	1	
Start	Stop	Motor																													
0	0																														
0	1																														
1	0																														
1	1																														
Start	Stop	Motor																													
0	0																														
0	1																														
1	0																														
1	1																														
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Fault analysis</div>																															
Suppose component <span style="border: 1px solid black; display: inline-block; width: 50px; height: 20px; vertical-align: middle;"></span> fails <div style="display: flex; justify-content: flex-end; margin-top: 5px;"> <div style="display: flex; align-items: center; margin-right: 20px;"> <input type="checkbox"/> open           <input type="checkbox"/> other _____         </div> <input type="checkbox"/> shorted       </div> <p><i>What will happen in the circuit?</i></p>																															

---

Answer 35

The real circuit you build will validate your circuit design.

---

Notes 35

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.



Competency: <b>Relay start/stop motor control circuit</b> Version:	
Description	<p>Build a start/stop motor control circuit using an electro-mechanical relay and two (momentary) pushbutton switches</p>
Schematic	
Parameters	<p>Motor latches in the energized state when "Start" switch is pressed and released <input type="checkbox"/></p> <p>Motor latches in the de-energized state when "Stop" switch is pressed and released <input type="checkbox"/></p>

file 02390

---

Answer 36

The real circuit you build will validate your circuit design.

---

Notes 36

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: <b>Reversing start/stop motor control circuit</b> Version:	
Schematic	
Parameters	
Motor starts and latches in "Forward"	<input type="checkbox"/>
Motor starts and latches in "Reverse"	<input type="checkbox"/>

file 03151

---

#### Answer 37


The real circuit you build will validate your circuit design.

---

#### Notes 37

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

The two diodes in this circuit are a matter of necessity: getting the circuit to work with only two sets of switch contacts per relay. Ideally, each relay would be 3PDT with separate contact sets for latching, interlocking, and motor power. To use a DPDT relay requires that one of these contact sets do double-duty. In this case, one of the contact sets on each relay handling power to the motor must also handle the job of seal-in (latching). Without the diodes in place, both relays chatter when either motion button is pressed. This is because both relay coils receive power: one coil directly through the switch; the other through the same switch, back through the motor, and then through the seal-in (latching) connection. The diodes prevent this "feed-through" to the other relay coil from happening, without interfering with the normal latching function.
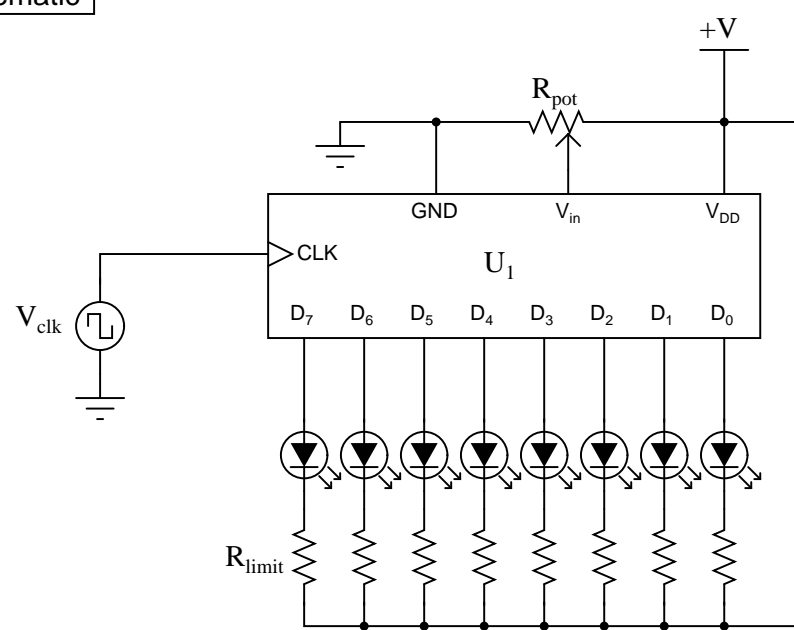
<b>Competency: Analog-digital converter IC</b>	<b>Version:</b>						
<div style="border: 1px solid black; padding: 2px; display: inline-block;"><b>Description</b></div> <p style="margin-top: 10px; text-align: center;">Demonstrate the operation of an analog-to-digital converter integrated circuit, using a potentiometer as the variable input signal source.</p>							
<div style="border: 1px solid black; padding: 2px; display: inline-block;"><b>Schematic</b></div> 							
<div style="border: 1px solid black; padding: 2px; display: inline-block;"><b>Parameters</b></div> <table style="width: 100%; margin-top: 10px;"><thead><tr><th></th><th style="text-align: center;">Predicted</th><th style="text-align: center;">Measured</th></tr></thead><tbody><tr><td style="vertical-align: middle;"><math>V_{\text{resolution}}</math></td><td style="border: 1px solid black; width: 80px; height: 25px;"></td><td style="border: 1px solid black; width: 80px; height: 25px;"></td></tr></tbody></table>			Predicted	Measured	$V_{\text{resolution}}$		
	Predicted	Measured					
$V_{\text{resolution}}$							

---

**Answer 38**

Use circuit simulation software to verify your predicted and actual truth tables.

---

**Notes 38**

In this activity, students are asked to figure out the details of configuring the ADC: what power supply voltage to use, what resistor values, etc. The best source for this information is the ADC's datasheet!


For those students who have trouble figuring out how to calculate resolution, I recommend the following formula:

$$V_{resolution} = \frac{V_{range}}{2^n - 1}$$

Where,

$V_{range}$  = "Span" of analog voltage input (how many volts of range it has from 00000000 to 11111111)

$n$  = Number of output bits for the ADC
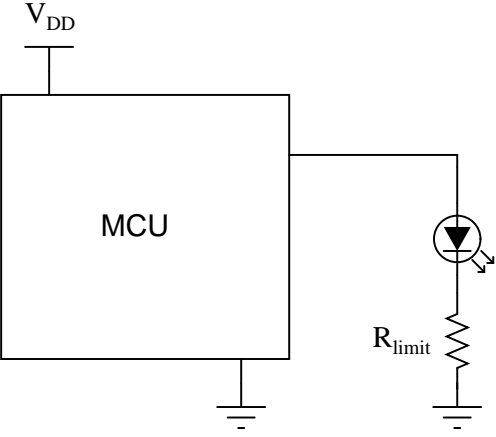
<b>Competency: Light flasher using MCU</b>		Version:
<b>Schematic</b>		
		
<b>Given conditions</b>		
$t_{on} =$	$t_{off} =$	
<b>Program</b>		

file 03152

---

Answer 39


Use circuit simulation software to verify your predicted and actual truth tables.

---

Notes 39

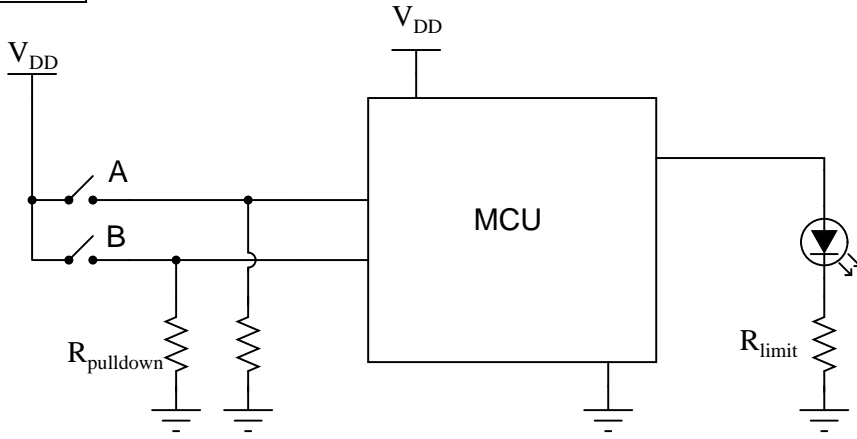Here, I let students choose appropriate values for  $R_{pulldown}$  and  $R_{limit}$ , rather than specify them as given conditions.



Competency: <b>Logic function using MCU</b>		Version:
<b>Description</b>		
Program a microcontroller (MCU) to emulate a two-input logic gate of the instructor's choosing.		
<b>Emulated function</b>		
<i>(instructor checks one box)</i>		
<input type="checkbox"/> AND	<input type="checkbox"/> OR	<input type="checkbox"/> NAND <input type="checkbox"/> NOR
<b>Schematic</b>		
		
<b>Program</b>		

file 03150

---

Answer 40


Use circuit simulation software to verify your predicted and actual truth tables.

---

Notes 40

Here, I let students choose appropriate values for  $R_{pulldown}$  and  $R_{limit}$ , rather than specify them as given conditions.

Question 41

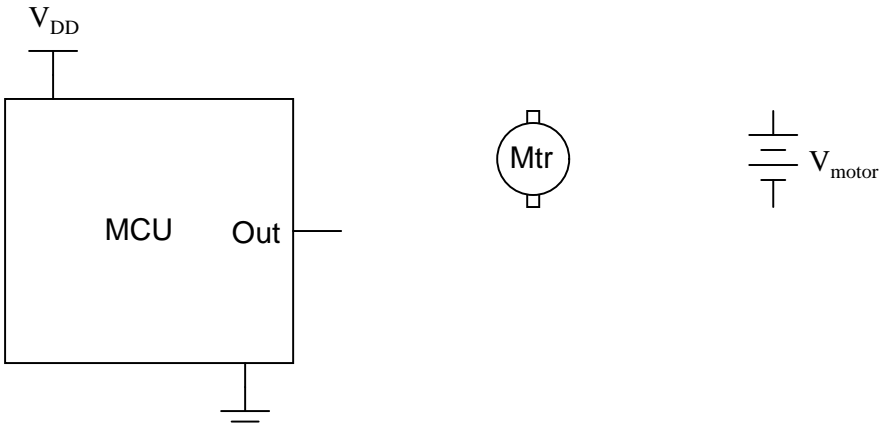Competency: <b>Motor speed control using MCU</b>	Version:
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Description</div> <p style="text-align: center; margin-top: 10px;">Use the Pulse-Width Modulation (PWM) capability of a microcontroller to set the speed of a DC motor.</p>	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div>  <p>The schematic diagram illustrates the connection of a microcontroller unit (MCU) to a DC motor (Mtr). The MCU is represented by a rectangular block with a power supply input <math>V_{DD}</math> at the top and a ground connection at the bottom. An output pin labeled 'Out' is connected to the motor. The motor is represented by a circle with 'Mtr' inside. It is also connected to a separate power supply <math>V_{motor}</math> and ground.</p>	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <p style="margin-top: 10px;"><math>V_{motor} =</math>                      D (duty cycle) =</p>	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Program</div> <div style="border: 1px solid black; height: 150px; width: 100%; margin-top: 5px;"></div>	

file 04018

---


Answer 41

Use circuit simulation software to verify your predicted and actual truth tables.

---

Notes 41

Here, I let students design and build their own transistor drive circuit to interpose between the MCU and the DC motor.

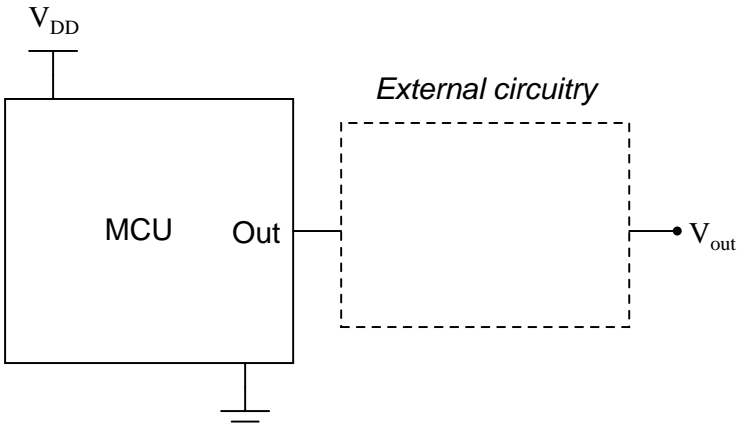Competency: <b>MCU analog voltage output</b>		Version:
Description		
Generate an analog output voltage using an MCU.		
Schematic		
		
Given conditions		
$V_{out} =$		
Program		

file 04019

---

Answer 42

Use circuit simulation software to verify your predicted and actual truth tables.

---

Notes 42

One method that is convenient for generating an analog output voltage with many microcontrollers is to program the MCU to generate a PWM output, then build an analog filter circuit to capture just the average DC value of that PWM waveform.

(Template)

Competency:		Version:	
Schematic			
Given conditions			
Parameters			
Predicted		Measured	
<div></div>	<div></div>	<div></div>	<div></div>
<div></div>	<div></div>	<div></div>	<div></div>

---

Answer 43

Here, you would indicate where or how to obtain answers for the requested parameters, but not actually give the figures. My stock answer here is “use circuit simulation software” (Spice, Multisim, etc.).

---

Notes 43

Any relevant notes for the assessment activity go here.