

## Design Project: Audio tone control

This worksheet and all related files are licensed under the Creative Commons Attribution License, version 1.0. To view a copy of this license, visit <http://creativecommons.org/licenses/by/1.0/>, or send a letter to Creative Commons, 559 Nathan Abbott Way, Stanford, California 94305, USA. The terms and conditions of this license allow for free copying, distribution, and/or modification of all licensed works by the general public.

---

Your project is to research the schematic diagram and component values for an audio tone control circuit (bass and treble controls), then build one in a nice enclosure. There are plenty of resources on the internet for you to research, as well as many good textbooks on audio circuitry for you to read. If you are a musician, you may want to consider building a tone control for your electric instrument (electric guitar, electric violin or viola, etc.). If you like to listen to portable music devices, you may want to consider building a stereo tone control (using double-ganged potentiometers so both channels have the same tone) for your portable music player.


Deadlines (set by instructor):

- Project design completed:
- Components purchased:
- Working prototype:
- Finished system:
- Full documentation:

---
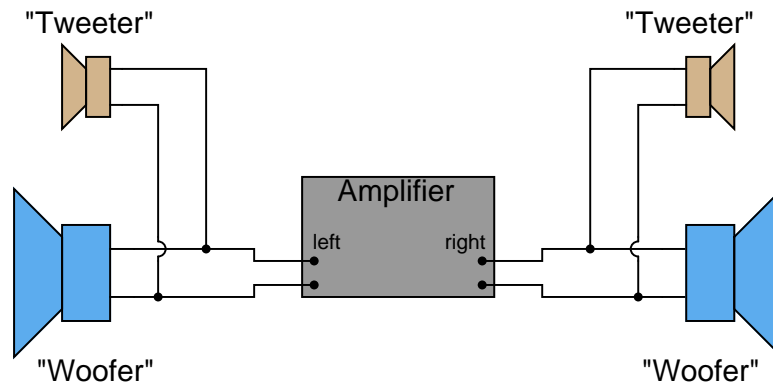
### Question 1


Suppose you were installing a high-power stereo system in your car, and you wanted to build a simple filter for the "tweeter" (high-frequency) speakers so that no bass (low-frequency) power is wasted in these speakers. Modify the schematic diagram below with a filter circuit of your choice:



Hint: this only requires a single component per tweeter!  
[file 00613](#)

---

### Answer 1

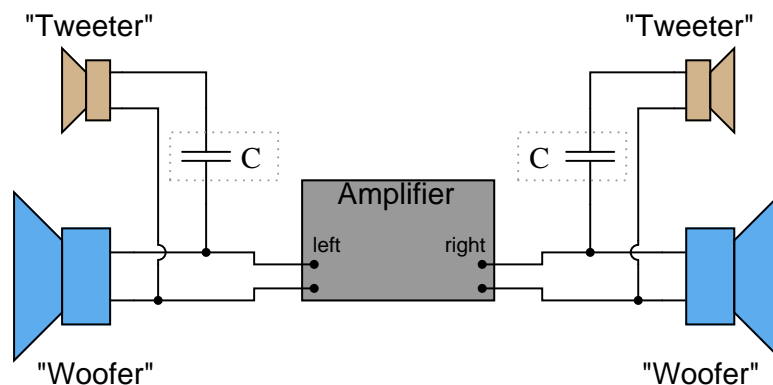

Follow-up question: what type of capacitor would you recommend using in this application (electrolytic, mylar, ceramic, etc.)? Why?

---

### Notes 1


Ask your students to describe what type of filter circuit a series-connected capacitor forms: low-pass, high-pass, band-pass, or band-stop? Discuss how the name of this filter should describe its intended function in the sound system.

Regarding the follow-up question, it is important for students to recognize the practical limitations of certain capacitor types. One thing is for sure, ordinary (polarized) electrolytic capacitors will not function properly in an application like this!

---
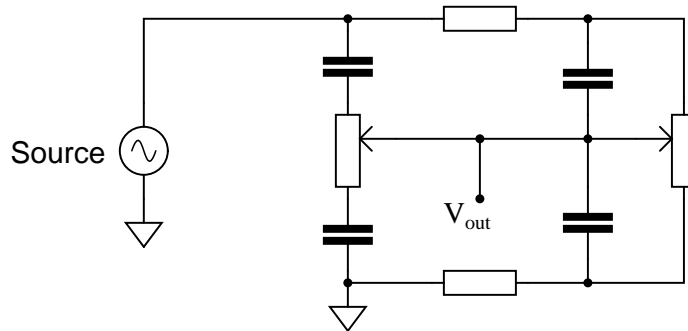
### Question 2

Examine the following schematic diagram for an audio tone control circuit:




Determine which potentiometer controls the bass (low frequency) tones and which controls the treble (high frequency) tones, and explain how you made those determinations.

file 03506

---

### Answer 2

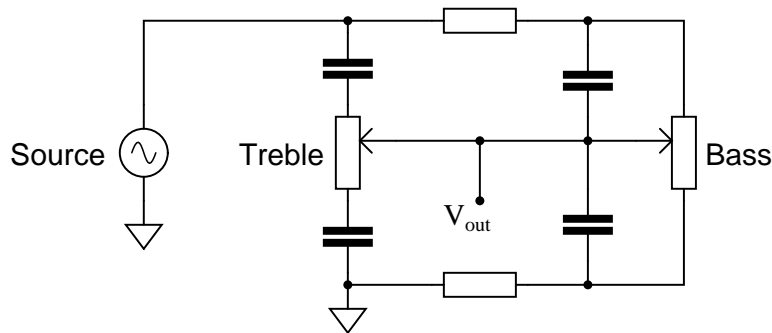

---

### Notes 2

The most important answer to this question is *how* your students arrived at the correct potentiometer identifications. If none of your students were able to figure out how to identify the potentiometers, give them this tip: use the *superposition theorem* to analyze the response of this circuit to both low-frequency signals and high-frequency signals. Assume that for bass tones the capacitors are opaque ( $Z = \infty$ ) and that for treble tones they are transparent ( $Z = 0$ ). The answers should be clear if they follow this technique.

This general problem-solving technique – analyzing two or more “extreme” scenarios to compare the results – is an important one for your students to become familiar with. It is extremely helpful in the analysis of filter circuits!

Question 3

Competency: <b>Tone balance control circuit</b>		Version:																																																																						
Schematic																																																																								
Given conditions																																																																								
$L_1 =$	$C_1 =$	$R_{pot1} = R_{pot2} =$																																																																						
$R_1 = R_2 =$		$Z_{headphones} =$																																																																						
(Use audio source for signal, voltage adjusted for ample volume)																																																																								
Parameters																																																																								
	Predicted	Measured																																																																						
Bass control																																																																								
Treble control																																																																								
(Identify which pot is which)																																																																								
<p style="text-align: center;"><b>Frequency response</b> (maximum bass, minimum treble)</p> <div style="display: flex; align-items: center;"> <div style="margin-right: 10px;"><math>V_{out}</math></div> <table border="1" style="border-collapse: collapse; text-align: center;"> <tr><td></td><td></td><td></td><td></td><td></td><td></td><td></td></tr> <tr><td></td><td></td><td></td><td></td><td></td><td></td><td></td></tr> <tr><td></td><td></td><td></td><td></td><td></td><td></td><td></td></tr> <tr><td></td><td></td><td></td><td></td><td></td><td></td><td></td></tr> <tr><td></td><td></td><td></td><td></td><td></td><td></td><td></td></tr> </table> </div> <p style="text-align: center;"><math>f</math></p>																																					<p style="text-align: center;"><b>Frequency response</b> (minimum bass, maximum treble)</p> <div style="display: flex; align-items: center;"> <div style="margin-right: 10px;"><math>V_{out}</math></div> <table border="1" style="border-collapse: collapse; text-align: center;"> <tr><td></td><td></td><td></td><td></td><td></td><td></td><td></td></tr> <tr><td></td><td></td><td></td><td></td><td></td><td></td><td></td></tr> <tr><td></td><td></td><td></td><td></td><td></td><td></td><td></td></tr> <tr><td></td><td></td><td></td><td></td><td></td><td></td><td></td></tr> <tr><td></td><td></td><td></td><td></td><td></td><td></td><td></td></tr> </table> </div> <p style="text-align: center;"><math>f</math></p>																																			

Note: when testing the frequency response of the tone control circuit, you may need to replace the headphones with a non-inductive resistor of equivalent impedance, and measure  $V_{out}$  across it.  
[file 02022](#)

---

### Answer 3

Use circuit simulation software to verify your predicted and measured parameter values.

---

### Notes 3

A good source of audio signal is the headphone output jack of almost any radio, media player, or other portable audio device. Students like being able to do a lab exercise that directly relates to technology they're already familiar with.

The higher-impedance the headphones are, the better this circuit works, since the combination of potentiometers and mixing resistors tends to result in a relatively high output impedance. I have used cheap headphones (32 ohm) with some success, given the following component values:

- $C_1 = 0.1 \mu\text{F}$
- $L_1 = 200 \text{ mH}$  (actually two 100 mH inductors in series)
- $R_1 = R_2 = 1 \text{ k}\Omega$
- $R_{pot1} = R_{pot2} = 10 \text{ k}\Omega$

Some students with limited hearing range have difficulty detecting the changes in tone using 10 k $\Omega$  potentiometers. You may wish to use 100 k $\Omega$  potentiometers instead for added attenuation. Operating such a circuit is akin to operating a water faucet with "hot" and "cold" water valves: the two settings together determine temperature *and* flow (tone and volume, respectively, for the metaphorically challenged).

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

If you plan to use this exercise as a troubleshooting assessment, I recommend *against* inducing the following component failures, as they are difficult to detect when the signal source is music rather than a constant tone of known frequency and amplitude:

- Shorted capacitor ( $C_1$ )
- Shorted inductor ( $L_1$ )
- Shorted fixed-value resistors ( $R_1$  or  $R_2$ )

Question 4

Competency: <b>Tone balance control circuit</b>		Version:											
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="text-align: center; padding: 20px;"> </div>													
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <div style="padding: 10px;"> <math>L_1 =</math>                      <math>C_1 =</math>                      <math>R_{pot1} = R_{pot2} =</math>  <math>R_1 = R_2 =</math>                      <math>Z_{speaker} =</math>                      <math>T_1 =</math>              (Use audio source for signal, voltage adjusted for ample volume)           </div>													
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <div style="padding: 10px;"> <table style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="width: 30%;"></th> <th style="width: 20%; text-align: center;">Predicted</th> <th style="width: 20%; text-align: center;">Measured</th> <th style="width: 30%;"></th> </tr> </thead> <tbody> <tr> <td>Bass control</td> <td style="border: 1px solid black; height: 30px;"></td> <td style="border: 1px solid black; height: 30px;"></td> <td rowspan="2" style="vertical-align: middle; padding-left: 10px;">(Identify which pot is which)</td> </tr> <tr> <td>Treble control</td> <td style="border: 1px solid black; height: 30px;"></td> <td style="border: 1px solid black; height: 30px;"></td> </tr> </tbody> </table> <div style="display: flex; justify-content: space-around; margin-top: 20px;"> <div style="text-align: center;"> <p><b>Frequency response</b> (maximum bass, minimum treble)</p> <div style="display: flex; align-items: center;"> <div style="margin-right: 10px;"><math>V_{out}</math></div> <div style="border: 1px solid black; width: 200px; height: 100px; position: relative;"> <!-- Grid lines --> </div> </div> <p style="margin-top: 10px;"><math>f</math></p> </div> <div style="text-align: center;"> <p><b>Frequency response</b> (minimum bass, maximum treble)</p> <div style="display: flex; align-items: center;"> <div style="margin-right: 10px;"><math>V_{out}</math></div> <div style="border: 1px solid black; width: 200px; height: 100px; position: relative;"> <!-- Grid lines --> </div> </div> <p style="margin-top: 10px;"><math>f</math></p> </div> </div> </div>				Predicted	Measured		Bass control			(Identify which pot is which)	Treble control		
	Predicted	Measured											
Bass control			(Identify which pot is which)										
Treble control													

Note: when testing the frequency response of the tone control circuit, you may need to replace the transformer/speaker assembly with a non-inductive resistor of equivalent impedance, and measure  $V_{out}$  across it.

file 02023

---

#### Answer 4

Use circuit simulation software to verify your predicted and measured parameter values.

---

#### Notes 4

A good source of audio signal is the headphone output jack of almost any radio, media player, or other portable audio device. Students like being able to do a lab exercise that directly relates to technology they're already familiar with.

I have experienced good success with the following component values:

- $C_1 = 0.1 \mu\text{F}$
- $L_1 = 200 \text{ mH}$  (actually two 100 mH inductors in series)
- $R_1 = R_2 = 1 \text{ k}\Omega$
- $T_1 = 1000:8 \text{ ohm}$  audio output transformer
- $R_{pot} = R_{pot2} = 10 \text{ k}\Omega$
- Speaker = small  $8 \Omega$  unit (salvaged from an old clock radio or other inexpensive audio device)

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.