

Performance-based assessments for semiconductor circuit competencies

This worksheet and all related files are licensed under the Creative Commons Attribution License, version 1.0. To view a copy of this license, visit <http://creativecommons.org/licenses/by/1.0/>, or send a letter to Creative Commons, 559 Nathan Abbott Way, Stanford, California 94305, USA. The terms and conditions of this license allow for free copying, distribution, and/or modification of all licensed works by the general public.

The purpose of these assessments is for instructors to accurately measure the learning of their electronics students, in a way that melds theoretical knowledge with hands-on application. In each assessment, students are asked to predict the behavior of a circuit from a schematic diagram and component values, then they build that circuit and measure its real behavior. If the behavior matches the predictions, the student then simulates the circuit on computer and presents the three sets of values to the instructor. If not, then the student then must correct the error(s) and once again compare measurements to predictions. Grades are based on the number of attempts required before all predictions match their respective measurements.

You will notice that no component values are given in this worksheet. The *instructor* chooses component values suitable for the students' parts collections, and ideally chooses different values for each student so that no two students are analyzing and building the exact same circuit. These component values may be hand-written on the assessment sheet, printed on a separate page, or incorporated into the document by editing the graphic image.

This is the procedure I envision for managing such assessments:

1. The instructor hands out individualized assessment sheets to each student.
2. Each student predicts their circuit's behavior at their desks using pencil, paper, and calculator (if appropriate).
3. Each student builds their circuit at their desk, under such conditions that it is impossible for them to verify their predictions using test equipment. Usually this will mean the use of a multimeter only (for measuring component values), but in some cases even the use of a multimeter would not be appropriate.
4. When ready, each student brings their predictions and completed circuit up to the instructor's desk, where any necessary test equipment is already set up to operate and test the circuit. There, the student sets up their circuit and takes measurements to compare with predictions.
5. If any measurement fails to match its corresponding prediction, the student goes back to their own desk with their circuit and their predictions in hand. There, the student tries to figure out where the error is and how to correct it.
6. Students repeat these steps as many times as necessary to achieve correlation between all predictions and measurements. The instructor's task is to count the number of attempts necessary to achieve this, which will become the basis for a percentage grade.
7. (OPTIONAL) As a final verification, each student simulates the same circuit on computer, using circuit simulation software (Spice, Multisim, etc.) and presenting the results to the instructor as a final pass/fail check.


These assessments more closely mimic real-world work conditions than traditional written exams:

- Students cannot pass such assessments only knowing circuit theory or only having hands-on construction and testing skills – they must be proficient at both.
- Students do not receive the “authoritative answers” from the instructor. Rather, they learn to validate their answers through real circuit measurements.
- Just as on the job, the work isn't complete until *all errors* are corrected.
- Students must recognize and correct their own errors, rather than having someone else do it for them.
- Students must be fully prepared on exam days, bringing not only their calculator and notes, but also their tools, breadboard, and circuit components.

Instructors may elect to reveal the assessments before test day, and even use them as preparatory labwork and/or discussion questions. Remember that there is absolutely nothing wrong with “teaching to

the test” *so long as the test is valid*. Normally, it is bad to reveal test material in detail prior to test day, lest students merely memorize responses in advance. With performance-based assessments, however, there is no way to pass without truly understanding the subject(s).

Question 1

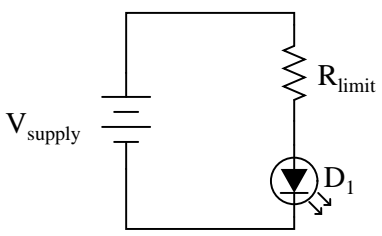Competency: LED current limiting		Version:	
Schematic			
			
Given conditions			
$V_{\text{supply}} =$	$V_{\text{forward (LED)}} =$	$I_{\text{forward(LED)}} =$	
Parameters			
Given	Predicted	Measured	
$V_{\text{supply}} =$ <input style="width: 100px;" type="text"/>	$V_{R_{\text{limit}}}$ <input style="width: 100px;" type="text"/>	<input style="width: 100px;" type="text"/>	
	V_{D1} <input style="width: 100px;" type="text"/>	<input style="width: 100px;" type="text"/>	
	I_{D1} <input style="width: 100px;" type="text"/>	<input style="width: 100px;" type="text"/>	
Analysis			
<p style="text-align: center;">Show how you calculated the appropriate value for R_{limit}</p> <p style="text-align: center;">Draw the directions of both electron and conventional current</p>			
Fault analysis			
<p>Suppose component <input style="width: 50px;" type="text"/> fails <input type="checkbox"/> open <input type="checkbox"/> other _____</p> <p><input type="checkbox"/> shorted</p> <p><i>What will happen in the circuit?</i></p>			

file 04075

Answer 1

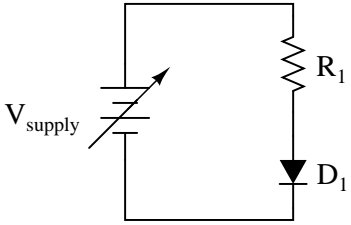
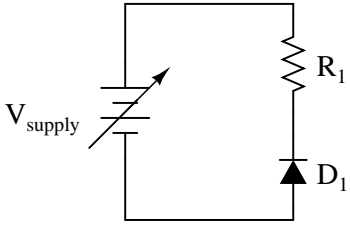
Use circuit simulation software to verify your predicted and measured parameter values.

Notes 1

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Have students calculate the necessary current-limiting resistor for their LEDs based on measured values of $V_{forward}$ for the LED (using a multimeter with a "diode-check" function). Let students research the typical forward current for their LED from an appropriate datasheet. Any LED should suffice for this activity.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Question 2

Competency: Rectifying diode behavior		Version:																																									
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="display: flex; justify-content: space-around; align-items: center; padding: 10px;"> <div style="text-align: center;"> <p><i>Forward-biased</i></p>  </div> <div style="text-align: center;"> <p><i>Reverse-biased</i></p>  </div> </div>																																											
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <p>$V_{\text{supply}} =$ (see multiple values given below)</p> <p>$R_1 =$</p>																																											
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <div style="display: flex;"> <div style="flex: 1;"> <p><i>Forward-biased</i></p> <table style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="width: 30%;"></th> <th style="width: 35%; text-align: center;">Given</th> <th style="width: 15%; text-align: center;">Predicted</th> <th style="width: 20%; text-align: center;">Measured</th> </tr> </thead> <tbody> <tr> <td>$V_{\text{supply}} =$</td> <td><input style="width: 100%;" type="text"/></td> <td>V_{R1} <input style="width: 100%;" type="text"/></td> <td><input style="width: 100%;" type="text"/></td> </tr> <tr> <td></td> <td></td> <td>V_{D1} <input style="width: 100%;" type="text"/></td> <td><input style="width: 100%;" type="text"/></td> </tr> <tr> <td>$V_{\text{supply}} =$</td> <td><input style="width: 100%;" type="text"/></td> <td>V_{R1} <input style="width: 100%;" type="text"/></td> <td><input style="width: 100%;" type="text"/></td> </tr> <tr> <td></td> <td></td> <td>V_{D1} <input style="width: 100%;" type="text"/></td> <td><input style="width: 100%;" type="text"/></td> </tr> </tbody> </table> </div> <div style="flex: 1;"> <p><i>Reverse-biased</i></p> <table style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="width: 30%;"></th> <th style="width: 35%; text-align: center;">Given</th> <th style="width: 15%; text-align: center;">Predicted</th> <th style="width: 20%; text-align: center;">Measured</th> </tr> </thead> <tbody> <tr> <td>$V_{\text{supply}} =$</td> <td><input style="width: 100%;" type="text"/></td> <td>V_{R1} <input style="width: 100%;" type="text"/></td> <td><input style="width: 100%;" type="text"/></td> </tr> <tr> <td></td> <td></td> <td>V_{D1} <input style="width: 100%;" type="text"/></td> <td><input style="width: 100%;" type="text"/></td> </tr> <tr> <td>$V_{\text{supply}} =$</td> <td><input style="width: 100%;" type="text"/></td> <td>V_{R1} <input style="width: 100%;" type="text"/></td> <td><input style="width: 100%;" type="text"/></td> </tr> <tr> <td></td> <td></td> <td>V_{D1} <input style="width: 100%;" type="text"/></td> <td><input style="width: 100%;" type="text"/></td> </tr> </tbody> </table> </div> </div>					Given	Predicted	Measured	$V_{\text{supply}} =$	<input style="width: 100%;" type="text"/>	V_{R1} <input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>			V_{D1} <input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>	$V_{\text{supply}} =$	<input style="width: 100%;" type="text"/>	V_{R1} <input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>			V_{D1} <input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>		Given	Predicted	Measured	$V_{\text{supply}} =$	<input style="width: 100%;" type="text"/>	V_{R1} <input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>			V_{D1} <input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>	$V_{\text{supply}} =$	<input style="width: 100%;" type="text"/>	V_{R1} <input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>			V_{D1} <input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>
	Given	Predicted	Measured																																								
$V_{\text{supply}} =$	<input style="width: 100%;" type="text"/>	V_{R1} <input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>																																								
		V_{D1} <input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>																																								
$V_{\text{supply}} =$	<input style="width: 100%;" type="text"/>	V_{R1} <input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>																																								
		V_{D1} <input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>																																								
	Given	Predicted	Measured																																								
$V_{\text{supply}} =$	<input style="width: 100%;" type="text"/>	V_{R1} <input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>																																								
		V_{D1} <input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>																																								
$V_{\text{supply}} =$	<input style="width: 100%;" type="text"/>	V_{R1} <input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>																																								
		V_{D1} <input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>																																								

file 01940

Answer 2

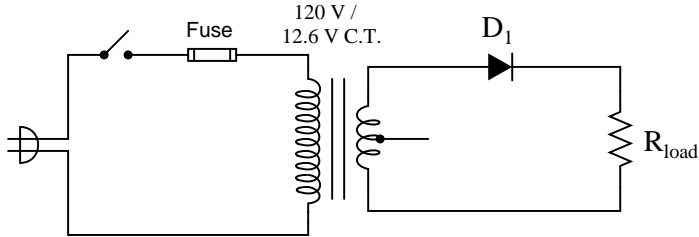
Use circuit simulation software to verify your predicted and measured parameter values.

Notes 2

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k Ω and 100 k Ω (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k 47k, 68k, etc.). I recommend using one of the 1N400X series of rectifying diodes for their low cost and ruggedness.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Question 3

Competency: Half-wave rectifier		Version:
Schematic		
		
Given conditions		
$V_{\text{secondary}} =$ (VAC RMS)		$R_{\text{load}} =$
Parameters		
	Predicted	Measured
$V_{\text{load(DC)}}$		
(Approximate only)		
V_{ripple}		
f_{ripple}		
Fault analysis		
Suppose component fails		
<div style="display: flex; justify-content: flex-end; align-items: center;"> <input type="checkbox"/> open <input type="checkbox"/> other _____ <input type="checkbox"/> shorted </div>		
<i>What will happen in the circuit?</i>		

file 01941

Answer 3

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 3

I recommend using 1N400X series rectifying diodes for all rectifier circuit designs. Make sure that the resistance value you specify for your load is not so low that the resistor's power dissipation is exceeded.

Watch out for harmonics in the power line voltage creating problems with RMS/peak voltage relationships. If this is a problem, try using a ferroresonant transformer to filter out some of the harmonic content. *Do not* try to use a sine-wave signal generator as an alternate source of AC power, because most signal generators have internal impedances that are much too high for such a task.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Question 4

Competency: Full-wave center-tap rectifier		Version:
Schematic		
Given conditions		
$V_{\text{secondary}} =$ (VAC RMS)		$R_{\text{load}} =$
Parameters		
	Predicted	Measured
$V_{\text{load(DC)}}$		
(Approximate only)		
V_{ripple}		
f_{ripple}		
Fault analysis		
Suppose component fails <div style="display: inline-block; vertical-align: middle; margin-left: 10px;"> <input type="checkbox"/> open <input type="checkbox"/> other _____ <input type="checkbox"/> shorted </div>		
<i>What will happen in the circuit?</i>		

file 01942

Answer 4


Use circuit simulation software to verify your predicted and measured parameter values.

Notes 4

I recommend using 1N400X series rectifying diodes for all rectifier circuit designs. Make sure that the resistance value you specify for your load is not so low that the resistor's power dissipation is exceeded.

Watch out for harmonics in the power line voltage creating problems with RMS/peak voltage relationships. If this is a problem, try using a ferroresonant transformer to filter out some of the harmonic content. *Do not* try to use a sine-wave signal generator as an alternate source of AC power, because most signal generators have internal impedances that are much too high for such a task.

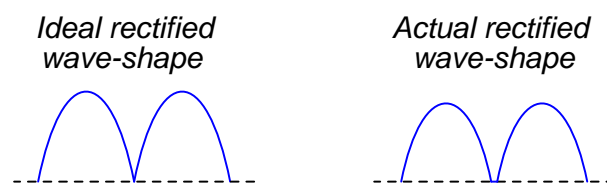It is difficult to precisely calculate the DC load voltage from a rectifier circuit such as this when the transformer secondary voltage is relatively low. The diodes' forward voltage drop essentially distorts the rectified waveform so that it is not quite the same as what you would expect a full-wave rectified waveform to be:




Accurate calculation of the actual rectified wave-shape's average voltage value requires integration of the half-sine peak over a period less than π radians, which may very well be beyond the capabilities of your students. This is why I request approximations only on this parameter.

One approximation that works fairly well is to take the AC RMS voltage (in this case, half of the secondary winding's output, since this is a center-tap design), convert it to *average* voltage (multiply by 0.9), and then subtract the forward junction voltage lost by the diode (0.7 volts typical for silicon).

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Question 5

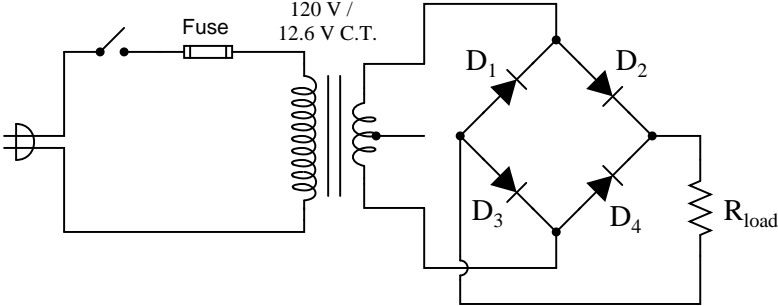Competency: Full-wave bridge rectifier		Version:
Schematic		
		
Given conditions		
$V_{\text{secondary}} =$ (VAC RMS)		$R_{\text{load}} =$
Parameters		
	Predicted	Measured
$V_{\text{load(DC)}}$		
(Approximate only)		
V_{ripple}		
f_{ripple}		
Fault analysis		
Suppose component fails		
<div style="display: flex; justify-content: flex-end; align-items: center;"> <input type="checkbox"/> open <input type="checkbox"/> other _____ <input type="checkbox"/> shorted </div>		
<i>What will happen in the circuit?</i>		

file 01943

Answer 5


Use circuit simulation software to verify your predicted and measured parameter values.

Notes 5

I recommend using 1N400X series rectifying diodes for all rectifier circuit designs. Make sure that the resistance value you specify for your load is not so low that the resistor's power dissipation is exceeded.

Watch out for harmonics in the power line voltage creating problems with RMS/peak voltage relationships. If this is a problem, try using a ferroresonant transformer to filter out some of the harmonic content. *Do not* try to use a sine-wave signal generator as an alternate source of AC power, because most signal generators have internal impedances that are much too high for such a task.

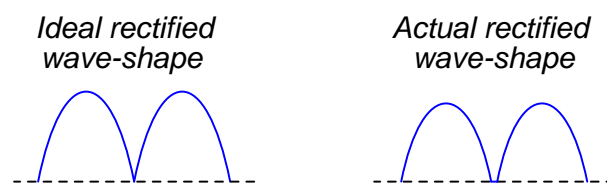It is difficult to precisely calculate the DC load voltage from a rectifier circuit such as this when the transformer secondary voltage is relatively low. The diodes' forward voltage drop essentially distorts the rectified waveform so that it is not quite the same as what you would expect a full-wave rectified waveform to be:




Accurate calculation of the actual rectified wave-shape's average voltage value requires integration of the half-sine peak over a period less than π radians, which may very well be beyond the capabilities of your students. This is why I request approximations only on this parameter.

One approximation that works fairly well is to take the AC RMS voltage, convert it to *average* voltage (multiply by 0.9), and then subtract the total forward junction voltage lost by the diode (0.7 volts per diode typical for silicon, for a total of 1.4 volts).

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Question 6

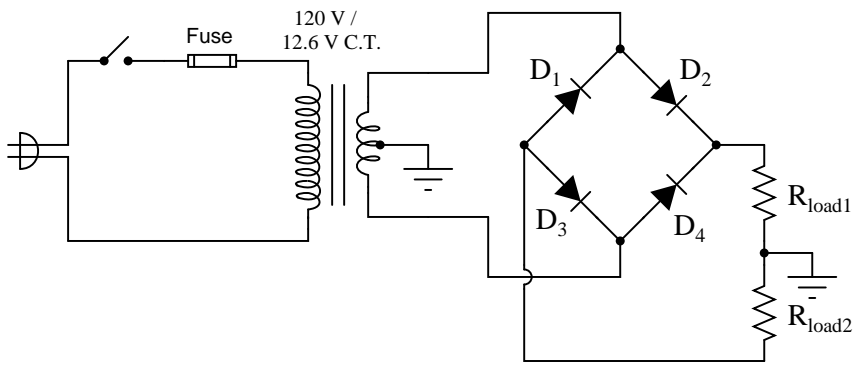Competency: Full-wave center-tap bridge rectifier Version:																																	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> 																																	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <div style="display: flex; justify-content: space-around; align-items: center; margin-top: 10px;"> <div> $V_{\text{secondary}} =$ (VAC RMS) </div> <div> $R_{\text{load1}} = R_{\text{load2}} =$ </div> </div>																																	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; border-collapse: collapse; margin-top: 10px;"> <thead> <tr> <th style="width: 15%;"></th> <th style="width: 20%; text-align: center;">Predicted</th> <th style="width: 20%; text-align: center;">Measured</th> <th style="width: 45%;"></th> </tr> </thead> <tbody> <tr> <td>$V_{\text{load(DC)}}$</td> <td><input style="width: 100%;" type="text"/></td> <td><input style="width: 100%;" type="text"/></td> <td rowspan="3" style="vertical-align: middle; padding-left: 10px;"> <div style="display: flex; align-items: center;"> <div style="font-size: 3em; margin-right: 5px;">}</div> <div>For R_{load1}</div> </div> </td> </tr> <tr> <td>V_{ripple}</td> <td><input style="width: 100%;" type="text"/></td> <td><input style="width: 100%;" type="text"/></td> </tr> <tr> <td>f_{ripple}</td> <td><input style="width: 100%;" type="text"/></td> <td><input style="width: 100%;" type="text"/></td> </tr> <tr> <td></td> <td></td> <td></td> <td></td> </tr> <tr> <td></td> <td></td> <td></td> <td></td> </tr> <tr> <td>$V_{\text{load(DC)}}$</td> <td><input style="width: 100%;" type="text"/></td> <td><input style="width: 100%;" type="text"/></td> <td rowspan="3" style="vertical-align: middle; padding-left: 10px;"> <div style="display: flex; align-items: center;"> <div style="font-size: 3em; margin-right: 5px;">}</div> <div>For R_{load2}</div> </div> </td> </tr> <tr> <td>V_{ripple}</td> <td><input style="width: 100%;" type="text"/></td> <td><input style="width: 100%;" type="text"/></td> </tr> <tr> <td>f_{ripple}</td> <td><input style="width: 100%;" type="text"/></td> <td><input style="width: 100%;" type="text"/></td> </tr> </tbody> </table>			Predicted	Measured		$V_{\text{load(DC)}}$	<input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>	<div style="display: flex; align-items: center;"> <div style="font-size: 3em; margin-right: 5px;">}</div> <div>For R_{load1}</div> </div>	V_{ripple}	<input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>	f_{ripple}	<input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>									$V_{\text{load(DC)}}$	<input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>	<div style="display: flex; align-items: center;"> <div style="font-size: 3em; margin-right: 5px;">}</div> <div>For R_{load2}</div> </div>	V_{ripple}	<input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>	f_{ripple}	<input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>
	Predicted	Measured																															
$V_{\text{load(DC)}}$	<input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>	<div style="display: flex; align-items: center;"> <div style="font-size: 3em; margin-right: 5px;">}</div> <div>For R_{load1}</div> </div>																														
V_{ripple}	<input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>																															
f_{ripple}	<input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>																															
$V_{\text{load(DC)}}$	<input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>	<div style="display: flex; align-items: center;"> <div style="font-size: 3em; margin-right: 5px;">}</div> <div>For R_{load2}</div> </div>																														
V_{ripple}	<input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>																															
f_{ripple}	<input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>																															

file 01944

Answer 6


Use circuit simulation software to verify your predicted and measured parameter values.

Notes 6

I recommend using 1N400X series rectifying diodes for all rectifier circuit designs. Make sure that the resistance value you specify for your load is not so low that the resistor's power dissipation is exceeded.

Watch out for harmonics in the power line voltage creating problems with RMS/peak voltage relationships. If this is a problem, try using a ferroresonant transformer to filter out some of the harmonic content. *Do not* try to use a sine-wave signal generator as an alternate source of AC power, because most signal generators have internal impedances that are much too high for such a task.

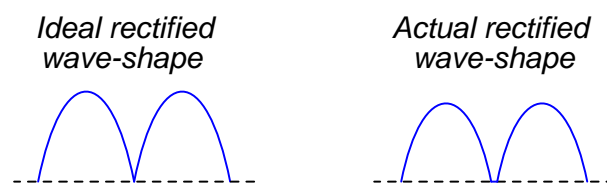It is difficult to precisely calculate the DC load voltage from a rectifier circuit such as this when the transformer secondary voltage is relatively low. The diodes' forward voltage drop essentially distorts the rectified waveform so that it is not quite the same as what you would expect a full-wave rectified waveform to be:



Accurate calculation of the actual rectified wave-shape's average voltage value requires integration of the half-sine peak over a period less than π radians, which may very well be beyond the capabilities of your students. This is why I request approximations only on this parameter.

One approximation that works fairly well is to take the AC RMS voltage (in this case, half of the secondary winding's output, since this is a center-tap design), convert it to *average* voltage (multiply by 0.9), and then subtract the forward junction voltage lost by the diode (0.7 volts typical for silicon).

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Question 7

Competency: Full-wave rectifier circuit	Version:									
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Description</div> <p style="text-align: center; margin-top: 20px;">Design and build a full-wave rectifier circuit of any configuration desired. It simply needs to output DC when energized by an AC source (provided by the instructor).</p>										
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <div style="display: flex; justify-content: space-around; margin-top: 20px;"> $V_{\text{supply(AC)}} =$ $f_{\text{supply}} =$ </div>										
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="height: 200px; border: 1px solid black; margin-top: 5px;"></div>										
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; margin-top: 20px;"> <thead> <tr> <th style="width: 30%;"></th> <th style="width: 35%; text-align: center;">Predicted</th> <th style="width: 35%; text-align: center;">Measured</th> </tr> </thead> <tbody> <tr> <td>V_{ripple}</td> <td style="border: 1px solid black; height: 25px;"></td> <td style="border: 1px solid black; height: 25px;"></td> </tr> <tr> <td>f_{ripple}</td> <td style="border: 1px solid black; height: 25px;"></td> <td style="border: 1px solid black; height: 25px;"></td> </tr> </tbody> </table>			Predicted	Measured	V_{ripple}			f_{ripple}		
	Predicted	Measured								
V_{ripple}										
f_{ripple}										

file 02296

Answer 7

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 7

I recommend using 1N400X series rectifying diodes for all rectifier circuit designs. Make sure that the resistance value you specify for your load is not so low that the resistor's power dissipation is exceeded.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Question 8

Competency: AC-DC power supply circuit	Version:									
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Description</div> <p style="text-align: center; margin-top: 20px;">Build a "brute force" AC-DC power supply circuit, consisting of a step-down transformer, full-wave bridge rectifier, capacitive filter, and load resistor.</p>										
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <div style="display: flex; justify-content: space-around; align-items: center; margin-top: 20px;"> <div>$V_{\text{supply}} =$</div> <div>$C_{\text{filter}} =$</div> <div>$R_{\text{load}} =$</div> </div>										
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="height: 200px; border: 1px solid black; margin-top: 10px;"></div>										
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; margin-top: 20px;"> <thead> <tr> <th style="width: 20%;"></th> <th style="width: 20%; text-align: center;">Predicted</th> <th style="width: 20%; text-align: center;">Measured</th> </tr> </thead> <tbody> <tr> <td>$V_{\text{out(DC)}}$</td> <td style="border: 1px solid black; height: 25px;"></td> <td style="border: 1px solid black; height: 25px;"></td> </tr> <tr> <td>$V_{\text{out(ripple)}}$</td> <td style="border: 1px solid black; height: 25px;"></td> <td style="border: 1px solid black; height: 25px;"></td> </tr> </tbody> </table>			Predicted	Measured	$V_{\text{out(DC)}}$			$V_{\text{out(ripple)}}$		
	Predicted	Measured								
$V_{\text{out(DC)}}$										
$V_{\text{out(ripple)}}$										

file 01622

Answer 8

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 8

Use a Variac at the test bench to provide variable-voltage AC power for the students' power supply circuits.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Question 9

Competency: Zener diode voltage regulator		Version:
Schematic		
Given conditions		
$V_{supply} =$	$V_{zener} =$	$R_{series} =$ $R_{load} =$
Parameters		
	Predicted	Measured
V_{load} (nominal)	<input style="width: 100px; height: 30px;" type="text"/>	<input style="width: 100px; height: 30px;" type="text"/>
V_{supply} (max)	<input style="width: 100px; height: 30px;" type="text"/>	<div style="border: 1px solid black; width: 100px; height: 30px; position: relative;"><div style="position: absolute; top: 0; bottom: 0; left: 0; right: 0;">X</div></div>
V_{supply} (min)	<input style="width: 100px; height: 30px;" type="text"/>	<input style="width: 100px; height: 30px;" type="text"/>
Fault analysis		
Suppose component <input style="width: 50px;" type="text"/> fails <input type="checkbox"/> open <input type="checkbox"/> other _____ <input type="checkbox"/> shorted What will happen in the circuit? 		

The V_{supply} (min) parameter is the minimum voltage setting that V_{supply} may be adjusted to with the regulator circuit maintaining constant load voltage at R_{load} . V_{supply} (max) is the maximum voltage that V_{supply} may be adjusted to without exceeding the zener diode's power rating. V_{load} (nominal) is simply the regulated voltage output of the circuit under normal conditions.

file 01623

Answer 9

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 9

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard load resistor values, all between 1 k Ω and 100 k Ω (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k 47k, 68k, etc.), and let the students determine the proper resistance values for their series dropping resistors.

I recommend specifying a series resistor value (R_{series}) high enough that there will little danger in damaging the zener diode due to excessive supply voltage, but also low enough so that the normal operating current of the zener diode is great enough for it to drop its rated voltage. If R_{series} is too large, the zener diode's current will be too small, resulting in lower than expected voltage drop and poorer regulation (operating near the flatter end of the characteristic curve).

Values I have used with success are as follows:

- $R_{series} = 1 \text{ k}\Omega$
- $R_{load} = 10 \text{ k}\Omega$
- $V_{zener} = 5.1 \text{ volts}$ (diode part number 1N4733)
- $V_{supply} = 12 \text{ volts}$

Measuring the minimum supply voltage is a difficult thing to do, because students must look for a point where the output voltage begins to directly follow the input voltage (going down) instead of holding relatively stable. One interesting way to measure the rate of output voltage change is to set a DMM on the AC voltage setting, then use that to measure V_{load} as V_{supply} is decreased. While turning the voltage adjustment knob on V_{supply} at a steady rate, students will look for an increase in AC voltage (a greater rate of change) at V_{load} . Essentially, what students are looking for is the point where $\frac{dV_{load}}{dV_{supply}}$ begins to increase.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: Half-wave voltage doubler		Version:
Schematic		
Given conditions		
$V_{\text{supply}} =$	$C_1 = C_2 =$	$V_F (\text{typical}) =$
Parameters		
	Predicted	Measured
V_{C1}		
V_{C2}		
V_{out}		
Fault analysis		
Suppose component fails <div style="display: inline-block; vertical-align: middle; margin-left: 10px;"> <input type="checkbox"/> open <input type="checkbox"/> other _____ <input type="checkbox"/> shorted </div>		
<i>What will happen in the circuit?</i>		

Answer 10

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 10

I've used 47 μF electrolytic capacitors and 1N4001 diodes with good success on a 10 volt AC (RMS) power supply. I recommend that students measure their own diodes to determine typical forward voltage (V_F).

Don't forget to mention the polarity sensitivity of these capacitors! Electrolytic capacitors can explode violently if reverse-connected!

Question 11

Competency: Voltage multiplier		Version:
Schematic		
Given conditions		
$V_{\text{supply}} =$ $C_1 = C_2 = C_3 = C_4 = C_5 =$		
Parameters		
	Predicted	Measured
V_{C1}	<input type="text"/>	<input type="text"/>
V_{C2}	<input type="text"/>	<input type="text"/>
V_{C3}	<input type="text"/>	<input type="text"/>
V_{C4}	<input type="text"/>	<input type="text"/>
V_{C5}	<input type="text"/>	<input type="text"/>
$V_{\text{out}} (\text{max})$	<input type="text"/>	<input type="text"/>
<i>Show where to measure greatest DC output voltage</i>		

file 02012

Answer 11

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 11

I've used $0.47\ \mu\text{F}$ capacitors and 1N4001 diodes with good success on a 10 volt AC (RMS) power supply. I recommend using low-capacity capacitors to minimize the amount of stored energy, since voltages in this circuit are potentially hazardous.

Competency: Diode clipper circuit		Version:
Schematic		
Given conditions		
$V_{\text{supply}} =$	$R_1 =$	$V_F (\text{typical}) =$
Parameters		
<div style="display: flex; justify-content: space-around;"> <div style="text-align: center;"> Predicted V_{out} </div> <div style="text-align: center;"> Measured </div> </div>	Input and output waveforms 	
Fault analysis		
Suppose component fails <div style="display: inline-block; vertical-align: middle; margin-left: 10px;"> <input type="checkbox"/> open <input type="checkbox"/> other _____ <input type="checkbox"/> shorted </div> <p><i>What will happen in the circuit?</i></p>		

Answer 12

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 12

Any diodes will work for this, so long as the source frequency is not too high. I recommend students set the volts/division controls on both channels to the exact same range, so that the slope of the clipped wave near zero-crossing may seem to be exactly the same as the slope of the input sine wave at the same points. This makes it absolutely clear that the output waveform is nothing more than the input waveform with the tops and bottoms cut off.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: Diode clipper circuit, adjustable	Version:												
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Schematic</div>													
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Given conditions</div>													
$V_{\text{source}} =$ $C_1 =$ $R_1 =$ $V_F (\text{typical}) =$ $V_{\text{DC}} =$													
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Parameters</div>													
<table style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="width: 10%;"></th> <th style="width: 20%; text-align: center;">Predicted</th> <th style="width: 20%; text-align: center;">Measured</th> <th style="width: 50%;"></th> </tr> </thead> <tbody> <tr> <td>V_{out}</td> <td style="border: 1px solid black; width: 80px; height: 30px;"></td> <td style="border: 1px solid black; width: 80px; height: 30px;"></td> <td>(positive peak)</td> </tr> <tr> <td>V_{out}</td> <td style="border: 1px solid black; width: 80px; height: 30px;"></td> <td style="border: 1px solid black; width: 80px; height: 30px;"></td> <td>(negative peak)</td> </tr> </tbody> </table> <p style="text-align: center; margin-top: 10px;">Input and output waveforms</p> <div style="text-align: center;"> </div>			Predicted	Measured		V_{out}			(positive peak)	V_{out}			(negative peak)
	Predicted	Measured											
V_{out}			(positive peak)										
V_{out}			(negative peak)										

Answer 13

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 13

Any diodes will work for this, so long as the source frequency is not too high.

I have had good success with the following values:

- $V_{source} = 4$ volts (peak)
- $f_{source} = 3$ kHz
- $V_{DC} = 6$ volts
- $C_1 = 0.47 \mu\text{F}$
- $R_1 = 100 \text{ k}\Omega$
- Potentiometer = $10 \text{ k}\Omega$, linear
- D_1 = part number 1N4004 (any 1N400x diode should work)

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: Zener diode clipper circuit		Version:
Schematic		
Given conditions		
$V_{\text{supply}} =$	$R_1 =$	$V_F (\text{typical}) =$
		$V_Z =$
Parameters		
<div style="display: flex; justify-content: space-around;"> <div>Predicted</div> <div>Measured</div> </div> <div style="display: flex; justify-content: space-around; margin-top: 10px;"> <div style="text-align: center;">V_{out}</div> <div style="border: 1px solid black; width: 100px; height: 30px;"></div> <div style="border: 1px solid black; width: 100px; height: 30px;"></div> </div>	Input and output waveforms 	
Fault analysis		
Suppose component fails <div style="display: flex; justify-content: flex-end; align-items: center; margin-top: 5px;"> <input type="checkbox"/> open <input type="checkbox"/> other _____ <input type="checkbox"/> shorted </div> <p><i>What will happen in the circuit?</i></p>		



Answer 14

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 14

Be sure to use zener diodes with reasonably low breakdown voltages, and specify the source voltage accordingly.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

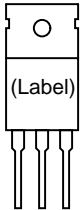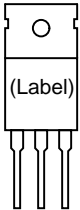Competency: BJT terminal identification		Version:
Description		
Identify the terminals (emitter, base, and collector) of a bipolar junction transistor using a multimeter. Then, compare your conclusions with information from a datasheet or cross-reference book.		
Given conditions		
Part number =		
Parameters		
<div>Measured</div> <div>$V_{\text{bias(BE)}}$ <input type="text"/></div> <div>$V_{\text{bias(BC)}}$ <input type="text"/></div>		
Terminal identification (Draw your own sketch if the one shown is not appropriate)		
Advertised	Your conclusion	
		

Answer 15

Contrary to what you might think, the datasheet or cross-reference is not the "final authority" for checking your meter-based conclusions! I have seen datasheets and cross-reference manuals wrong more than once!

Notes 15

Identification of BJT terminals is a very important skill for technicians to have. Most modern multimeters have a *diode check* feature which may be used to positively identify PN junction polarities, and this is what I recommend students use for identifying BJT terminals.

To make this a really good performance assessment, you might want to take several BJT's and scratch the identifying labels off, so students cannot refer to memory for pin identification (for instance, if they remember the pin assignments of a 2N2222 because they use it so often). Label these transistors with your own numbers ("1", "2", etc.) so *you* will know which is which, but not the students!

Competency: Current-sourcing BJT switch		Version:
Schematic		
Given conditions		
$V_{\text{supply}} =$	$R_{\text{load}} =$	$\beta =$
Parameters		
	Predicted	Measured
I_{load}		
I_{switch}		
		Calculated
		β
		P_{Q1}
Fault analysis		
Suppose component fails <div style="display: inline-block; vertical-align: middle; margin-left: 10px;"> <input type="checkbox"/> open <input type="checkbox"/> other _____ <input type="checkbox"/> shorted </div>		
<i>What will happen in the circuit?</i>		

Answer 16

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 16

Being able to design a circuit using a BJT as a switch is a valuable skill for technicians and engineers alike to have. The circuit shown in this question is not the only possibility, but it is the simplest.

Remind your students that the equation for calculating BJT power dissipation is as follows:

$$P_Q = I_C \left(V_{CE} + \frac{V_{BE}}{\beta} \right)$$

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: Current-sinking BJT switch		Version:
Schematic		
Given conditions		
$V_{\text{supply}} =$	$R_{\text{load}} =$	$\beta =$
Parameters		
	Predicted	Measured
I_{load}		
I_{switch}		
		Calculated
		β
		P_{Q1}
Fault analysis		
Suppose component fails <div style="display: inline-block; vertical-align: middle; margin-left: 10px;"> <input type="checkbox"/> open <input type="checkbox"/> other _____ <input type="checkbox"/> shorted </div>		
<i>What will happen in the circuit?</i>		

Answer 17

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 17

Being able to design a circuit using a BJT as a switch is a valuable skill for technicians and engineers alike to have. The circuit shown in this question is not the only possibility, but it is the simplest.

Remind your students that the equation for calculating BJT power dissipation is as follows:

$$P_Q = I_C \left(V_{CE} + \frac{V_{BE}}{\beta} \right)$$

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: BJT switch circuit	Version:
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Description</div> <p style="margin-top: 10px;">Design and build a circuit that uses a switch to turn on a bipolar junction transistor, which then turns on a DC load such as a light bulb or small electric motor. The switch must only carry enough current to activate the BJT, and must not carry the full load current.</p>	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <p style="margin-top: 10px;">$V_{\text{supply}} =$</p>	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="height: 200px; border: 1px solid black; margin-top: 5px;"></div>	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <div style="display: flex; align-items: flex-start; margin-top: 10px;"> <div style="margin-right: 20px;"> <p>Measured</p> <div style="display: flex; align-items: center;"> I_{load} <div style="border: 1px solid black; width: 100px; height: 20px; margin-left: 10px;"></div> </div> <div style="display: flex; align-items: center; margin-top: 5px;"> I_{switch} <div style="border: 1px solid black; width: 100px; height: 20px; margin-left: 10px;"></div> </div> </div> <div> <p>Is $I_{\text{load}} \gg I_{\text{switch}}$?</p> </div> </div>	

file 02319

Answer 18

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 18

Being able to design a circuit using a BJT as a switch is a valuable skill for technicians and engineers alike to have.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: Buffered zener diode voltage regulator Version:									
Schematic									
Given conditions									
$V_{\text{supply}} =$	$V_{\text{zener}} =$								
$R_{\text{series}} =$									
Parameters									
	<table style="margin: auto;"> <thead> <tr> <th style="padding: 5px;">Predicted</th> <th style="padding: 5px;">Measured</th> </tr> </thead> <tbody> <tr> <td style="padding: 5px;">V_{load} (nominal)</td> <td style="border: 1px solid black; width: 100px; height: 20px;"></td> </tr> <tr> <td style="padding: 5px;">R_{load} (max)</td> <td style="border: 1px solid black; width: 100px; height: 20px;"></td> </tr> <tr> <td style="padding: 5px;">R_{load} (min)</td> <td style="border: 1px solid black; width: 100px; height: 20px;"></td> </tr> </tbody> </table>	Predicted	Measured	V_{load} (nominal)		R_{load} (max)		R_{load} (min)	
Predicted	Measured								
V_{load} (nominal)									
R_{load} (max)									
R_{load} (min)									
<i>While still regulating V_{load}</i>									
<p><i>Be sure to calculate transistor power dissipation before loading the circuit with R_{load} (min) and measuring V_{load} to ensure there will be no damage done to the circuit.</i></p>									
Fault analysis									
Suppose component fails <div style="display: inline-block; vertical-align: middle; margin-left: 10px;"> <input type="checkbox"/> open <input type="checkbox"/> other _____ <input type="checkbox"/> shorted </div>									
<i>What will happen in the circuit?</i>									

The R_{load} (max) and R_{load} (min) parameters are the maximum and minimum resistance settings that R_{load} may be adjusted to with the regulator circuit maintaining constant load voltage. V_{load} (nominal) is simply the regulated voltage output of the circuit under normal conditions.

file 01945

Answer 19

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 19

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts.

I highly recommend specifying a large value for R_{series} and/or a high-wattage rated transistor and variable load resistor, so that students do not dissipate excessive power at either the transistor or the load as they test for R_{load} (min). *Do not* use a decade resistance box for R_{load} unless you have made sure its power dissipation will not be exceeded under any circuit condition!

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: Darlington-buffered zener voltage regulator Version:									
Schematic									
Given conditions									
$V_{\text{supply}} =$	$V_{\text{zener}} =$								
$R_{\text{series}} =$									
Parameters									
	<table border="1" style="margin: auto; border-collapse: collapse;"> <thead> <tr> <th style="padding: 5px;">Predicted</th> <th style="padding: 5px;">Measured</th> </tr> </thead> <tbody> <tr> <td style="padding: 10px;">V_{load} (nominal)</td> <td style="padding: 10px;"></td> </tr> <tr> <td style="padding: 10px;">R_{load} (max)</td> <td style="padding: 10px;"></td> </tr> <tr> <td style="padding: 10px;">R_{load} (min)</td> <td style="padding: 10px;"></td> </tr> </tbody> </table>	Predicted	Measured	V_{load} (nominal)		R_{load} (max)		R_{load} (min)	
Predicted	Measured								
V_{load} (nominal)									
R_{load} (max)									
R_{load} (min)									
While still regulating V_{load}									
<p><i>Be sure to calculate transistor power dissipation before loading the circuit with R_{load} (min) and measuring V_{load} to ensure there will be no damage done to the circuit.</i></p>									
Fault analysis									
Suppose component fails <div style="display: inline-block; vertical-align: middle; margin-left: 10px;"> <input type="checkbox"/> open <input type="checkbox"/> other _____ <input type="checkbox"/> shorted </div>									
What will happen in the circuit?									

The R_{load} (max) and R_{load} (min) parameters are the maximum and minimum resistance settings that R_{load} may be adjusted to with the regulator circuit maintaining constant load voltage. V_{load} (nominal) is simply the regulated voltage output of the circuit under normal conditions.

file 2010

Answer 20

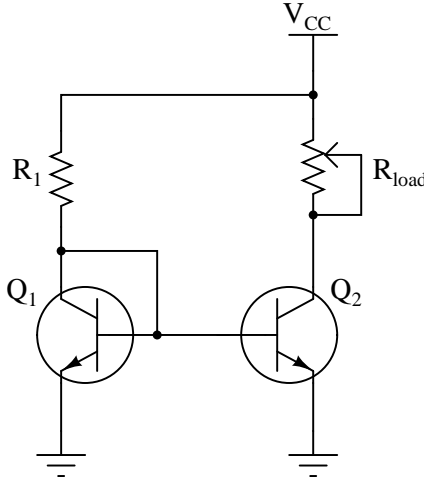
Use circuit simulation software to verify your predicted and measured parameter values.

Notes 20

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts.

I highly recommend specifying a large value for R_{series} and/or a high-wattage rated transistor and variable load resistor, so that students do not dissipate excessive power at either the transistor or the load as they test for R_{load} (min). *Do not* use a decade resistance box for R_{load} unless you have made sure its power dissipation will not be exceeded under any circuit condition!

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: Current mirror		Version:																					
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> 																							
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <div style="display: flex; justify-content: space-around; margin-top: 10px;"> $V_{CC} =$ $R_1 =$ $R_{load} \text{ (max)} =$ </div>																							
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="width: 15%;"></th> <th style="width: 20%; text-align: center;">Predicted</th> <th style="width: 20%; text-align: center;">Measured</th> <th style="width: 45%;"></th> </tr> </thead> <tbody> <tr> <td>I_{R1}</td> <td><input style="width: 80%;" type="text"/></td> <td><input style="width: 80%;" type="text"/></td> <td></td> </tr> <tr> <td>I_{load}</td> <td><input style="width: 80%;" type="text"/></td> <td><input style="width: 80%;" type="text"/></td> <td>(R_{load} set to mid-value)</td> </tr> <tr> <td>$R_{load(max)}$</td> <td><input style="width: 80%;" type="text"/></td> <td><input style="width: 80%;" type="text"/></td> <td>(Maximum R with I_{load} stable)</td> </tr> <tr> <td>$R_{load(min)}$</td> <td><input style="width: 80%;" type="text"/></td> <td><input style="width: 80%;" type="text"/></td> <td>(Minimum R with I_{load} stable)</td> </tr> </tbody> </table>					Predicted	Measured		I_{R1}	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>		I_{load}	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>	(R_{load} set to mid-value)	$R_{load(max)}$	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>	(Maximum R with I_{load} stable)	$R_{load(min)}$	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>	(Minimum R with I_{load} stable)
	Predicted	Measured																					
I_{R1}	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>																					
I_{load}	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>	(R_{load} set to mid-value)																				
$R_{load(max)}$	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>	(Maximum R with I_{load} stable)																				
$R_{load(min)}$	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>	(Minimum R with I_{load} stable)																				
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Fault analysis</div> <p>Suppose component <input style="width: 50px;" type="text"/> fails <input type="checkbox"/> open <input type="checkbox"/> other _____</p> <p><input type="checkbox"/> shorted</p> <p><i>What will happen in the circuit?</i></p>																							

file 01938

Answer 21

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 21

I recommend a 47 k Ω resistor for R_1 and a 100 k Ω potentiometer for R_{load} .

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: Signal biasing/unbiasing network		Version:
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div>		
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <div style="display: flex; justify-content: space-between; align-items: flex-start; margin-top: 10px;"> <div style="text-align: center;">$V_{in} =$</div> <div style="text-align: center;">$+V =$</div> <div style="text-align: center;">$C_1 = C_2 =$</div> <div style="text-align: center;">$R_{load} =$</div> <div style="text-align: center;">$R_{pot} =$</div> </div>		
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <p style="text-align: center; margin-top: 10px;"><i>With potentiometer set to its ____% position:</i></p> <div style="display: flex; justify-content: space-around; align-items: flex-start; margin-top: 10px;"> <div style="text-align: center;"> V_{TP1} </div> <div style="text-align: center;"> V_{TP2} </div> <div style="text-align: center;"> V_{TP3} </div> </div>		
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Explanation</div> <p style="margin-top: 10px;">What effect, if any, does the potentiometer position have on the voltage measured at each test point?</p> <p style="margin-top: 20px;">Explain how you could measure the effects of the potentiometer's position <i>without</i> using an oscilloscope.</p>		

Answer 22

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 22

The purpose of this exercise is to get students to understand how AC signals are mixed with DC voltages ("biased") and also how these DC bias voltages are removed to leave just an AC signal. This is important to understand for the purpose of analyzing BJT amplifier circuits.

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k Ω and 100 k Ω (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k 47k, 68k, etc.). Use a sine-wave function generator to supply an audio-frequency input signal.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: Common-collector biasing	Version:																								
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="text-align: center; margin-top: 20px;"> </div>																									
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <div style="display: flex; justify-content: space-around; margin-top: 10px;"> <div>$V_{CC} =$</div> <div>$R_{pot} =$</div> <div>$R_E =$</div> </div>																									
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; border-collapse: collapse; margin-top: 10px;"> <thead> <tr> <th style="width: 10%;"></th> <th style="width: 20%;">Predicted</th> <th style="width: 20%;">Measured</th> <th style="width: 50%;"> R_{pot} setting </th> </tr> </thead> <tbody> <tr> <td>V_E</td> <td><input style="width: 80%;" type="text"/></td> <td><input style="width: 80%;" type="text"/></td> <td>$V_B = 0$ volts</td> </tr> <tr> <td>V_E</td> <td><input style="width: 80%;" type="text"/></td> <td><input style="width: 80%;" type="text"/></td> <td>$V_B = 25\%$ of V_{CC}</td> </tr> <tr> <td>V_E</td> <td><input style="width: 80%;" type="text"/></td> <td><input style="width: 80%;" type="text"/></td> <td>$V_B = 50\%$ of V_{CC}</td> </tr> <tr> <td>V_E</td> <td><input style="width: 80%;" type="text"/></td> <td><input style="width: 80%;" type="text"/></td> <td>$V_B = 75\%$ of V_{CC}</td> </tr> <tr> <td>V_E</td> <td><input style="width: 80%;" type="text"/></td> <td><input style="width: 80%;" type="text"/></td> <td>$V_B = V_{CC}$</td> </tr> </tbody> </table>			Predicted	Measured	R_{pot} setting 	V_E	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>	$V_B = 0$ volts	V_E	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>	$V_B = 25\%$ of V_{CC}	V_E	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>	$V_B = 50\%$ of V_{CC}	V_E	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>	$V_B = 75\%$ of V_{CC}	V_E	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>	$V_B = V_{CC}$
	Predicted	Measured	R_{pot} setting 																						
V_E	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>	$V_B = 0$ volts																						
V_E	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>	$V_B = 25\%$ of V_{CC}																						
V_E	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>	$V_B = 50\%$ of V_{CC}																						
V_E	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>	$V_B = 75\%$ of V_{CC}																						
V_E	<input style="width: 80%;" type="text"/>	<input style="width: 80%;" type="text"/>	$V_B = V_{CC}$																						

file 01977

Answer 23

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 23

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k Ω and 100 k Ω (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k 47k, 68k, etc.).

Competency: Common-collector class-A amplifier Version:																	
Schematic																	
Given conditions																	
$V_{in} =$	$V_{CC} =$	$R_E =$															
$C_1 =$	$R_1 =$	$R_2 =$															
Parameters																	
<table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="padding: 5px;"></th> <th style="padding: 5px;">Predicted</th> <th style="padding: 5px;">Measured</th> </tr> </thead> <tbody> <tr> <td style="padding: 5px;">V_B (DC)</td> <td style="width: 100px; height: 30px;"></td> <td style="width: 100px; height: 30px;"></td> </tr> <tr> <td style="padding: 5px;">V_{out} (DC)</td> <td style="width: 100px; height: 30px;"></td> <td style="width: 100px; height: 30px;"></td> </tr> <tr> <td style="padding: 5px;">V_{out} (AC)</td> <td style="width: 100px; height: 30px;"></td> <td style="width: 100px; height: 30px;"></td> </tr> <tr> <td style="padding: 5px;">A_V</td> <td style="width: 100px; height: 30px;"></td> <td style="width: 100px; height: 30px;"></td> </tr> </tbody> </table>		Predicted	Measured	V_B (DC)			V_{out} (DC)			V_{out} (AC)			A_V			<p style="text-align: center; margin-bottom: 10px;"><i>Input and output waveforms (measured)</i></p>	
	Predicted	Measured															
V_B (DC)																	
V_{out} (DC)																	
V_{out} (AC)																	
A_V																	
Inverting . . . <input style="width: 30px; height: 20px;" type="checkbox"/>																	
or noninverting? <input style="width: 30px; height: 20px;" type="checkbox"/>																	

Answer 24

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 24

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between $1\text{ k}\Omega$ and $100\text{ k}\Omega$ (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k, 47k, 68k, etc.). Use a sine-wave function generator to supply an audio-frequency input signal, and make sure its amplitude isn't set so high that the amplifier clips.

I have had good success using the following values:

- $V_{CC} = 9\text{ volts}$
- $V_{in} = 1\text{ volt RMS, audio frequency}$
- $R_1 = 10\text{ k}\Omega$
- $R_2 = 10\text{ k}\Omega$
- $R_E = 27\text{ k}\Omega$
- $C_1 = 10\text{ }\mu\text{F}$

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: Common-emitter biasing		Version:	
Schematic			
Given conditions			
$V_{CC} =$	$R_{pot} =$	$R_C =$	$R_E =$
Parameters			
	Predicted	Measured	R_{pot} setting
V_C			$V_B = 0$ volts
V_C			$V_B = 25\%$ of V_{CC}
V_C			$V_B = 50\%$ of V_{CC}
V_C			$V_B = 75\%$ of V_{CC}
V_C			$V_B = V_{CC}$

file 01978

Answer 25

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 25

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k Ω and 100 k Ω (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k 47k, 68k, etc.).

Competency: Common-emitter class-A amplifier		Version:															
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="text-align: center; margin-top: 20px;"> </div>																	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <table style="width: 100%; margin-top: 10px;"> <tr> <td style="width: 25%;">$V_{in} =$</td> <td style="width: 25%;">$V_{CC} =$</td> <td style="width: 25%;">$R_C =$</td> <td style="width: 25%;">$R_E =$</td> </tr> <tr> <td></td> <td>$C_1 =$</td> <td>$R_1 =$</td> <td>$R_2 =$</td> </tr> </table>			$V_{in} =$	$V_{CC} =$	$R_C =$	$R_E =$		$C_1 =$	$R_1 =$	$R_2 =$							
$V_{in} =$	$V_{CC} =$	$R_C =$	$R_E =$														
	$C_1 =$	$R_1 =$	$R_2 =$														
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; margin-top: 10px;"> <thead> <tr> <th></th> <th style="text-align: center;">Predicted</th> <th style="text-align: center;">Measured</th> </tr> </thead> <tbody> <tr> <td>V_B (DC)</td> <td><div style="border: 1px solid black; width: 100px; height: 25px;"></div></td> <td><div style="border: 1px solid black; width: 100px; height: 25px;"></div></td> </tr> <tr> <td>V_{out} (DC)</td> <td><div style="border: 1px solid black; width: 100px; height: 25px;"></div></td> <td><div style="border: 1px solid black; width: 100px; height: 25px;"></div></td> </tr> <tr> <td>V_{out} (AC)</td> <td><div style="border: 1px solid black; width: 100px; height: 25px;"></div></td> <td><div style="border: 1px solid black; width: 100px; height: 25px;"></div></td> </tr> <tr> <td>A_V</td> <td><div style="border: 1px solid black; width: 100px; height: 25px;"></div></td> <td><div style="border: 1px solid black; width: 100px; height: 25px;"></div></td> </tr> </tbody> </table> <div style="margin-top: 10px;"> Inverting . . . <input type="checkbox"/> </div> <div style="margin-top: 5px;"> or noninverting? <input type="checkbox"/> </div> <div style="margin-top: 20px; text-align: right;"> <i>Input and output waveforms (measured)</i> </div> <div style="text-align: center; margin-top: 10px;"> </div>				Predicted	Measured	V_B (DC)	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>	V_{out} (DC)	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>	V_{out} (AC)	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>	A_V	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>
	Predicted	Measured															
V_B (DC)	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>															
V_{out} (DC)	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>															
V_{out} (AC)	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>															
A_V	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>															

Answer 26

Use circuit simulation software to verify your predicted and measured parameter values.





Notes 26

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between $1\text{ k}\Omega$ and $100\text{ k}\Omega$ (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k 47k, 68k, etc.). Use a sine-wave function generator to supply an audio-frequency input signal, and make sure its amplitude isn't set so high that the amplifier clips.

I have had good success using the following values:

- $V_{CC} = 9\text{ volts}$
- $V_{in} = \text{audio-frequency signal, } 0.5\text{ volt peak-to-peak}$
- $R_1 = 220\text{ k}\Omega$
- $R_2 = 27\text{ k}\Omega$
- $R_C = 10\text{ k}\Omega$
- $R_E = 1.5\text{ k}\Omega$
- $C_1 = 10\text{ }\mu\text{F}$

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

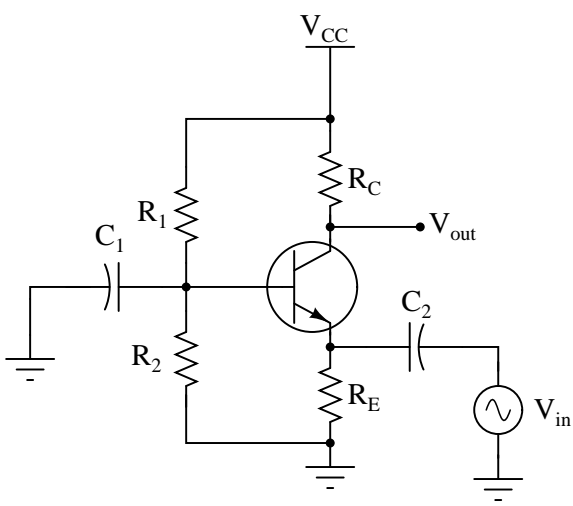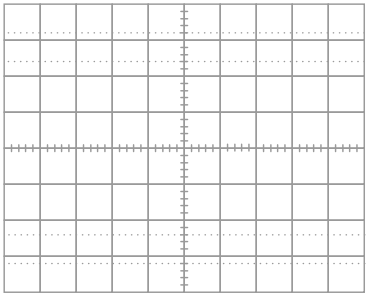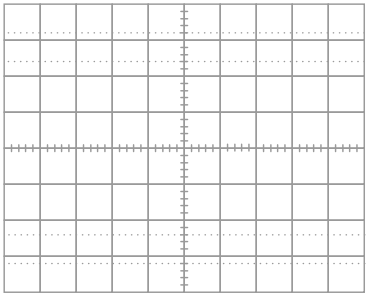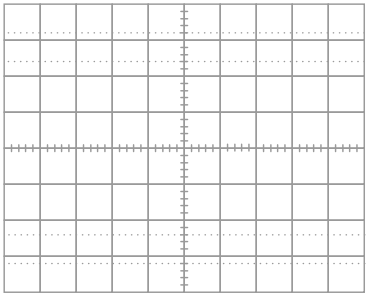Competency: Common-base class-A amplifier		Version:																									
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> 																											
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <table style="width: 100%; border-collapse: collapse;"> <tr> <td style="width: 25%; text-align: right;">$V_{in} =$</td> <td style="width: 25%; text-align: right;">$V_{CC} =$</td> <td style="width: 25%; text-align: right;">$R_C =$</td> <td style="width: 25%; text-align: right;">$R_E =$</td> </tr> <tr> <td style="text-align: right;">$C_1 = C_2 =$</td> <td style="text-align: right;">$R_1 =$</td> <td style="text-align: right;">$R_2 =$</td> <td></td> </tr> </table>			$V_{in} =$	$V_{CC} =$	$R_C =$	$R_E =$	$C_1 = C_2 =$	$R_1 =$	$R_2 =$																		
$V_{in} =$	$V_{CC} =$	$R_C =$	$R_E =$																								
$C_1 = C_2 =$	$R_1 =$	$R_2 =$																									
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="width: 15%;"></th> <th style="width: 20%; text-align: center;">Predicted</th> <th style="width: 20%; text-align: center;">Measured</th> <th style="width: 45%;"></th> </tr> </thead> <tbody> <tr> <td>V_B (DC)</td> <td><div style="border: 1px solid black; width: 100px; height: 25px;"></div></td> <td><div style="border: 1px solid black; width: 100px; height: 25px;"></div></td> <td rowspan="4" style="text-align: center; vertical-align: middle;"> <i>Input and output waveforms (measured)</i>  </td> </tr> <tr> <td>V_{out} (DC)</td> <td><div style="border: 1px solid black; width: 100px; height: 25px;"></div></td> <td><div style="border: 1px solid black; width: 100px; height: 25px;"></div></td> </tr> <tr> <td>V_{out} (AC)</td> <td><div style="border: 1px solid black; width: 100px; height: 25px;"></div></td> <td><div style="border: 1px solid black; width: 100px; height: 25px;"></div></td> </tr> <tr> <td>A_V</td> <td><div style="border: 1px solid black; width: 100px; height: 25px;"></div></td> <td><div style="border: 1px solid black; width: 100px; height: 25px;"></div></td> </tr> <tr> <td colspan="4" style="padding-top: 10px;"> Inverting . . . <input style="width: 30px; height: 20px;" type="checkbox"/> </td> </tr> <tr> <td colspan="4" style="padding-top: 10px;"> or noninverting? <input style="width: 30px; height: 20px;" type="checkbox"/> </td> </tr> </tbody> </table>				Predicted	Measured		V_B (DC)	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>	<i>Input and output waveforms (measured)</i> 	V_{out} (DC)	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>	V_{out} (AC)	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>	A_V	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>	Inverting . . . <input style="width: 30px; height: 20px;" type="checkbox"/>				or noninverting? <input style="width: 30px; height: 20px;" type="checkbox"/>			
	Predicted	Measured																									
V_B (DC)	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>	<i>Input and output waveforms (measured)</i> 																								
V_{out} (DC)	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>																									
V_{out} (AC)	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>																									
A_V	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>																									
Inverting . . . <input style="width: 30px; height: 20px;" type="checkbox"/>																											
or noninverting? <input style="width: 30px; height: 20px;" type="checkbox"/>																											

Answer 27

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 27

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between $1\text{ k}\Omega$ and $100\text{ k}\Omega$ (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k, 47k, 68k, etc.). Use a sine-wave function generator to supply an audio-frequency input signal, and make sure its amplitude isn't set so high that the amplifier clips.

The voltage gain of this amplifier configuration tends to be very high, approximately equal to $\frac{R_C}{r'_e}$. Your students will have to use fairly low input voltages to achieve class A operation with this amplifier circuit. I have had good success using the following values:

- $V_{CC} = 12\text{ volts}$
- $V_{in} = 20\text{ mV}$ peak-to-peak, at 5 kHz
- $R_1 = 1\text{ k}\Omega$
- $R_2 = 4.7\text{ k}\Omega$
- $R_C = 100\text{ }\Omega$
- $R_E = 1\text{ k}\Omega$
- $C_1 = 33\text{ }\mu\text{F}$

Your students will find the actual voltage gain deviates somewhat from predicted values with this circuit, largely because it is so dependent on the value of r'_e , and that parameter tends to be unpredictable.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: Variable-bias, common-emitter BJT amp		Version:
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Schematic</div>		
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Given conditions</div>		
$V_{in} =$	$V_{CC} =$	$R_C =$ $R_E =$
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Parameters</div>		
	Predicted	Measured
A_V	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>
V_{out}	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>	<div style="border: 1px solid black; width: 100px; height: 25px;"></div>
<i>In class-A mode</i>		
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Fault analysis</div>		
Suppose component <div style="border: 1px solid black; display: inline-block; width: 50px; height: 20px; vertical-align: middle;"></div> fails <div style="display: inline-block; vertical-align: middle; margin-left: 10px;"> <input type="checkbox"/> open <input type="checkbox"/> other _____ <input type="checkbox"/> shorted </div>		
<i>What will happen in the circuit?</i>		

file 03919

Answer 28

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 28

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k Ω and 100 k Ω (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k 47k, 68k, etc.). Use a sine-wave function generator to supply an audio-frequency input signal, about 0.5 volts AC (peak).

Resistor values I have found practical are 10 k Ω for R_C and 2.2 k Ω for R_E . This gives a voltage gain of 4.545, and quiescent current values that are well within the range of common small-signal transistors.

An important aspect of this performance assessment is that students know what to do with the potentiometer. It is their responsibility to configure the circuit so that it operates in Class-A mode, and to explain the importance of proper biasing.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: Variable-class BJT amplifier circuit		Version:						
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Schematic</div>								
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Given conditions</div>								
$V_{in} =$	$V_{CC} =$	$R_C =$						
$R_E =$								
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Parameters</div>								
A_v V_{out}	<table border="1" style="margin: auto;"> <thead> <tr> <th style="padding: 5px;">Predicted</th> <th style="padding: 5px;">Measured</th> </tr> </thead> <tbody> <tr> <td style="height: 30px;"></td> <td style="height: 30px;"></td> </tr> <tr> <td style="height: 30px;"></td> <td style="height: 30px;"></td> </tr> </tbody> </table>	Predicted	Measured					<i>In class-A mode</i>
Predicted	Measured							
Input and output voltage waveform plots								
<i>Class-A output</i> 	<i>Class-B output</i> 	<i>Class-C output</i> 						

file 01624

Answer 29

Use circuit simulation software to verify your predicted and measured parameter values.




Notes 29

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k Ω and 100 k Ω (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k 47k, 68k, etc.). Use a sine-wave function generator to supply an audio-frequency input signal, about 0.5 volts AC (peak).

Resistor values I have found practical are 10 k Ω for R_C and 2.2 k Ω for R_E . This gives a voltage gain of 4.545, and quiescent current values that are well within the range of common small-signal transistors.

An important aspect of this performance assessment is that students know what to do with the potentiometer. It is their responsibility to configure the circuit so that it operates in each mode (Class-A, Class-B, and Class-C).

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

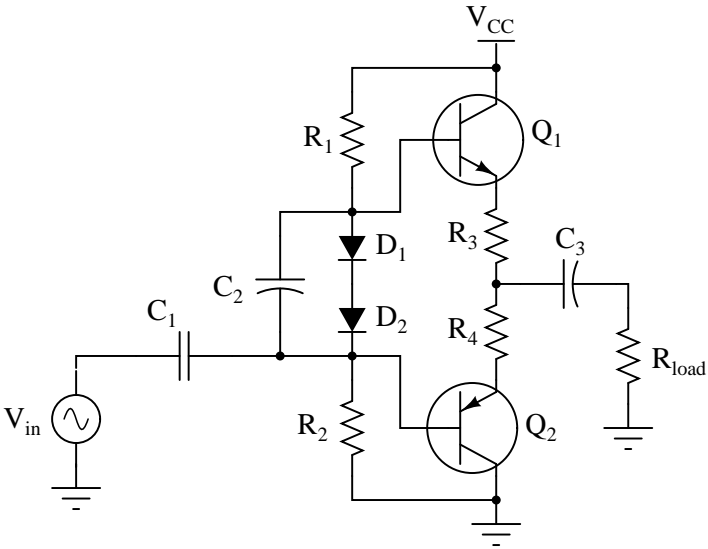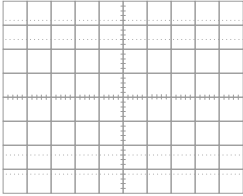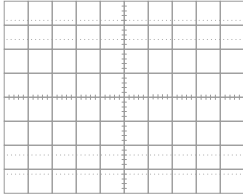Competency: Push-pull BJT amplifier circuit		Version:											
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> 													
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <table style="width: 100%; border-collapse: collapse;"> <tr> <td style="width: 20%;">$V_{in} =$</td> <td style="width: 20%;">$V_{CC} =$</td> <td style="width: 20%;">$R_1 = R_2 =$</td> <td style="width: 20%;">$C_1 =$</td> <td style="width: 20%;">$C_2 =$</td> </tr> <tr> <td></td> <td></td> <td>$R_3 = R_4 =$</td> <td>$C_3 =$</td> <td></td> </tr> </table>				$V_{in} =$	$V_{CC} =$	$R_1 = R_2 =$	$C_1 =$	$C_2 =$			$R_3 = R_4 =$	$C_3 =$	
$V_{in} =$	$V_{CC} =$	$R_1 = R_2 =$	$C_1 =$	$C_2 =$									
		$R_3 = R_4 =$	$C_3 =$										
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="width: 15%;"></th> <th style="width: 20%; text-align: center;">Predicted</th> <th style="width: 20%; text-align: center;">Measured</th> </tr> </thead> <tbody> <tr> <td>A_v</td> <td style="border: 1px solid black; height: 20px;"></td> <td style="border: 1px solid black; height: 20px;"></td> </tr> <tr> <td>V_{out}</td> <td style="border: 1px solid black; height: 20px;"></td> <td style="border: 1px solid black; height: 20px;"></td> </tr> </tbody> </table> <p style="text-align: center; margin-top: 10px;">Draw the output waveforms with 2 diodes and with 1 diode and explain why there is more distortion in one case.</p> <div style="display: flex; justify-content: space-around; margin-top: 10px;"> <div style="text-align: center;"> <p><i>With both diodes working</i></p>  </div> <div style="text-align: center;"> <p><i>With one diode shorted</i></p>  </div> </div>					Predicted	Measured	A_v			V_{out}			
	Predicted	Measured											
A_v													
V_{out}													

Answer 30

Use circuit simulation software to verify your predicted and measured parameter values.


Notes 30

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between $1\text{ k}\Omega$ and $100\text{ k}\Omega$ (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k, 47k, 68k, etc.). Use a sine-wave function generator to supply an audio-frequency input signal, and make sure its amplitude isn't set so high that the amplifier clips.

I have had good success using the following values:

- $V_{CC} = 6\text{ volts}$
- $V_{in} = 1\text{ volt (peak)}$
- $R_1 = R_2 = 10\text{ k}\Omega$
- $R_3 = R_4 = 10\text{ }\Omega$
- $C_1 = 0.47\text{ }\mu\text{F}$
- $C_2 = 10\text{ }\mu\text{F}$
- $C_3 = 47\text{ }\mu\text{F}$
- $D_1 = D_2 = \text{part number 1N4001}$
- $Q_1 = \text{part number 2N2222}$
- $Q_2 = \text{part number 2N2907}$

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

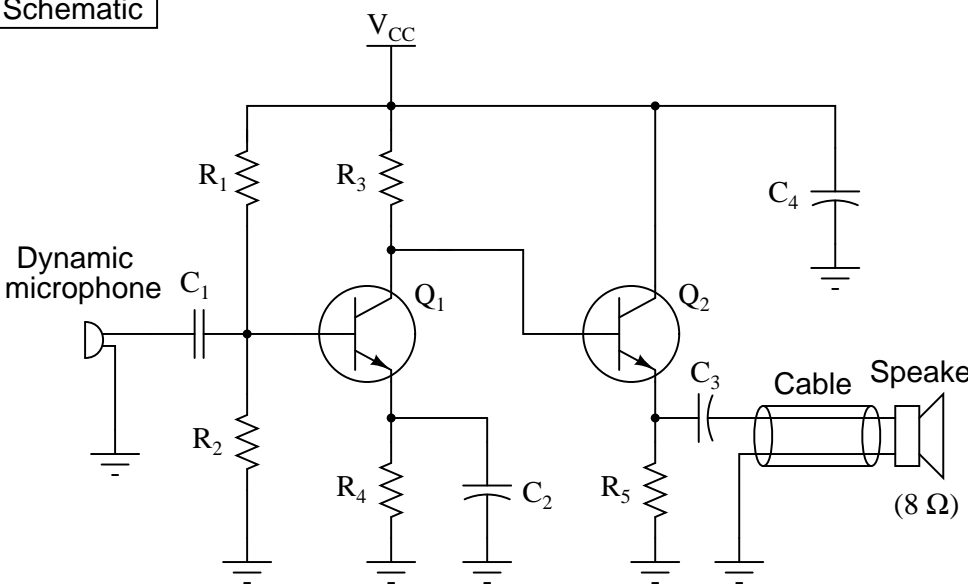Competency: Audio intercom circuit		Version:			
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> 					
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given component values</div> <table style="width: 100%; border-collapse: collapse;"> <tr> <td style="width: 33%; vertical-align: top;">$V_{CC} =$</td> <td style="width: 33%; vertical-align: top;"> $C_1 =$ $C_2 =$ $C_3 =$ $C_4 =$ </td> <td style="width: 33%; vertical-align: top;"> $R_1 =$ $R_2 =$ $R_3 =$ $R_4 =$ $R_5 =$ </td> </tr> </table>			$V_{CC} =$	$C_1 =$ $C_2 =$ $C_3 =$ $C_4 =$	$R_1 =$ $R_2 =$ $R_3 =$ $R_4 =$ $R_5 =$
$V_{CC} =$	$C_1 =$ $C_2 =$ $C_3 =$ $C_4 =$	$R_1 =$ $R_2 =$ $R_3 =$ $R_4 =$ $R_5 =$			
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Fault analysis</div> <p>Suppose component fails <input type="checkbox"/> open <input type="checkbox"/> other _____ <input type="checkbox"/> shorted </p> <p><i>What will happen in the circuit?</i></p> <div style="height: 150px; border: 1px solid black; margin-top: 10px;"></div>					

Answer 31

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 31

I've experienced good results using the following component values:

- $V_{CC} = 12$ volts
- $R_1 = 220$ k Ω
- $R_2 = 27$ k Ω
- $R_3 = 10$ k Ω
- $R_4 = 1.5$ k Ω
- $R_5 = 1$ k Ω
- $C_1 = 0.47$ μ F
- $C_2 = 4.7$ μ F
- $C_3 = 33$ μ F
- $C_4 = 47$ μ F
- Q_1 and $Q_2 = 2N3403$

Students have a lot of fun connecting long lengths of cable between the output stage and the speaker, and using this circuit to talk (one-way, simplex communication) between rooms.

One thing I've noticed some students misunderstand in their study of electronic amplifier circuits is their practical purpose. So many textbooks emphasize abstract analysis with sinusoidal voltage sources and resistive loads that some of the real applications of amplifiers may be overlooked by some students. One student of mine in particular, when building this circuit, kept asking me, "so where does the signal generator connect to this amplifier?" He was so used to seeing signal generators connected to amplifier inputs in his textbook (and lab manual!) that he never realized you could use an amplifier circuit to amplify a *real*, practical audio signal!!! An extreme example, perhaps, but real nevertheless, and illustrative of the need for practical application in labwork.

In order for students to measure the voltage gain of this amplifier, they must apply a steady, sinusoidal signal to the input. The microphone and speaker are indeed practical, but the signals produced in such a circuit are too chaotic for students to measure with simple test equipment.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: Audio intercom circuit, push-pull output Version:													
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div>													
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Two-wire electret microphone schematic</div>	<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given component values</div> <table style="width: 100%; border-collapse: collapse;"> <tr> <td style="width: 50%;">$C_1 = C_2 =$</td> <td style="width: 50%;">$R_1 =$</td> </tr> <tr> <td>$C_3 = C_4 =$</td> <td>$R_2 =$</td> </tr> <tr> <td>$C_5 =$</td> <td>$R_3 =$</td> </tr> <tr> <td>$C_6 =$</td> <td>$R_4 =$</td> </tr> <tr> <td>$V_{CC} =$</td> <td>$R_5 = R_6 =$</td> </tr> <tr> <td></td> <td>$R_7 = R_8 =$</td> </tr> </table>	$C_1 = C_2 =$	$R_1 =$	$C_3 = C_4 =$	$R_2 =$	$C_5 =$	$R_3 =$	$C_6 =$	$R_4 =$	$V_{CC} =$	$R_5 = R_6 =$		$R_7 = R_8 =$
$C_1 = C_2 =$	$R_1 =$												
$C_3 = C_4 =$	$R_2 =$												
$C_5 =$	$R_3 =$												
$C_6 =$	$R_4 =$												
$V_{CC} =$	$R_5 = R_6 =$												
	$R_7 = R_8 =$												
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Fault analysis</div> <p>Suppose component fails <input type="checkbox"/> open <input type="checkbox"/> other _____</p> <p style="margin-left: 100px;"><input type="checkbox"/> shorted</p> <p><i>What will happen in the circuit?</i></p>													

Answer 32

Use circuit simulation software to verify your predicted and measured parameter values.


Notes 32

Use a variable-voltage, regulated power supply to supply a DC voltage safely below the maximum rating of the electret microphone (typically 10 volts). Specify standard resistor values, all between 1 k Ω and 100 k Ω (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k 47k, 68k, etc.). Use a sine-wave function generator to supply an audio-frequency input signal, and make sure its amplitude isn't set so high that the amplifier clips.

I have had good success using the following values:

- $V_{CC} = 6$ volts
- $R_1 = 68$ k Ω
- $R_2 = 33$ k Ω
- $R_3 = 4.7$ k Ω
- $R_4 = 1.5$ k Ω
- $R_5 = R_6 = 10$ k Ω
- $R_7 = R_8 = 10$ Ω
- $C_1 = C_2 = 0.47$ μ F
- $C_3 = C_4 = 47$ μ F
- $C_5 = 1000$ μ F
- $C_6 = 100$ μ F
- $D_1 = D_2 =$ part number 1N4001
- $Q_1 =$ part number 2N2222
- $Q_2 =$ part number 2N2222
- $Q_3 =$ part number 2N2907

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

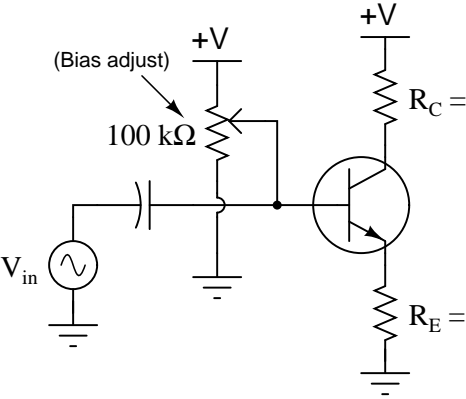Competency: Class-A BJT amplifier w/specified gain Version:													
<div>Description</div> <p>Design and build a class-A BJT amplifier circuit with a voltage gain (A_V) that is within tolerance of the gain specified.</p> <p>You may use a potentiometer to adjust the biasing of the transistor, to make the design process easier.</p>													
<div>Given conditions</div> <p>$V_{in} =$ $+V =$ $A_V =$ Tolerance$_{A_V} =$</p>													
<div>Schematic</div> 													
<div>Parameters</div> <table><thead><tr><th></th><th>Measured</th><th></th><th>Calculated</th></tr></thead><tbody><tr><td>V_{in}</td><td><input type="text"/></td><td>A_V</td><td><input type="text"/></td></tr><tr><td>V_{out}</td><td><input type="text"/></td><td>Error$_{A_V}$</td><td><input type="text"/></td></tr></tbody></table> <div>$\frac{A_{V(actual)} - A_{V(ideal)}}{A_{V(ideal)}} \times 100\%$</div>			Measured		Calculated	V_{in}	<input type="text"/>	A_V	<input type="text"/>	V_{out}	<input type="text"/>	Error $_{A_V}$	<input type="text"/>
	Measured		Calculated										
V_{in}	<input type="text"/>	A_V	<input type="text"/>										
V_{out}	<input type="text"/>	Error $_{A_V}$	<input type="text"/>										

file 01935

Answer 33

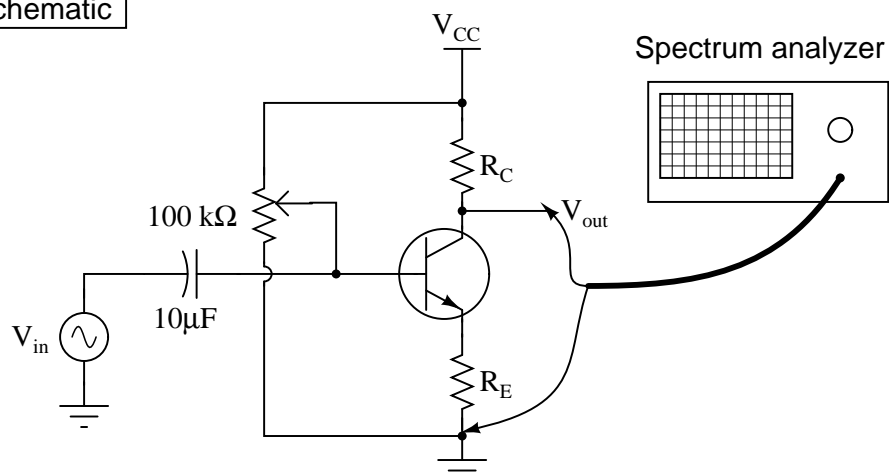
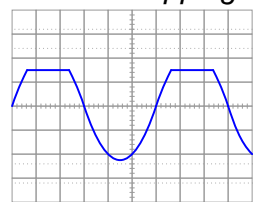
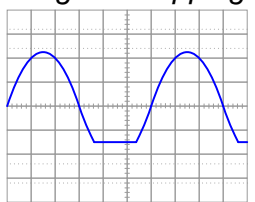
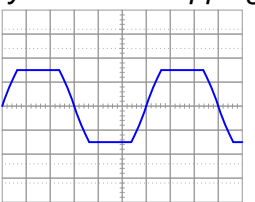
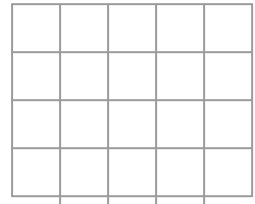
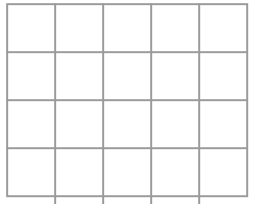
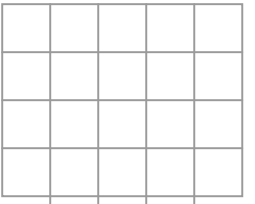
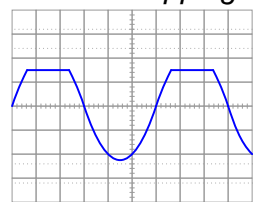
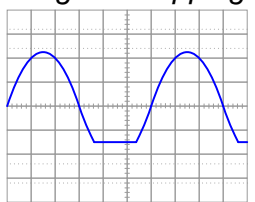
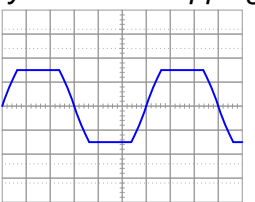
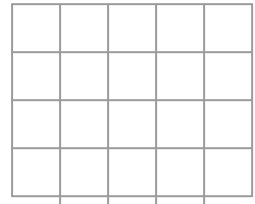
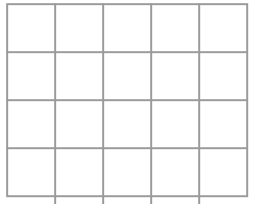
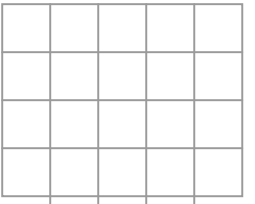
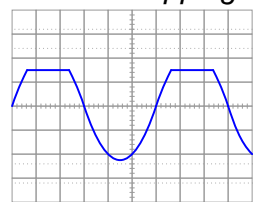
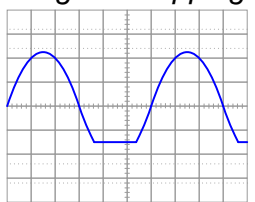
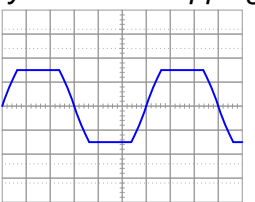
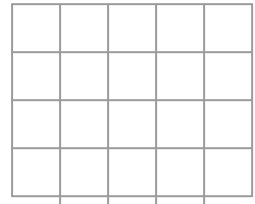
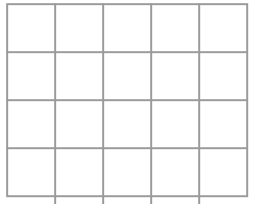
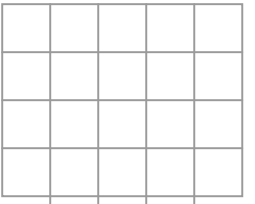
Use circuit simulation software to verify your predicted and measured parameter values.

Notes 33

Students are allowed to adjust the bias potentiometer to achieve class-A operation after calculating and inserting the resistance values R_C and R_E . However, they are not allowed to change either R_C or R_E once the circuit is powered and tested, lest they achieve the specified gain through trial-and-error!

A good percentage tolerance for gain is $\pm 10\%$. The lower you set the target gain, the more accuracy you may expect out of your students' circuits. I usually select random values of voltage gain between 2 and 10, and I strongly recommend that students choose resistor values between 1 k Ω and 100 k Ω . Resistor values much lower than 1 k Ω lead to excessive quiescent currents, which may cause accuracy problems (r'_e drifting due to temperature effects).

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: Testing amplifier distortion		Version:															
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> 																	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <div style="display: flex; justify-content: space-around; align-items: flex-end;"> <div style="text-align: center;">$V_{in} =$</div> <div style="text-align: center;">$V_{CC} =$</div> <div style="text-align: center;">$R_C =$</div> <div style="text-align: center;">$R_E =$</div> </div>																	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="text-align: center; padding: 5px;"><i>Positive clipping</i></th> <th style="text-align: center; padding: 5px;"><i>Negative clipping</i></th> <th style="text-align: center; padding: 5px;"><i>Symmetrical clipping</i></th> </tr> </thead> <tbody> <tr> <td style="text-align: center; padding: 10px;">  </td> <td style="text-align: center; padding: 10px;">  </td> <td style="text-align: center; padding: 10px;">  </td> </tr> <tr> <td style="text-align: center; padding: 5px;">Oscilloscope trace</td> <td style="text-align: center; padding: 5px;">Oscilloscope trace</td> <td style="text-align: center; padding: 5px;">Oscilloscope trace</td> </tr> <tr> <td style="text-align: center; padding: 10px;">  </td> <td style="text-align: center; padding: 10px;">  </td> <td style="text-align: center; padding: 10px;">  </td> </tr> <tr> <td style="text-align: center; padding: 5px;">1st 2nd 3rd 4th Spectrum analyzer display</td> <td style="text-align: center; padding: 5px;">1st 2nd 3rd 4th Spectrum analyzer display</td> <td style="text-align: center; padding: 5px;">1st 2nd 3rd 4th Spectrum analyzer display</td> </tr> </tbody> </table>			<i>Positive clipping</i>	<i>Negative clipping</i>	<i>Symmetrical clipping</i>				Oscilloscope trace	Oscilloscope trace	Oscilloscope trace				1st 2nd 3rd 4th Spectrum analyzer display	1st 2nd 3rd 4th Spectrum analyzer display	1st 2nd 3rd 4th Spectrum analyzer display
<i>Positive clipping</i>	<i>Negative clipping</i>	<i>Symmetrical clipping</i>															
																	
Oscilloscope trace	Oscilloscope trace	Oscilloscope trace															
																	
1st 2nd 3rd 4th Spectrum analyzer display	1st 2nd 3rd 4th Spectrum analyzer display	1st 2nd 3rd 4th Spectrum analyzer display															
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Analysis</div> <div style="margin-left: 20px;"> <p>Which clipping conditions generate even harmonics?</p> <p>Which clipping conditions generate odd harmonics?</p> </div>																	

Answer 34

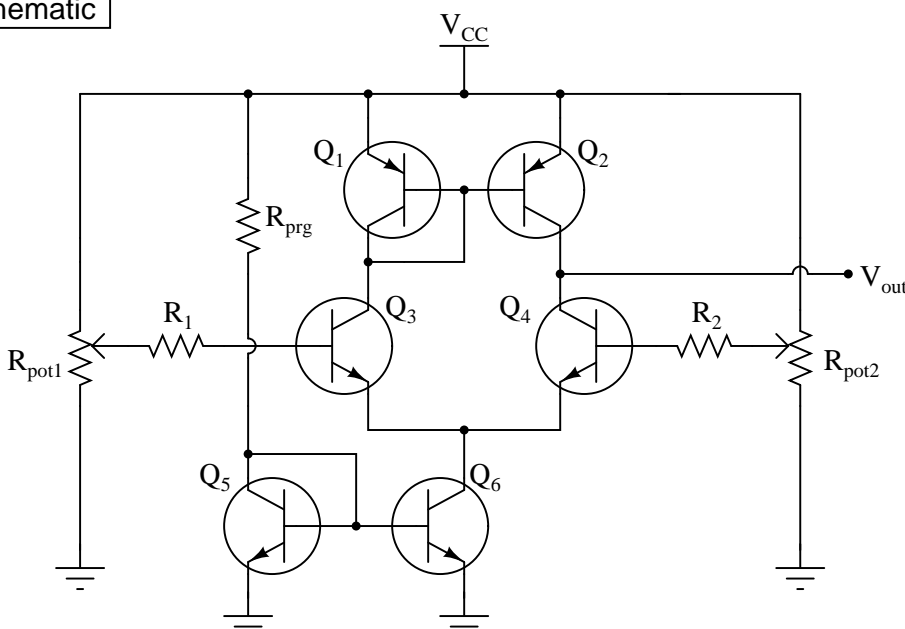
Use circuit simulation software to verify your predicted and measured parameter values.

Notes 34

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k Ω and 100 k Ω (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k 47k, 68k, etc.). Use a sine-wave function generator to supply an audio-frequency input signal.

If you lack a spectrum analyzer in your lab, fear not! There are free software packages in existence allowing you to use the audio input of a personal computer's sound card as a (limited) spectrum analyzer and oscilloscope! You may find some of these packages by searching on the Internet. One that I've used (2002) successfully in my own class is called WinScope.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: BJT differential amplifier		Version:												
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> 														
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <div style="display: flex; justify-content: space-around; align-items: flex-start;"> <div style="text-align: center;"> $V_{CC} =$ </div> <div style="text-align: center;"> $R_1 = R_2 =$ </div> <div style="text-align: center;"> $R_{prg} =$ </div> </div> <div style="text-align: center; margin-top: 10px;"> $R_{pot1} = R_{pot2} =$ </div>														
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="width: 15%;"></th> <th style="width: 20%; text-align: center;">Predicted</th> <th style="width: 20%; text-align: center;">Measured</th> </tr> </thead> <tbody> <tr> <td>$I_C (Q_6)$</td> <td style="border: 1px solid black; height: 20px;"></td> <td style="border: 1px solid black; height: 20px;"></td> </tr> <tr> <td colspan="3" style="padding-top: 10px;"> Which transistor does the inverting input belong to? </td> </tr> <tr> <td colspan="3" style="padding-top: 10px;"> Which transistor does the non-inverting input belong to? </td> </tr> </tbody> </table>				Predicted	Measured	$I_C (Q_6)$			Which transistor does the inverting input belong to? 			Which transistor does the non-inverting input belong to? 		
	Predicted	Measured												
$I_C (Q_6)$														
Which transistor does the inverting input belong to? 														
Which transistor does the non-inverting input belong to? 														

Answer 35

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 35

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k Ω and 100 k Ω (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k 47k, 68k, etc.).



I suggest using ordinary (general-purpose) signal transistors in this circuit, such as the 2N2222 and 2N3403 (NPN), and the 2N2907 and 2N3906 (PNP) models, operating with a V_{CC} of 12 volts. When constructed as shown, this circuit has sufficient gain to be used as a crude operational amplifier (connect the inverting input to the output through various feedback networks).

These values have worked well for me:

- $V_{CC} = 12$ volts
- $R_1 = 10$ k Ω
- $R_2 = 10$ k Ω
- $R_{prg} = 10$ k Ω
- $R_{pot1} = 10$ k Ω
- $R_{pot2} = 10$ k Ω

I recommend instructing students to set each potentiometer near its mid-position of travel, then slightly adjusting each one to see the sharp change in output voltage as one input voltage crosses the other. If students wish to monitor each of the input voltages to check for a condition of crossing, they should measure right at the transistor base terminals, not at the potentiometer wiper terminals, so as to not incur error resulting from current through protection resistors R_1 or R_2 .

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

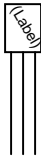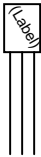Competency: JFET terminal identification		Version:
Description		
Identify the terminals (emitter, base, and collector) of a junction field-effect transistor using a multimeter. Then, compare your conclusions with information from a datasheet or cross-reference book.		
Given conditions		
Part number =		
Parameters		
	Measured	
$V_{\text{gate-channel}}$		<input type="text"/>
V_{channel}		<input type="text"/>
Terminal identification		
(Draw your own sketch if the one shown is not appropriate)		
Advertised	Your conclusion	
		

Answer 36

Contrary to what you might think, the datasheet or cross-reference is not the "final authority" for checking your meter-based conclusions! I have seen datasheets and cross-reference manuals wrong more than once!

Notes 36

Identification of JFET terminals is a very important skill for technicians to have. Most modern multimeters have a *diode check* feature which may be used to positively identify PN junction polarities, and this is what I recommend students use for identifying JFET terminals.

To make this a really good performance assessment, you might want to take several JFET's and scratch the identifying labels off, so students cannot refer to memory for pin identification (for instance, if they remember the pin assignments of a J309 because they use it so often). Label these transistors with your own numbers ("1", "2", etc.) so *you* will know which is which, but not the students!

Competency: Current-sourcing JFET switch		Version:	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Schematic</div>			
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Given conditions</div>			
$V_{\text{supply}} =$	$R_1 =$	$R_{\text{dropping}} =$	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Parameters</div>			
$I_{\text{LED}} (\text{max})$	Predicted	Measured	
	<input style="width: 100px; height: 25px;" type="text"/>	<input style="width: 100px; height: 25px;" type="text"/>	
$V_{\text{GS (off)}}$	Advertised	Measured	Calculated
	<input style="width: 100px; height: 25px;" type="text"/>	<input style="width: 100px; height: 25px;" type="text"/>	P_{Q1} <input style="width: 100px; height: 25px;" type="text"/>
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Schematic</div>			
(Draw a schematic diagram showing what is necessary to turn the transistor fully <i>off</i>)			

Answer 37

Use circuit simulation software to verify your predicted and measured parameter values.


Notes 37

I strongly recommend a value for R_1 of $1\text{ M}\Omega$ or more, to protect the JFET gate from overcurrent damage. The students will calculate their own dropping resistor value, based on the supply voltage and the LED ratings.

This exercise lends itself to experimentation with static electricity. The input impedance of an average JFET is so high that the LED may be made to turn on and off with just a touch of the probe wire to a charged object (such as a person).

Using only the components shown, students may not be able to get their JFETs to completely turn off. This is left for them as a challenge to figure out!

I expect students to be able to figure out how to calculate the transistor's power dissipation without being told what measurements to take!

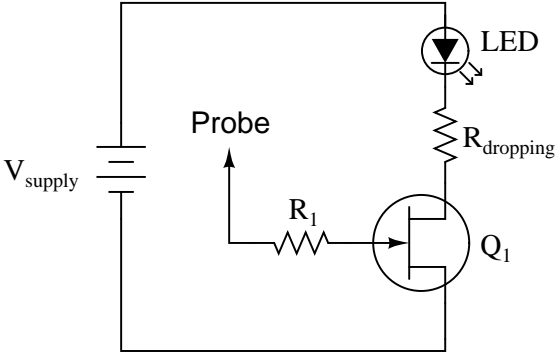Competency: Current-sinking JFET switch		Version:																	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> 																			
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <div style="display: flex; justify-content: space-around; margin-top: 10px;"> <div>$V_{\text{supply}} =$</div> <div>$R_1 =$</div> <div>$R_{\text{dropping}} =$</div> </div>																			
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; border-collapse: collapse; margin-top: 10px;"> <tr> <td style="width: 20%;"></td> <td style="width: 20%; text-align: center;">Predicted</td> <td style="width: 20%; text-align: center;">Measured</td> <td style="width: 40%;"></td> </tr> <tr> <td>$I_{\text{LED}} (\text{max})$</td> <td style="border: 1px solid black; height: 25px;"></td> <td style="border: 1px solid black; height: 25px;"></td> <td></td> </tr> <tr> <td></td> <td style="text-align: center;">Advertised</td> <td style="text-align: center;">Measured</td> <td style="text-align: center;">Calculated</td> </tr> <tr> <td>$V_{\text{GS (off)}}$</td> <td style="border: 1px solid black; height: 25px;"></td> <td style="border: 1px solid black; height: 25px;"></td> <td>P_{Q1} </td> </tr> </table>					Predicted	Measured		$I_{\text{LED}} (\text{max})$					Advertised	Measured	Calculated	$V_{\text{GS (off)}}$			P_{Q1}
	Predicted	Measured																	
$I_{\text{LED}} (\text{max})$																			
	Advertised	Measured	Calculated																
$V_{\text{GS (off)}}$			P_{Q1} 																
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="margin-top: 10px; text-align: center;"> <p>(Draw a schematic diagram showing what is necessary to turn the transistor fully <i>off</i>)</p> <div style="border: 1px solid black; height: 150px; width: 100%; margin-top: 10px;"></div> </div>																			

Answer 38

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 38

I strongly recommend a value for R_1 of $1\text{ M}\Omega$ or more, to protect the JFET gate from overcurrent damage. The students will calculate their own dropping resistor value, based on the supply voltage and the LED ratings.

This exercise lends itself to experimentation with static electricity. The input impedance of an average JFET is so high that the LED may be made to turn on and off with just a touch of the probe wire to a charged object (such as a person).

Using only the components shown, students may not be able to get their JFETs to completely turn off. This is left for them as a challenge to figure out!

I expect students to be able to figure out how to calculate the transistor's power dissipation without being told what measurements to take!

Competency: Current-sinking MOSFET switch		Version:															
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="text-align: center; margin-top: 20px;"> </div>																	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <div style="display: flex; justify-content: space-around; margin-top: 10px;"> <div>$V_{\text{supply}} =$</div> <div>$R_{\text{bleed}} =$</div> <div>$R_{\text{dropping}} =$</div> </div>																	
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; border-collapse: collapse; margin-top: 10px;"> <thead> <tr> <th></th> <th style="text-align: center;">Predicted</th> <th style="text-align: center;">Measured</th> <th></th> <th style="text-align: center;">Calculated</th> </tr> </thead> <tbody> <tr> <td style="text-align: right;">I_{LED}</td> <td style="border: 1px solid black; width: 80px; height: 25px;"></td> <td style="border: 1px solid black; width: 80px; height: 25px;"></td> <td style="text-align: right;">$R_{\text{DS(on)}}$</td> <td style="border: 1px solid black; width: 80px; height: 25px;"></td> </tr> <tr> <td style="text-align: right;">I_{switch}</td> <td style="border: 1px solid black; width: 80px; height: 25px;"></td> <td style="border: 1px solid black; width: 80px; height: 25px;"></td> <td style="text-align: right;">P_{Q1}</td> <td style="border: 1px solid black; width: 80px; height: 25px;"></td> </tr> </tbody> </table>				Predicted	Measured		Calculated	I_{LED}			$R_{\text{DS(on)}}$		I_{switch}			P_{Q1}	
	Predicted	Measured		Calculated													
I_{LED}			$R_{\text{DS(on)}}$														
I_{switch}			P_{Q1}														
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Fault analysis</div> <div style="margin-top: 10px;"> <p>Suppose component fails <input type="checkbox"/> open <input type="checkbox"/> other _____</p> <p><input type="checkbox"/> shorted</p> <p><i>What will happen in the circuit?</i></p> <div style="height: 150px; border: 1px solid black; margin-top: 10px;"></div> </div>																	

Answer 39

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 39

I recommend a value for R1 of 1 M Ω or more, to show that the bleed resistor need not be very conductive to do its job well. The students will calculate their own dropping resistor value, based on the supply voltage and the LED ratings.

Students predict the LED current (approximately 20 mA) and the switch current (0 mA), and then calculate the transistor's "on" channel resistance and power dissipation after taking additional measurements. I expect students to be able to figure out how to calculate both these parameters without being told what measurements to take!

Competency: MOSFET switch circuit		Version:								
Description	Design and build a circuit that uses a switch to turn on an E-type MOSFET, which then turns on a DC load such as a light bulb or small electric motor. The switch must carry zero current, with the transistor carrying 100% of the load current.									
Given conditions	$V_{\text{supply}} =$									
Schematic										
Parameters	<table><tr><td></td><td>Measured</td><td></td></tr><tr><td>I_{load}</td><td><input type="text"/></td><td rowspan="2">Is $I_{\text{switch}} = 0 \text{ mA}$?</td></tr><tr><td>I_{switch}</td><td><input type="text"/></td></tr></table>			Measured		I_{load}	<input type="text"/>	Is $I_{\text{switch}} = 0 \text{ mA}$?	I_{switch}	<input type="text"/>
	Measured									
I_{load}	<input type="text"/>	Is $I_{\text{switch}} = 0 \text{ mA}$?								
I_{switch}	<input type="text"/>									

file 02424

Answer 40

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 40

Being able to design a circuit using a MOSFET as a switch is a valuable skill for technicians and engineers alike to have.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: JFET current regulator		Version:																				
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="text-align: center; margin-top: 20px;"> </div>																						
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <div style="display: flex; justify-content: space-around; margin-top: 10px;"> $V_{DD} =$ $R_1 =$ $R_{load} \text{ (max)} =$ </div>																						
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; border-collapse: collapse; margin-top: 10px;"> <thead> <tr> <th style="width: 15%;"></th> <th style="width: 20%; text-align: center;">Predicted</th> <th style="width: 20%; text-align: center;">Measured</th> <th style="width: 45%;"></th> </tr> </thead> <tbody> <tr> <td>I_{R1}</td> <td><input style="width: 100%;" type="text"/></td> <td><input style="width: 100%;" type="text"/></td> <td></td> </tr> <tr> <td>I_{load}</td> <td><input style="width: 100%;" type="text"/></td> <td><input style="width: 100%;" type="text"/></td> <td>(R_{load} set to mid-value)</td> </tr> <tr> <td>$R_{load(max)}$</td> <td><input style="width: 100%;" type="text"/></td> <td><input style="width: 100%;" type="text"/></td> <td>(Maximum R with I_{load} stable)</td> </tr> <tr> <td>$R_{load(min)}$</td> <td><input style="width: 100%;" type="text"/></td> <td><input style="width: 100%;" type="text"/></td> <td>(Minimum R with I_{load} stable)</td> </tr> </tbody> </table>				Predicted	Measured		I_{R1}	<input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>		I_{load}	<input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>	(R_{load} set to mid-value)	$R_{load(max)}$	<input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>	(Maximum R with I_{load} stable)	$R_{load(min)}$	<input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>	(Minimum R with I_{load} stable)
	Predicted	Measured																				
I_{R1}	<input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>																				
I_{load}	<input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>	(R_{load} set to mid-value)																			
$R_{load(max)}$	<input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>	(Maximum R with I_{load} stable)																			
$R_{load(min)}$	<input style="width: 100%;" type="text"/>	<input style="width: 100%;" type="text"/>	(Minimum R with I_{load} stable)																			

Answer 41

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 41

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: Common-drain class-A amplifier		Version:
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Schematic</div>		
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Given conditions</div>		
$V_{in} =$	$V_{DD} =$	$R_G =$
	$R_S =$	$C_1 =$
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Parameters</div>		
	Predicted	Measured
V_G (DC)		
V_{out} (AC)		
A_V		
<div style="display: flex; justify-content: space-between; align-items: center;"> <div> Inverting . . . <input style="width: 30px; height: 20px;" type="checkbox"/> or noninverting? <input style="width: 30px; height: 20px;" type="checkbox"/> </div> <div style="text-align: center;"> <i>Input and output waveforms (measured)</i> </div> </div>		

Answer 42

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 42

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between $1\text{ k}\Omega$ and $100\text{ k}\Omega$ (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k 47k, 68k, etc.). Use a sine-wave function generator to supply an audio-frequency input signal, and make sure its amplitude isn't set so high that the amplifier clips.



I have had good success using the following values:

- $V_{DD} = 9\text{ volts}$
- $V_{in} = 1\text{ volt (peak)}$, $f = 2\text{ kHz}$
- $R_G = 100\text{ k}\Omega$
- $R_S = 10\text{ k}\Omega$
- $C_1 = 0.47\text{ }\mu\text{F}$

Please note that the quiescent output voltage is impossible to precisely predict, as it depends on the particular characteristics of the JFET used (I_D versus V_{GS}). The fact that this circuit uses self-biasing instead of voltage divider biasing makes the situation worse. Predicting quiescent gate voltage, however should be extremely easy (0 volts) if one understands how JFETs function.

An interesting parameter to explore in this circuit is the effect of the source resistor value on voltage gain. The theoretical voltage gain of a simple common-drain amplifier circuit is unity (1), but this may be approximated only with relatively large load resistor (R_S) values. Try substituting a $1\text{ k}\Omega$ or less resistor for R_S , and notice what happens to the gain. Then, have your students explain why this happens!

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

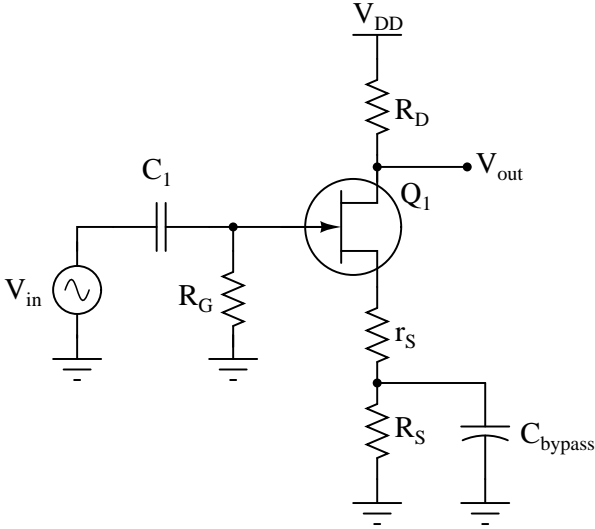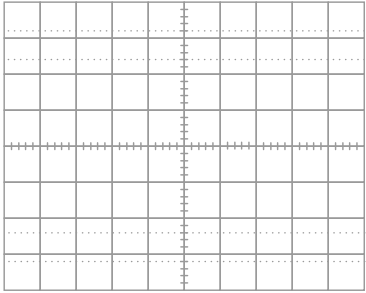Competency: Common-source class-A amplifier		Version:												
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> 														
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <table style="width: 100%; border-collapse: collapse;"> <tr> <td style="width: 20%;">$V_{in} =$</td> <td style="width: 20%;">$V_{DD} =$</td> <td style="width: 20%;">$R_G =$</td> <td style="width: 20%;">$R_D =$</td> <td style="width: 20%;">$C_1 =$</td> </tr> <tr> <td></td> <td></td> <td>$r_S =$</td> <td>$R_S =$</td> <td>$C_{bypass} =$</td> </tr> </table>			$V_{in} =$	$V_{DD} =$	$R_G =$	$R_D =$	$C_1 =$			$r_S =$	$R_S =$	$C_{bypass} =$		
$V_{in} =$	$V_{DD} =$	$R_G =$	$R_D =$	$C_1 =$										
		$r_S =$	$R_S =$	$C_{bypass} =$										
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="width: 20%;"></th> <th style="width: 20%; text-align: center;">Predicted</th> <th style="width: 20%; text-align: center;">Measured</th> </tr> </thead> <tbody> <tr> <td>V_G (DC)</td> <td style="border: 1px solid black; height: 20px;"></td> <td style="border: 1px solid black; height: 20px;"></td> </tr> <tr> <td>V_{out} (AC)</td> <td style="border: 1px solid black; height: 20px;"></td> <td style="border: 1px solid black; height: 20px;"></td> </tr> <tr> <td>A_V</td> <td style="border: 1px solid black; height: 20px;"></td> <td style="border: 1px solid black; height: 20px;"></td> </tr> </tbody> </table> <div style="margin-top: 20px;"> Inverting . . . <input type="checkbox"/> </div> <div style="margin-top: 5px;"> or noninverting? <input type="checkbox"/> </div> <div style="margin-top: 20px; text-align: right;"> <i>Input and output waveforms (measured)</i>  </div>				Predicted	Measured	V_G (DC)			V_{out} (AC)			A_V		
	Predicted	Measured												
V_G (DC)														
V_{out} (AC)														
A_V														

Answer 43

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 43

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between $1\text{ k}\Omega$ and $100\text{ k}\Omega$ (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k, 47k, 68k, etc.). Use a sine-wave function generator to supply an audio-frequency input signal, and make sure its amplitude isn't set so high that the amplifier clips.

I have had good success using the following values:

- $V_{DD} = 12\text{ volts}$
- $V_{in} = 0.5\text{ volt}$ (peak-to-peak), $f = 2\text{ kHz}$
- $R_G = 100\text{ k}\Omega$
- $r_S = 2.2\text{ k}\Omega$
- $R_S = 10\text{ k}\Omega$
- $R_D = 10\text{ k}\Omega$
- $C_1 = 0.47\text{ }\mu\text{F}$
- $C_{bypass} = 10\text{ }\mu\text{F}$

Please note that the quiescent output voltage is impossible to precisely predict, as it depends on the particular characteristics of the JFET used (I_D versus V_{GS}). The fact that this circuit uses self-biasing instead of voltage divider biasing makes the situation worse. Predicting quiescent gate voltage, however should be extremely easy (0 volts) if one understands how JFETs function.

All quiescent circuit values depend on V_{DD} , so if things aren't biased the way you would like, simply adjust the power supply voltage to suit.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: Class-A JFET amplifier w/specified phase Version:	
Description	Design and build a class-A JFET amplifier circuit with the phase (inverting or noninverting) specified.
Given conditions	$V_{in} =$ $+V =$ <input type="checkbox"/> Inverting <input type="checkbox"/> Noninverting
Schematic	<i>Show all component values!</i>
Parameters	Does the amplifier invert the waveform or not?

file 03879

Answer 44

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 44

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k Ω and 100 k Ω (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k 47k, 68k, etc.). Use a sine-wave function generator to supply an audio-frequency input signal, and make sure its amplitude isn't set so high that the amplifier clips.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: Class-A JFET amplifier w/specified gain Version:															
Description	<p>Design and build a class-A JFET amplifier circuit with a voltage gain (A_v) that is within tolerance of the gain specified.</p>														
Given conditions	$V_{in} =$ $+V =$ $A_v =$ Tolerance $A_v =$														
Schematic	<i>Show all component values!</i>														
<div> <div>Parameters</div> <div> <table> <tr> <td></td> <td>Measured</td> <td></td> <td>Calculated</td> <td></td> </tr> <tr> <td>V_{in}</td> <td><input type="text"/></td> <td>A_v</td> <td><input type="text"/></td> <td rowspan="2"> $\frac{A_{v(\text{actual})} - A_{v(\text{ideal})}}{A_{v(\text{ideal})}} \times 100\%$ </td> </tr> <tr> <td>V_{out}</td> <td><input type="text"/></td> <td>Error A_v</td> <td><input type="text"/></td> </tr> </table> </div> </div>			Measured		Calculated		V_{in}	<input type="text"/>	A_v	<input type="text"/>	$\frac{A_{v(\text{actual})} - A_{v(\text{ideal})}}{A_{v(\text{ideal})}} \times 100\%$	V_{out}	<input type="text"/>	Error A_v	<input type="text"/>
	Measured		Calculated												
V_{in}	<input type="text"/>	A_v	<input type="text"/>	$\frac{A_{v(\text{actual})} - A_{v(\text{ideal})}}{A_{v(\text{ideal})}} \times 100\%$											
V_{out}	<input type="text"/>	Error A_v	<input type="text"/>												

file 01936

Answer 45

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 45

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k Ω and 100 k Ω (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k 47k, 68k, etc.). Use a sine-wave function generator to supply an audio-frequency input signal, and make sure its amplitude isn't set so high that the amplifier clips at the specified gain.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: Class-A transistor amplifier w/specified phase	
Description	Design and build a class-A transistor amplifier circuit with the phase (inverting or noninverting) specified.
Given conditions	$V_{in} =$ $+V =$ <input type="checkbox"/> Inverting <input type="checkbox"/> Noninverting
Schematic	<i>Show all component values!</i>
Parameters	Does the amplifier invert the waveform or not?

file 03884

Answer 46

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 46

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k Ω and 100 k Ω (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k 47k, 68k, etc.). Use a sine-wave function generator to supply an audio-frequency input signal, and make sure its amplitude isn't set so high that the amplifier clips.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: BJT multivibrator circuit, astable		Version:
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Schematic</div>		
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Given conditions</div>		
$V_{CC} =$	$R_1 =$	$R_2 =$
	$R_4 =$	$R_3 =$
$C_1 =$		$C_2 =$
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Parameters</div>		
Duty Cycle (at Q_1 collector)	<div style="border: 1px solid black; display: inline-block; width: 100px; height: 30px; margin-bottom: 5px;"></div> Predicted	<div style="border: 1px solid black; display: inline-block; width: 100px; height: 30px; margin-bottom: 5px;"></div> Measured
Potentiometer turned fully clockwise		
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Fault analysis</div>		
Suppose component fails <div style="display: inline-block; vertical-align: middle; margin-left: 10px;"> <input type="checkbox"/> open <input type="checkbox"/> shorted </div> <div style="display: inline-block; vertical-align: middle; margin-left: 20px;"> <input type="checkbox"/> other _____ </div>		
<i>What will happen in the circuit?</i>		

Answer 47

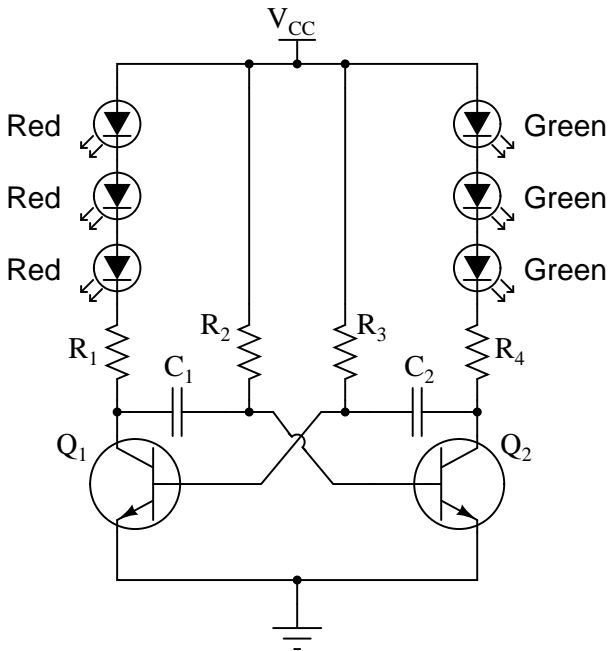
Use circuit simulation software to verify your predicted and measured parameter values.

Notes 47

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between $1\text{ k}\Omega$ and $100\text{ k}\Omega$ (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k 47k, 68k, etc.).

This circuit produces nice, sharp-edged square wave signals at the transistor collector terminals when resistors R_1 and R_4 are substantially smaller than resistors R_2 and R_3 . This way, R_2 and R_3 dominate the capacitors' charging times, making calculation of duty cycle much more accurate. Component values I've used with success are $1\text{ k}\Omega$ for R_1 and R_4 , $100\text{ k}\Omega$ for R_2 and R_3 , and $0.1\text{ }\mu\text{F}$ for C_1 and C_2 .

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: BJT multivibrator circuit, astable		Version:									
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> 											
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <div style="display: flex; justify-content: space-around; margin-top: 10px;"> <div>$V_{CC} =$</div> <div>$R_1 =$</div> <div>$R_2 =$</div> <div>$C_1 =$</div> </div> <div style="display: flex; justify-content: space-around; margin-top: 10px;"> <div>$R_4 =$</div> <div>$R_3 =$</div> <div>$C_2 =$</div> </div>											
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; border-collapse: collapse; margin-top: 10px;"> <thead> <tr> <th style="width: 35%;"></th> <th style="width: 20%; text-align: center;">Predicted</th> <th style="width: 20%; text-align: center;">Measured</th> </tr> </thead> <tbody> <tr> <td>t_{on} (red LED)</td> <td style="border: 1px solid black; height: 20px;"></td> <td style="border: 1px solid black; height: 20px;"></td> </tr> <tr> <td>t_{on} (green LED)</td> <td style="border: 1px solid black; height: 20px;"></td> <td style="border: 1px solid black; height: 20px;"></td> </tr> </tbody> </table>				Predicted	Measured	t_{on} (red LED)			t_{on} (green LED)		
	Predicted	Measured									
t_{on} (red LED)											
t_{on} (green LED)											

Answer 48

Use circuit simulation software to verify your predicted and measured parameter values.


Notes 48

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k Ω and 100 k Ω (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k 47k, 68k, etc.).

This circuit produces nice, sharp-edged square wave signals at the transistor collector terminals when resistors R_1 and R_4 are substantially smaller than resistors R_2 and R_3 . This way, R_2 and R_3 dominate the capacitors' charging times, making calculation of duty cycle much more accurate. Component values I've used with success are 470 Ω for R_1 and R_4 , 270 k Ω for R_2 and R_3 , 4.7 μ F for C_1 and C_2 , and 6 to 14 volts for V_{CC} . The frequency of this circuit *does* vary with supply voltage, so don't expect perfect agreement between predicted and measured values.

By the way, this circuit works very well for holiday flashing lights – decorate your lab room accordingly with student-built light flashers!

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

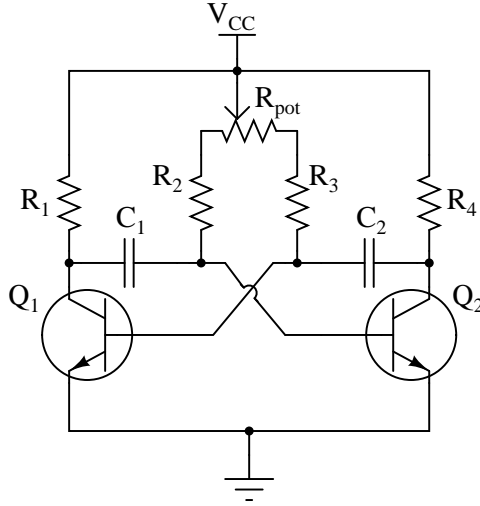Competency: BJT multivibrator w/ variable duty cycle		Version:								
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> 										
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <p> $V_{CC} =$ $R_1 =$ $R_2 =$ $R_{pot} =$ $C_1 =$ $R_4 =$ $R_3 =$ $C_2 =$ </p>										
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="width: 30%;"></th> <th style="width: 15%; text-align: center;">Predicted</th> <th style="width: 15%; text-align: center;">Measured</th> <th style="width: 40%;"></th> </tr> </thead> <tbody> <tr> <td>Duty Cycle (at Q_1 collector)</td> <td style="text-align: center;"><div style="border: 1px solid black; width: 60px; height: 20px; margin: 0 auto;"></div></td> <td style="text-align: center;"><div style="border: 1px solid black; width: 60px; height: 20px; margin: 0 auto;"></div></td> <td>Potentiometer turned fully clockwise</td> </tr> </tbody> </table>				Predicted	Measured		Duty Cycle (at Q_1 collector)	<div style="border: 1px solid black; width: 60px; height: 20px; margin: 0 auto;"></div>	<div style="border: 1px solid black; width: 60px; height: 20px; margin: 0 auto;"></div>	Potentiometer turned fully clockwise
	Predicted	Measured								
Duty Cycle (at Q_1 collector)	<div style="border: 1px solid black; width: 60px; height: 20px; margin: 0 auto;"></div>	<div style="border: 1px solid black; width: 60px; height: 20px; margin: 0 auto;"></div>	Potentiometer turned fully clockwise							
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Fault analysis</div> <p>Suppose component <div style="border: 1px solid black; width: 50px; height: 20px; display: inline-block; vertical-align: middle;"></div> fails <input type="checkbox"/> open <input type="checkbox"/> other _____ <input type="checkbox"/> shorted</p> <p><i>What will happen in the circuit?</i></p> <div style="height: 150px; border: 1px solid black; margin-top: 10px;"></div>										

Answer 49

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 49

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k Ω and 100 k Ω (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k 47k, 68k, etc.).

This circuit produces nice, sharp-edged square wave signals at the transistor collector terminals when resistors R_1 and R_4 are substantially smaller than the combined resistance of resistors R_2 and R_3 and the respective potentiometer section resistances. This way, R_{pot} , R_2 , and R_3 dominate the capacitors' charging times, making calculation of duty cycle much more accurate. Component values I've used with success are 1 k Ω for R_1 and R_4 , 10 k Ω for R_2 and R_3 , 100 k Ω for R_{pot} , and 0.001 μ F for C_1 and C_2 .

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: BJT multivibrator w/ variable duty cycle		Version:
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> <div style="text-align: center; margin-top: 20px;"> </div>		
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <div style="display: flex; flex-wrap: wrap; justify-content: space-around; margin-top: 10px;"> <div style="width: 15%;">$V_{CC} =$</div> <div style="width: 15%;">$R_1 =$</div> <div style="width: 15%;">$R_2 =$</div> <div style="width: 15%;">$R_{pot} =$</div> <div style="width: 15%;">$C_1 =$</div> <div style="width: 15%;">$R_4 =$</div> <div style="width: 15%;">$R_3 =$</div> <div style="width: 15%;">$C_2 =$</div> </div> <div style="margin-top: 10px;">$\text{Duty cycle (D)} =$</div>		
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <div style="display: flex; justify-content: space-between; align-items: flex-start; margin-top: 10px;"> <div style="width: 40%;"> <p style="margin-bottom: 10px;">Duty Cycle (at Q_1 collector)</p> <div style="display: flex; align-items: center;"> <div style="margin-right: 10px;">Measured</div> <div style="border: 1px solid black; width: 100px; height: 30px;"></div> </div> </div> <div style="width: 55%;"> <p style="margin-bottom: 10px;">Waveform at specified D</p> </div> </div>		

file 02607

Answer 50

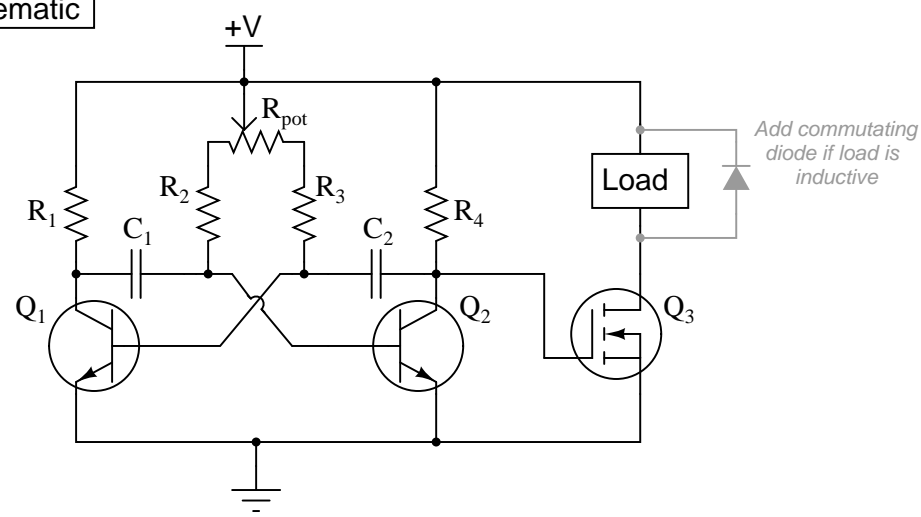
Use circuit simulation software to verify your predicted and measured parameter values.

Notes 50

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k Ω and 100 k Ω (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k 47k, 68k, etc.).

This circuit produces nice, sharp-edged square wave signals at the transistor collector terminals when resistors R_1 and R_4 are substantially smaller than the combined resistance of resistors R_2 and R_3 and the respective potentiometer section resistances. This way, R_{pot} , R_2 , and R_3 dominate the capacitors' charging times, making calculation of duty cycle much more accurate. Component values I've used with success are 1 k Ω for R_1 and R_4 , 10 k Ω for R_2 and R_3 , 100 k Ω for R_{pot} , and 0.001 μ F for C_1 and C_2 .

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: PWM power controller, discrete		Version:																				
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> 																						
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <p style="margin-top: 10px;"> $+V =$ $R_1 =$ $R_2 =$ $R_{pot} =$ $C_1 =$ $R_4 =$ $R_3 =$ $C_2 =$ </p>																						
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="width: 30%;"></th> <th style="width: 15%; text-align: center;">Predicted</th> <th style="width: 15%; text-align: center;">Measured</th> <th style="width: 40%;"></th> </tr> </thead> <tbody> <tr> <td>$V_{load} \text{ (avg.)}$</td> <td style="border: 1px solid black; height: 25px;"></td> <td style="border: 1px solid black; height: 25px;"></td> <td>Duty cycle = ____ %</td> </tr> <tr> <td>$V_{load} \text{ (avg.)}$</td> <td style="border: 1px solid black; height: 25px;"></td> <td style="border: 1px solid black; height: 25px;"></td> <td>Duty cycle = ____ %</td> </tr> <tr> <td>$V_{load} \text{ (avg.)}$</td> <td style="border: 1px solid black; height: 25px;"></td> <td style="border: 1px solid black; height: 25px;"></td> <td>Duty cycle = ____ %</td> </tr> <tr> <td>$V_{load} \text{ (avg.)}$</td> <td style="border: 1px solid black; height: 25px;"></td> <td style="border: 1px solid black; height: 25px;"></td> <td>Duty cycle = ____ %</td> </tr> </tbody> </table>				Predicted	Measured		$V_{load} \text{ (avg.)}$			Duty cycle = ____ %	$V_{load} \text{ (avg.)}$			Duty cycle = ____ %	$V_{load} \text{ (avg.)}$			Duty cycle = ____ %	$V_{load} \text{ (avg.)}$			Duty cycle = ____ %
	Predicted	Measured																				
$V_{load} \text{ (avg.)}$			Duty cycle = ____ %																			
$V_{load} \text{ (avg.)}$			Duty cycle = ____ %																			
$V_{load} \text{ (avg.)}$			Duty cycle = ____ %																			
$V_{load} \text{ (avg.)}$			Duty cycle = ____ %																			

file 01991

Answer 51

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 51

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k Ω and 100 k Ω (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k 47k, 68k, etc.).

This circuit produces nice, sharp-edged square wave signals at the transistor collector terminals when resistors R_1 and R_4 are substantially smaller than the combined resistance of resistors R_2 and R_3 and the respective potentiometer section resistances. This way, R_{pot} , R_2 , and R_3 dominate the capacitors' charging times, making calculation of duty cycle much more accurate. Component values I've used with success are 1 k Ω for R_1 and R_4 , 10 k Ω for R_2 and R_3 , 100 k Ω for R_{pot} , and 0.001 μ F for C_1 and C_2 . In my prototype circuit, I used 2N2222 bipolar transistors and an IRF510 power MOSFET.

Although small DC motors work well as demonstrative loads, their counter-EMF may wreak havoc with measurements of average load voltage. Purely resistive loads work best when comparing measured average load voltage against predicted average load voltage. Also, motors and other inductive loads may cause the MOSFET to switch incorrectly (or not switch at all!) unless a commutating diode is installed to limit the voltage induced by the collapsing magnetic field every time the transistor turns off.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: Oscillator/waveshaper/amplifier circuit		Version:																										
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div>																												
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <table style="width: 100%; border-collapse: collapse;"> <tr> <td style="width: 15%; vertical-align: top;">$-V =$</td> <td style="width: 15%;">$R_1 =$</td> <td style="width: 15%;">$R_6 =$</td> <td style="width: 15%;">$C_1 =$</td> <td style="width: 15%;">$C_5 =$</td> </tr> <tr> <td></td> <td>$R_2 =$</td> <td>$R_7 =$</td> <td>$C_2 =$</td> <td>$C_6 =$</td> </tr> <tr> <td></td> <td>$R_3 =$</td> <td>$R_8 =$</td> <td>$C_3 =$</td> <td>$C_7 =$</td> </tr> <tr> <td></td> <td>$R_4 =$</td> <td>$R_9 =$</td> <td>$C_4 =$</td> <td></td> </tr> <tr> <td></td> <td>$R_5 =$</td> <td>$R_{pot} =$</td> <td></td> <td></td> </tr> </table>				$-V =$	$R_1 =$	$R_6 =$	$C_1 =$	$C_5 =$		$R_2 =$	$R_7 =$	$C_2 =$	$C_6 =$		$R_3 =$	$R_8 =$	$C_3 =$	$C_7 =$		$R_4 =$	$R_9 =$	$C_4 =$			$R_5 =$	$R_{pot} =$		
$-V =$	$R_1 =$	$R_6 =$	$C_1 =$	$C_5 =$																								
	$R_2 =$	$R_7 =$	$C_2 =$	$C_6 =$																								
	$R_3 =$	$R_8 =$	$C_3 =$	$C_7 =$																								
	$R_4 =$	$R_9 =$	$C_4 =$																									
	$R_5 =$	$R_{pot} =$																										
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="width: 15%;"></th> <th style="width: 15%;">Predicted waveshape</th> <th style="width: 15%;">Measured waveshape</th> <th style="width: 15%;">Predicted waveshape</th> <th style="width: 15%;">Measured waveshape</th> </tr> </thead> <tbody> <tr> <td>$V_{C(Q2)}$</td> <td><div style="border: 1px solid black; height: 20px; width: 100%;"></div></td> <td><div style="border: 1px solid black; height: 20px; width: 100%;"></div></td> <td>V_{C4}</td> <td><div style="border: 1px solid black; height: 20px; width: 100%;"></div></td> </tr> <tr> <td>$V_{B(Q2)}$</td> <td><div style="border: 1px solid black; height: 20px; width: 100%;"></div></td> <td><div style="border: 1px solid black; height: 20px; width: 100%;"></div></td> <td>V_{R7}</td> <td><div style="border: 1px solid black; height: 20px; width: 100%;"></div></td> </tr> <tr> <td>V_{C3}</td> <td><div style="border: 1px solid black; height: 20px; width: 100%;"></div></td> <td><div style="border: 1px solid black; height: 20px; width: 100%;"></div></td> <td>V_{out}</td> <td><div style="border: 1px solid black; height: 20px; width: 100%;"></div></td> </tr> </tbody> </table>					Predicted waveshape	Measured waveshape	Predicted waveshape	Measured waveshape	$V_{C(Q2)}$	<div style="border: 1px solid black; height: 20px; width: 100%;"></div>	<div style="border: 1px solid black; height: 20px; width: 100%;"></div>	V_{C4}	<div style="border: 1px solid black; height: 20px; width: 100%;"></div>	$V_{B(Q2)}$	<div style="border: 1px solid black; height: 20px; width: 100%;"></div>	<div style="border: 1px solid black; height: 20px; width: 100%;"></div>	V_{R7}	<div style="border: 1px solid black; height: 20px; width: 100%;"></div>	V_{C3}	<div style="border: 1px solid black; height: 20px; width: 100%;"></div>	<div style="border: 1px solid black; height: 20px; width: 100%;"></div>	V_{out}	<div style="border: 1px solid black; height: 20px; width: 100%;"></div>					
	Predicted waveshape	Measured waveshape	Predicted waveshape	Measured waveshape																								
$V_{C(Q2)}$	<div style="border: 1px solid black; height: 20px; width: 100%;"></div>	<div style="border: 1px solid black; height: 20px; width: 100%;"></div>	V_{C4}	<div style="border: 1px solid black; height: 20px; width: 100%;"></div>																								
$V_{B(Q2)}$	<div style="border: 1px solid black; height: 20px; width: 100%;"></div>	<div style="border: 1px solid black; height: 20px; width: 100%;"></div>	V_{R7}	<div style="border: 1px solid black; height: 20px; width: 100%;"></div>																								
V_{C3}	<div style="border: 1px solid black; height: 20px; width: 100%;"></div>	<div style="border: 1px solid black; height: 20px; width: 100%;"></div>	V_{out}	<div style="border: 1px solid black; height: 20px; width: 100%;"></div>																								

file 02507

Answer 52

Use circuit simulation software to verify your predicted and measured parameter values.

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k Ω and 100 k Ω (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k 47k, 68k, etc.).

This circuit demonstrates the use of passive integrators to convert a square wave into a pseudo-sine wave output. The multivibrator portion produces nice, sharp-edged square wave signals at the transistor collector terminals when resistors R_1 and R_4 are substantially smaller than resistors R_2 and R_3 . Component values I've used with success are 1 k Ω for R_1 and R_4 , 100 k Ω for R_2 and R_3 , and 0.001 μ F for C_1 and C_2 .

Resistors R_5 and R_6 , along with capacitors C_3 and C_4 , form a dual passive integrator network to re-shape the square-wave output of the multivibrator into a pseudo-sine wave. These components' values must be chosen according to the multivibrator frequency, so that the integration is realistic without the attenuation being excessive. Integrator component values that have worked well for the multivibrator components previously specified are 10 k Ω for R_5 and R_6 , and 0.1 μ F for C_3 and C_4 .


Transistor Q_3 is just an emitter follower, placed there to give the amplifier section a high input impedance. Q_3 's emitter resistor value is not critical. I have used a 1 k Ω resistor for R_7 with good success.

The last transistor (Q_4) is for voltage amplification. A "trimmer" style potentiometer (10 k Ω recommended for R_{pot}) provides easy adjustment of biasing for different supply voltages. Using the potentiometer, I have operated this circuit on supply voltages ranging from -6 volts to -27 volts. Use a bypass capacitor (C_7) large enough that its reactance at the operating frequency is negligible (less than 1 ohm is good), such as 33 μ F. Resistor values I've used with success are 10 k Ω for R_8 and 4.7 k Ω for R_9 . Coupling capacitor values are not terribly important, so long as they present minimal reactance at the operating frequency. I have used 0.47 μ F for both C_5 and C_6 with good success.

You may find that the relatively high operating frequency of this circuit complicates matters with regard to parasitic capacitances. The fast rise and fall times of the strong square wave tend to couple easily to the sine-wave portions of the circuit, especially when the sine wave signal is so severely attenuated by the double integrators. One solution to this dilemma is to lower the operating frequency of the circuit, allowing a lower cutoff frequency for the double integrator (two-pole lowpass filter) section which in turn will improve the signal-to-noise ratio throughout. If you wish to try this, you may use these suggested component values:

- $R_1 = 1 \text{ k}\Omega$
- $R_2 = 100 \text{ k}\Omega$
- $R_3 = 100 \text{ k}\Omega$
- $R_4 = 1 \text{ k}\Omega$
- $R_5 = 100 \text{ k}\Omega$
- $R_6 = 100 \text{ k}\Omega$
- $R_7 = 1 \text{ k}\Omega$
- $R_8 = 10 \text{ k}\Omega$
- $R_9 = 4.7 \text{ k}\Omega$
- $R_{pot} = 10 \text{ k}\Omega$
- $C_1 = 0.047 \text{ }\mu\text{F}$
- $C_2 = 0.047 \text{ }\mu\text{F}$
- $C_3 = 0.1 \text{ }\mu\text{F}$
- $C_4 = 0.047 \text{ }\mu\text{F}$
- $C_5 = 1 \text{ }\mu\text{F}$
- $C_6 = 1 \text{ }\mu\text{F}$
- $C_7 = 33 \text{ }\mu\text{F}$

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

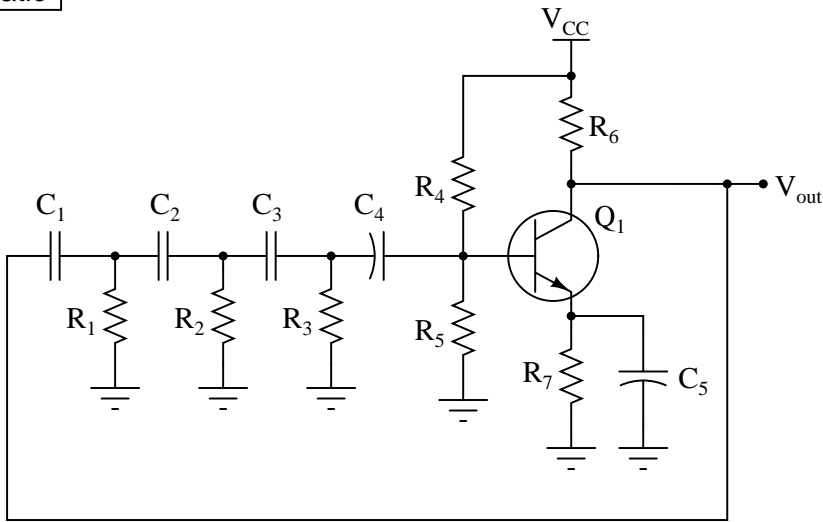Competency: RC phase-shift oscillator, BJT		Version:									
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> 											
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <table style="width: 100%; border-collapse: collapse;"> <tr> <td style="width: 33%;">$V_{CC} =$</td> <td style="width: 33%;">$C_1 = C_2 = C_3 =$</td> <td style="width: 33%;">$C_4 = C_5 =$</td> </tr> <tr> <td></td> <td>$R_1 = R_2 = R_3 =$</td> <td>$R_4 = \quad R_5 =$</td> </tr> <tr> <td></td> <td></td> <td>$R_6 = \quad R_7 =$</td> </tr> </table>			$V_{CC} =$	$C_1 = C_2 = C_3 =$	$C_4 = C_5 =$		$R_1 = R_2 = R_3 =$	$R_4 = \quad R_5 =$			$R_6 = \quad R_7 =$
$V_{CC} =$	$C_1 = C_2 = C_3 =$	$C_4 = C_5 =$									
	$R_1 = R_2 = R_3 =$	$R_4 = \quad R_5 =$									
		$R_6 = \quad R_7 =$									
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="width: 10%;"></th> <th style="width: 40%; text-align: center;">Predicted</th> <th style="width: 50%; text-align: center;">Measured</th> </tr> </thead> <tbody> <tr> <td>f_{out}</td> <td style="border: 1px solid black; height: 20px;"></td> <td style="border: 1px solid black; height: 20px;"></td> </tr> </tbody> </table>				Predicted	Measured	f_{out}					
	Predicted	Measured									
f_{out}											
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Fault analysis</div> <p>Suppose component fails <input type="checkbox"/> open <input type="checkbox"/> other _____ <input type="checkbox"/> shorted </p> <p><i>What will happen in the circuit?</i></p>											

file 01950

Answer 53

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 53

Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k Ω and 100 k Ω (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k 47k, 68k, etc.).


I have had relatively good success with the following values:

- $V_{CC} = 9$ volts (from battery)
- C_1 through $C_3 = 0.001 \mu\text{F}$
- C_4 and $C_5 = 4.7 \mu\text{F}$
- R_1 through $R_3 = 10 \text{ k}\Omega$
- $R_4 = 270 \text{ k}\Omega$
- $R_5 = 50 \text{ k}\Omega$ (two 100 k Ω resistors in parallel)
- $R_6 = 12 \text{ k}\Omega$ (you might want to make this resistor variable so students can experiment with A_V)
- $R_7 = 1 \text{ k}\Omega$
- $Q_1 =$ part number 2N3403

One of the problems with the RC phase-shift oscillator circuit design is the loading of the phase-shift network by the transistor's biasing network (R_4 and R_5), which will offset the predicted oscillation frequency from what you might expect from the RC network alone. While it is possible to account for all the factors in this circuit, it is not a simple task for students just beginning to understand how the circuit is supposed to work.

I have also noticed that the frequency of this circuit is significantly reduced by the capacitance of any test leads connected to it. Beware of oscilloscope probe cables – the capacitance they add to the circuit will offset the oscillation frequency!

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

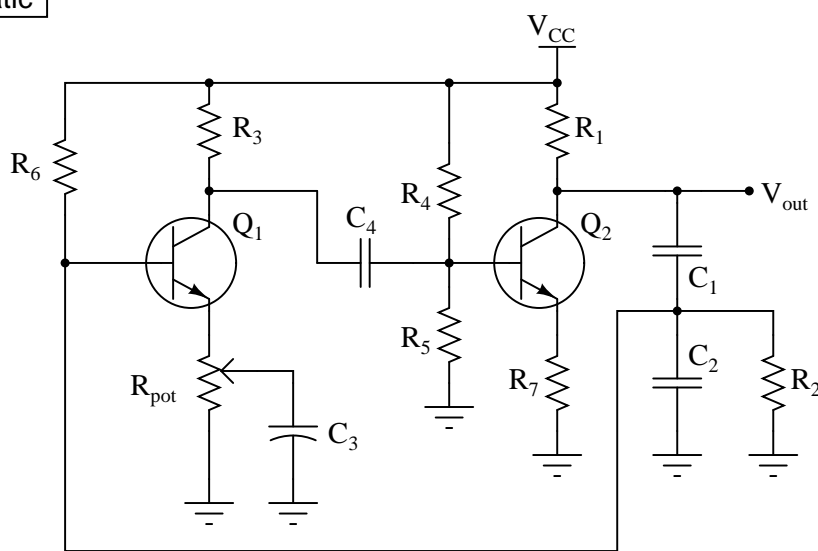Competency: Wien bridge oscillator, BJT		Version:												
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> 														
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <table style="width: 100%; border-collapse: collapse;"> <tr> <td style="width: 25%; text-align: right;">$V_{CC} =$</td> <td style="width: 25%; text-align: right;">$C_1 = C_2 =$</td> <td style="width: 25%; text-align: right;">$C_3 =$</td> <td style="width: 25%; text-align: right;">$C_4 =$</td> </tr> <tr> <td style="text-align: right;">$R_1 = R_2 =$</td> <td style="text-align: right;">$R_3 =$</td> <td style="text-align: right;">$R_4 =$</td> <td style="text-align: right;">$R_5 =$</td> </tr> <tr> <td style="text-align: right;">$R_6 =$</td> <td style="text-align: right;">$R_7 =$</td> <td style="text-align: right;">$R_{pot} =$</td> <td></td> </tr> </table>			$V_{CC} =$	$C_1 = C_2 =$	$C_3 =$	$C_4 =$	$R_1 = R_2 =$	$R_3 =$	$R_4 =$	$R_5 =$	$R_6 =$	$R_7 =$	$R_{pot} =$	
$V_{CC} =$	$C_1 = C_2 =$	$C_3 =$	$C_4 =$											
$R_1 = R_2 =$	$R_3 =$	$R_4 =$	$R_5 =$											
$R_6 =$	$R_7 =$	$R_{pot} =$												
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="width: 10%;"></th> <th style="width: 20%; text-align: center;">Predicted</th> <th style="width: 20%; text-align: center;">Measured</th> </tr> </thead> <tbody> <tr> <td style="text-align: right;">f_{out}</td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> <td style="border: 1px solid black; width: 100px; height: 30px;"></td> </tr> </tbody> </table>				Predicted	Measured	f_{out}								
	Predicted	Measured												
f_{out}														
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Fault analysis</div> <p>Suppose component fails <input type="checkbox"/> open <input type="checkbox"/> other _____</p> <p><input type="checkbox"/> shorted</p> <p><i>What will happen in the circuit?</i></p>														

Answer 54

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 54


Use a variable-voltage, regulated power supply to supply any amount of DC voltage below 30 volts. Specify standard resistor values, all between 1 k Ω and 100 k Ω (1k5, 2k2, 2k7, 3k3, 4k7, 5k1, 6k8, 10k, 22k, 33k, 39k, 47k, 68k, etc.).

R_{pot} serves the purpose of providing variable AC gain in the first amplifier stage to meet the Barkhausen criterion.

I have had good success with the following values:

- $V_{CC} = 12$ volts
- C_1 and $C_2 = 0.001$ μ F
- $C_3 = 47$ μ F
- $C_4 = 0.47$ μ F
- R_1 and $R_2 = 4.7$ k Ω
- $R_3 = 4.7$ k Ω
- $R_4 = 39$ k Ω
- $R_5 = 22$ k Ω
- $R_6 = 27$ k Ω
- $R_7 = 3.3$ k Ω
- $R_{pot} = 10$ k Ω , linear
- Q_1 and $Q_2 =$ part number 2N2222

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

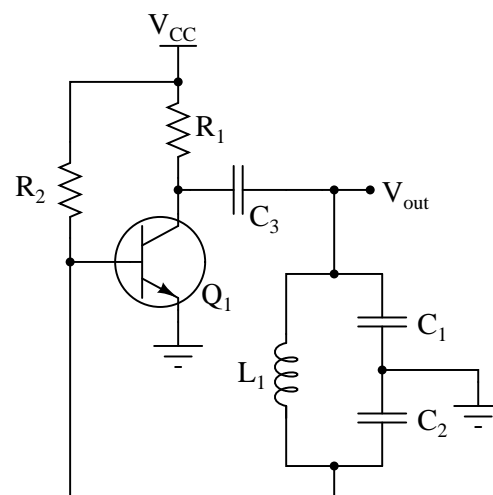Competency: Colpitts oscillator, BJT		Version:						
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Schematic</div> 								
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Given conditions</div> <div style="display: flex; justify-content: space-around; margin-top: 10px;"> <div>$V_{CC} =$</div> <div>$C_1 = C_2 =$</div> <div>$L_1 =$</div> <div>$C_3 =$</div> </div> <div style="display: flex; justify-content: space-around; margin-top: 10px;"> <div>$R_1 =$</div> <div>$R_2 =$</div> </div>								
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Parameters</div> <table style="width: 100%; border-collapse: collapse; margin-top: 10px;"> <thead> <tr> <th style="width: 10%;"></th> <th style="width: 20%; text-align: center;">Predicted</th> <th style="width: 20%; text-align: center;">Measured</th> </tr> </thead> <tbody> <tr> <td>f_{out}</td> <td style="border: 1px solid black; height: 20px;"></td> <td style="border: 1px solid black; height: 20px;"></td> </tr> </tbody> </table>				Predicted	Measured	f_{out}		
	Predicted	Measured						
f_{out}								
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px; margin-bottom: 5px;">Fault analysis</div> <div style="margin-top: 10px;"> Suppose component fails <div style="display: inline-block; vertical-align: middle; margin-left: 10px;"> <input type="checkbox"/> open <input type="checkbox"/> other _____ <input type="checkbox"/> shorted </div> </div> <p style="margin-top: 10px;"><i>What will happen in the circuit?</i></p> <div style="height: 150px; border: 1px solid black; margin-top: 10px;"></div>								

Answer 55

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 55

I have had great success with the following values:

- $V_{CC} = 7$ to 24 volts
- C_1 and $C_2 = 0.22 \mu\text{F}$
- $C_3 = 0.47 \mu\text{F}$
- $L_1 = 100 \mu\text{H}$ (ferrite core RF choke)
- $R_1 = 22 \text{ k}\Omega$
- $R_2 = 1.5 \text{ M}\Omega$
- $Q_1 =$ part number 2N3403

With these component values, the output waveform was quite clean and the frequency was very close to predicted:

$$f_{out} = \frac{1}{2\pi\sqrt{\frac{LC_1C_2}{C_1+C_2}}}$$

You might want to quiz your students on the purpose of resistor R_2 , since it usually only has to be present at power-up to initiate oscillation!

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: Hartley oscillator, series-fed BJT		Version:
Schematic		
Given conditions		
$V_{CC} =$	$C_1 =$	$L_{\text{primary}} =$
	$R_1 =$	$C_2 =$
Parameters		
Predicted	Measured	
f_{out}	<input style="width: 100px; height: 20px;" type="text"/>	<input style="width: 100px; height: 20px;" type="text"/>
Fault analysis		
Suppose component <input style="width: 50px; height: 20px;" type="text"/> fails <input type="checkbox"/> open <input type="checkbox"/> other _____ <input type="checkbox"/> shorted What will happen in the circuit? 		

file 01965

Answer 56

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 56

I have had success with the following values:

- $V_{CC} = 12$ to 24 volts
- $C_1 = 0.47 \mu\text{F}$
- $C_2 = 0.47 \mu\text{F}$
- $T_1 = 1000:8 \Omega$ audio matching transformer (used as center-tap inductor)
- $R_1 = 1.5 \text{ M}\Omega$
- $Q_1 =$ part number 2N3403

Capacitors C_1 and C_2 need not be equal value, since they serve entirely different purposes: C_1 is the tank circuit capacitance, while C_2 is merely a coupling capacitor. I just happened to be blessed with an abundance of $0.47 \mu\text{F}$ capacitors when I prototyped this circuit, so I chose that value for both capacitors!

With these component values, the output waveform I measured was not very sinusoidal, but at least it was oscillating. The harmonic output of a Hartley oscillator is substantially greater than a Colpitts, primary because the two capacitors in the Colpitts design act as decoupling capacitances, shunting high-order harmonic signals to ground.

Of course, in order to predict the frequency of oscillation in this Hartley oscillator circuit, you must know the inductance of the audio transformer's primary winding!

You might want to quiz your students on the purpose of resistor R_1 , since it usually only has to be present at power-up to initiate oscillation!

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: BJT oscillator w/specified frequency		Version:
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Description</div>		
Design and build a BJT oscillator circuit to output a <i>sine-wave</i> AC voltage at a frequency within the specified tolerance.		
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Given conditions</div>		
<div style="display: flex; justify-content: space-around; align-items: center;"> +V = f = Tolerance_f = </div>		
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Schematic</div>		
<i>Show all component values!</i>		
<div style="border: 1px solid black; display: inline-block; padding: 2px 5px;">Parameters</div>		
<div style="display: flex; justify-content: space-between; align-items: flex-start;"> <div style="text-align: center;"> Measured f </div> <div style="text-align: center;"> Calculated Error_f </div> <div style="text-align: center;"> $\frac{f_{(actual)} - f_{(ideal)}}{f_{(ideal)}} \times 100\%$ </div> </div>		

file 01949

Answer 57

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 57

Students are free to choose any oscillator design that meets the criteria: sinusoidal output at a specified frequency.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: AM radio transmitter		Version:
Schematic		
Given conditions		
$+V =$	$C_1 = C_2 =$	$L_1 =$
$V_{\text{signal}} =$	$R_1 =$	$R_2 =$
$f_{\text{signal}} =$	$R_3 =$	$R_4 =$
Parameters		
f_{out}	<div style="display: flex; justify-content: space-around;"> <div style="text-align: center;"> Predicted <input style="width: 80px; height: 20px;" type="text"/> </div> <div style="text-align: center;"> Measured <input style="width: 80px; height: 20px;" type="text"/> </div> </div>	Oscilloscope display of modulation
Audio signal can be heard on AM radio <input style="width: 30px; height: 20px;" type="checkbox"/>		

file 01953

Answer 58

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 58

I have had great success with the following values:



- $+V = 7$ to 24 volts
- C_1 and $C_2 = 0.001 \mu\text{F}$
- C_3, C_4 , and $C_5 = 0.47 \mu\text{F}$
- $L_1 = 100 \mu\text{H}$ (ferrite core RF choke)
- $R_1 = 22 \text{ k}\Omega$
- $R_2 = 1.5 \text{ M}\Omega$
- $R_3 = 6.8 \text{ k}\Omega$
- $R_4 = 100 \text{ k}\Omega$
- $Q_1 =$ part number 2N3403
- $Q_2 =$ part number MPF 102

With these component values, the carrier waveform was quite clean and the frequency was almost exactly 700 kHz:

$$f_{out} = \frac{1}{2\pi\sqrt{\frac{LC_1C_2}{C_1+C_2}}}$$

Modulation isn't that great, due to the crude nature of the circuit, but it is certainly good enough to hear over an appropriately tuned AM radio. Setting V_{signal} and f_{signal} is a matter of experimentation, to achieve the desired degree of modulation and tone pitch.

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

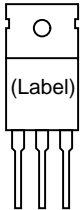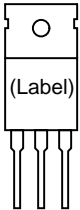Competency: SCR terminal identification		Version:
Description		
Identify the terminals (emitter, base, and collector) of a silicon-controlled rectifier using a multimeter. Then, compare your conclusions with information from a datasheet or cross-reference book.		
Given conditions		
Part number =		
Parameters		
Measured $V_{\text{bias(GK)}}$ <input type="text"/>		
Terminal identification (Draw your own sketch if the one shown is not appropriate)		
Advertised	Your conclusion	
		

Answer 59

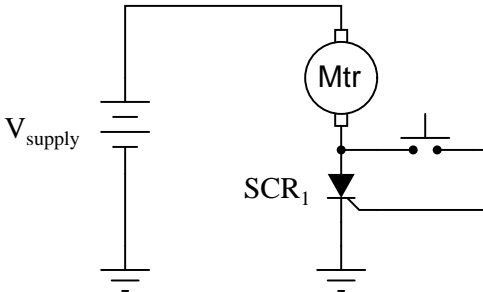
Contrary to what you might think, the datasheet or cross-reference is not the "final authority" for checking your meter-based conclusions! I have seen datasheets and cross-reference manuals wrong more than once!

Notes 59

Identification of SCR terminals is a very important skill for technicians to have. Most modern multimeters have a *diode check* feature which may be used to positively identify PN junction polarities, and this is what I recommend students use for identifying SCR terminals.

This exercise may be made even more interesting if students must differentiate between SCR's with sensitive gates versus SCR's without sensitive gates!

To make this a really good performance assessment, you might want to take several SCR's and scratch the identifying labels off, so students cannot refer to memory for pin identification. Label these thyristors with your own numbers ("1", "2", etc.) so *you* will know which is which, but not the students!

Competency: SCR latch circuit		Version:
Schematic		
		
Given conditions		
$V_{\text{supply}} =$		
Parameters		
	Predicted	Measured
V_{motor} (on)		
I_{supply} (on)		
	Calculated	
P_{SCR1}		

Answer 60

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 60

I have had good success using 12 volts DC for the supply voltage, an MCR8SN silicon-controlled rectifier, and a small brushless DC fan motor (80 mA running current) as the load. The MCR8SN is a "sensitive gate" SCR, which makes it easy to demonstrate static triggering (just *touch* the gate terminal with your finger to start the motor!). Some SCR's may be difficult to keep latched with low-current loads, so be sure to prototype your SCR/load combination before assigning part numbers to your students!

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

Competency: SCR latch circuit		Version:
Description		
Design and build a circuit that uses a switch to turn on a Silicon-Controlled Rectifier so that it "latches" in the ON state, maintaining power to a DC load such as a lamp or small electric motor after the switch has been opened.		
Given conditions		
$V_{\text{supply}} =$		
Schematic		
Parameters		
	Yes	No
Does the circuit <i>latch</i> ?	<input type="checkbox"/>	<input type="checkbox"/>

file 02345

Answer 61

Use circuit simulation software to verify your predicted and measured parameter values.

Notes 61

An extension of this exercise is to incorporate troubleshooting questions. Whether using this exercise as a performance assessment or simply as a concept-building lab, you might want to follow up your students' results by asking them to predict the consequences of certain circuit faults.

(Template)

Competency:		Version:	
Schematic			
Given conditions			
Parameters			
Predicted		Measured	
<div></div>	<div></div>	<div></div>	<div></div>
<div></div>	<div></div>	<div></div>	<div></div>

Answer 62

Here, you would indicate where or how to obtain answers for the requested parameters, but not actually give the figures. My stock answer here is “use circuit simulation software” (Spice, Multisim, etc.).

Notes 62

Any relevant notes for the assessment activity go here.