

Bipolar junction transistors in active mode

This worksheet and all related files are licensed under the Creative Commons Attribution License, version 1.0. To view a copy of this license, visit <http://creativecommons.org/licenses/by/1.0/>, or send a letter to Creative Commons, 559 Nathan Abbott Way, Stanford, California 94305, USA. The terms and conditions of this license allow for free copying, distribution, and/or modification of all licensed works by the general public.


Resources and methods for learning about these subjects (list a few here, in preparation for your research):

Questions

Question 1


The following schematic diagram is of a simple *curve tracer circuit*, used to plot the current/voltage characteristics of different electronic components on an oscilloscope screen:

Simple curve tracer circuit

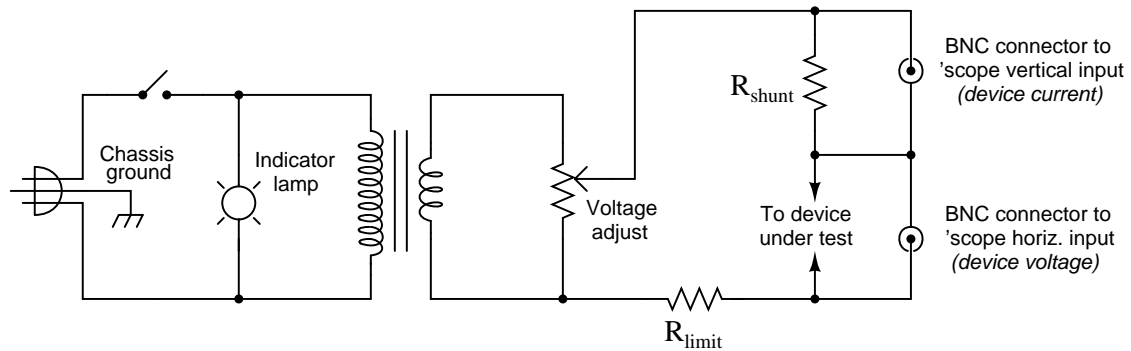


The way it works is by applying an AC voltage across the terminals of the device under test, outputting two different voltage signals to the oscilloscope. One signal, driving the horizontal axis of the oscilloscope, represents the voltage across the two terminals of the device. The other signal, driving the vertical axis of the oscilloscope, is the voltage dropped across the shunt resistor, representing current through the device. With the oscilloscope set for "X-Y" mode, the electron beam traces the device's characteristic curve.

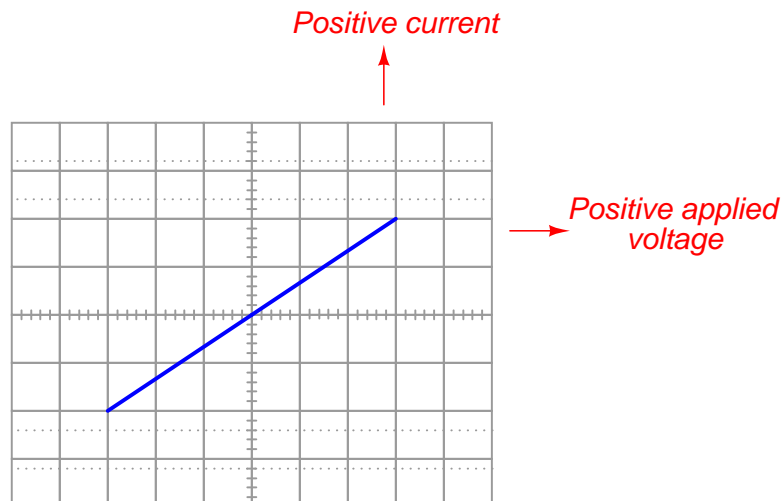For example, a simple resistor would generate this oscilloscope display:




A resistor of greater value (more ohms of resistance) would generate a characteristic plot with a shallower slope, representing less current for the same amount of applied voltage:

Higher-valued resistor

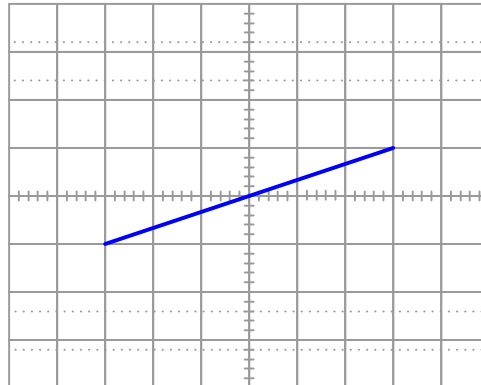

Curve tracer circuits find their real value in testing semiconductor components, whose voltage/current behaviors are nonlinear. Take for instance this characteristic curve for an ordinary rectifying diode:


Rectifying diode curve

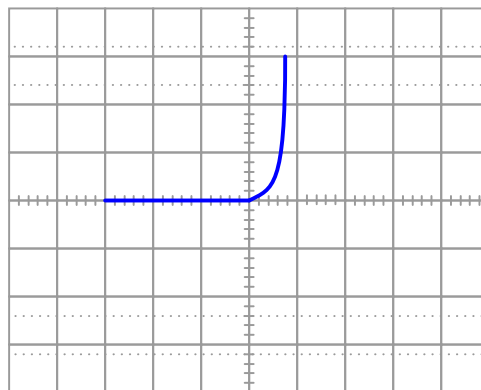


The trace is flat everywhere left of center where the applied voltage is negative, indicating no diode current when it is reverse-biased. To the right of center, though, the trace bends sharply upward, indicating exponential diode current with increasing applied voltage (forward-biased) just as the "diode equation" predicts.

On the following grids, plot the characteristic curve for a diode that is failed shorted, and also for one that is failed open:

Diode failed shorted

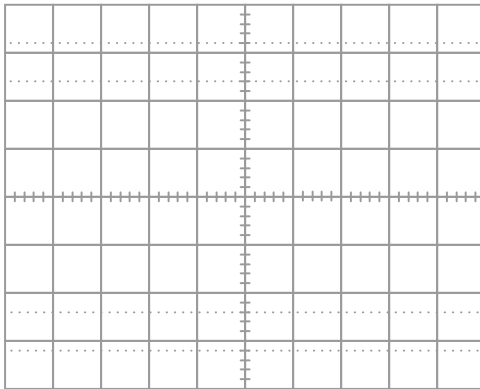


Diode failed open

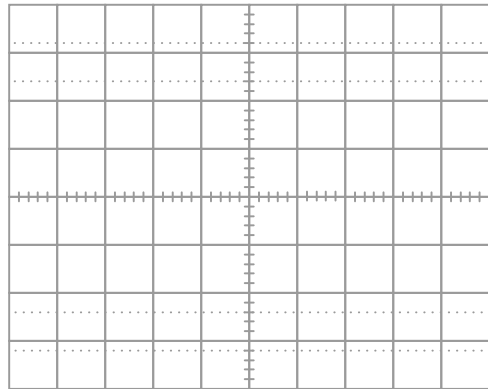


file 02431

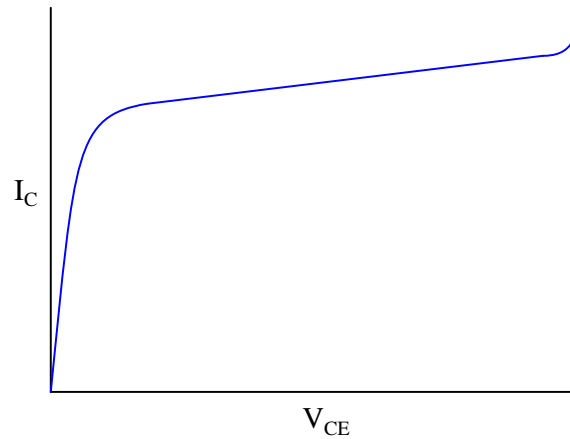Question 2

A very important measure of a transistor's behavior is its *characteristic curves*, a set of graphs showing collector current over a wide range of collector-emitter voltage drops, for a given amount of base current. The following plot is a typical curve for a bipolar transistor with a fixed value of base current:



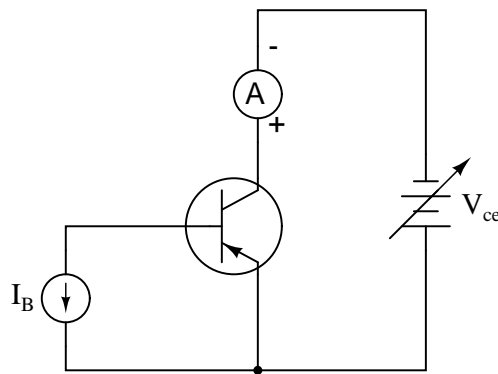A "test circuit" for collecting data to make this graph looks like this:



Identify three different regions on this graph: *saturation*, *active*, and *breakdown*, and explain what each of these terms mean. Also, identify which part of this curve the transistor acts most like a current-regulating device.

file 00940


Question 3

Explain what it means for a transistor to operate in its "active" mode (as opposed to cutoff, saturation, or breakdown).

file 02484

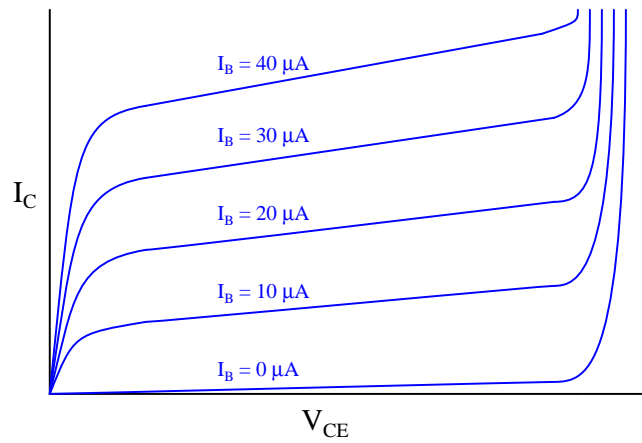Question 4

If a transistor is subjected to several different base currents, and the collector-emitter voltage (V_{CE}) "swept" through the full range for each of these base current values, data for an entire "family" of characteristic curves may be obtained and graphed:




What do these characteristic curves indicate about the base current's control over collector current?
How are the two currents related?

file 00941

Question 5


Determine the approximate amount of collector current for this transistor circuit, given the following characteristic curve set for the transistor:

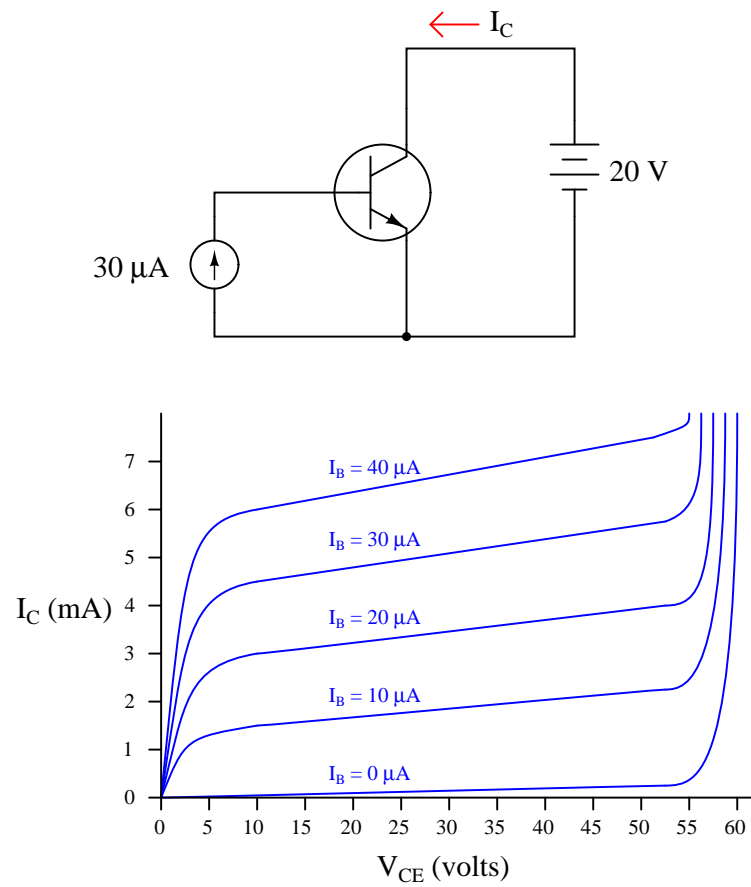

file 02435

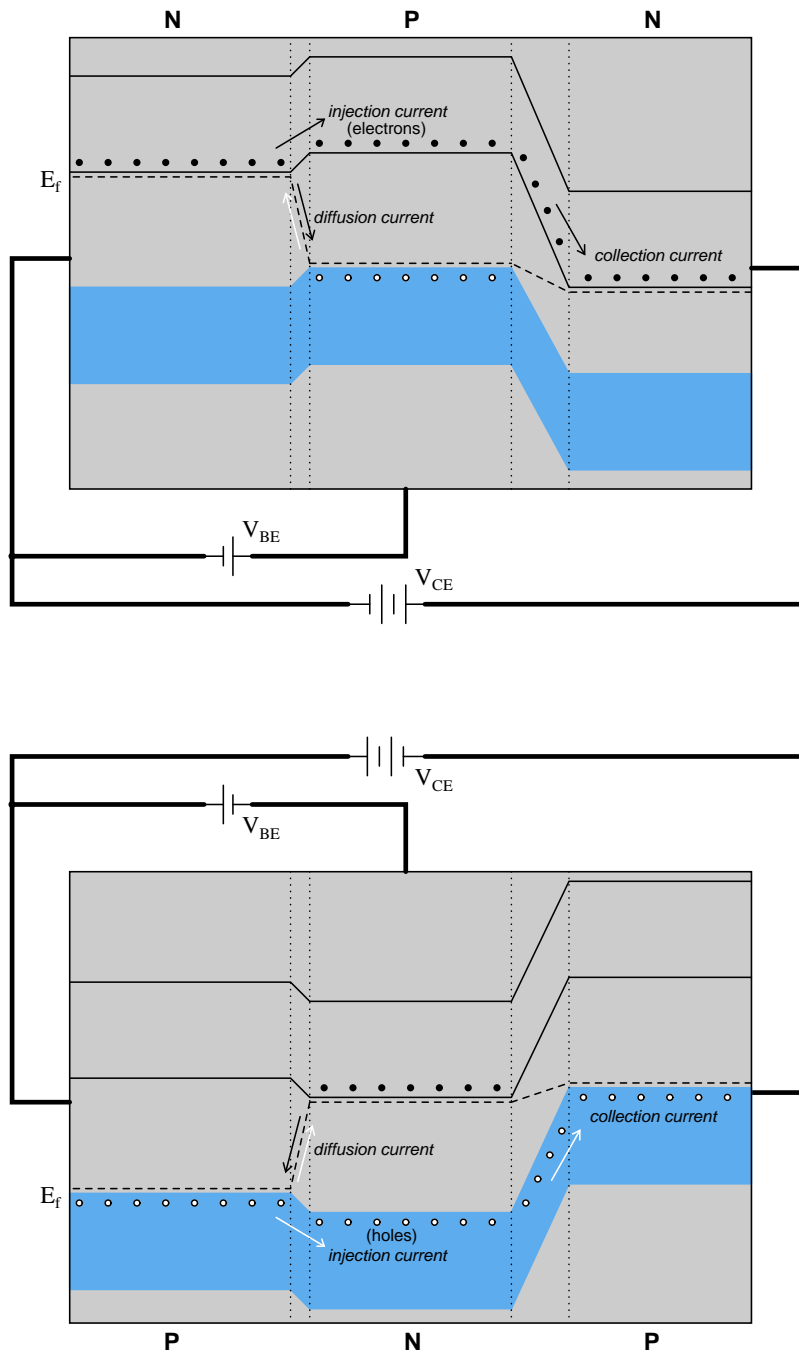Question 6

Conduction of an electric current through the collector terminal of a bipolar junction transistor requires that minority carriers be "injected" into the base region by a base-emitter current. Only after being injected into the base region may these charge carriers be swept toward the collector by the applied voltage between emitter and collector to constitute a collector current:



An analogy to help illustrate this is a person tossing flower petals into the air above their head, while a breeze carries the petals horizontally away from them. None of the flower petals may be "swept" away by the breeze until the person releases them into the air, and the velocity of the breeze has no bearing on

how many flower petals are swept away from the person, since they must be released from the person's grip before they can go anywhere.

By referencing either the energy diagram or the flower petal analogy, explain why the collector current for a BJT is strongly influenced by the base current and only weakly influenced by the collector-to-emitter voltage.

[file 02482](#)

Question 7

Explain why a bipolar junction transistor tends to regulate collector current over a wide range of collector-to-emitter voltage drops when its base current is constant. What happens internally that makes the BJT's collector current relatively independent of collector-to-emitter voltage and strongly dependent on base current?

[file 02163](#)

Question 8

Many technical references will tell you that bipolar junction transistors (BJTs) are *current-controlled* devices: collector current is controlled by base current. This concept is reinforced by the notion of "beta" (β), the ratio between collector current and base current:

$$\beta = \frac{I_C}{I_B}$$


Students learning about bipolar transistors are often confused when they encounter datasheet specifications for transistor β ratios. Far from being a constant parameter, the "beta" ratio of a transistor may vary significantly over its operating range, in some cases exceeding an order of magnitude (ten times)!

Explain how this fact agrees or disagrees with the notion of BJTs being "current-controlled" devices. If collector current really is a direct function of base current, then why would the constant of proportionality between the two (β) change so much?


[file 02164](#)

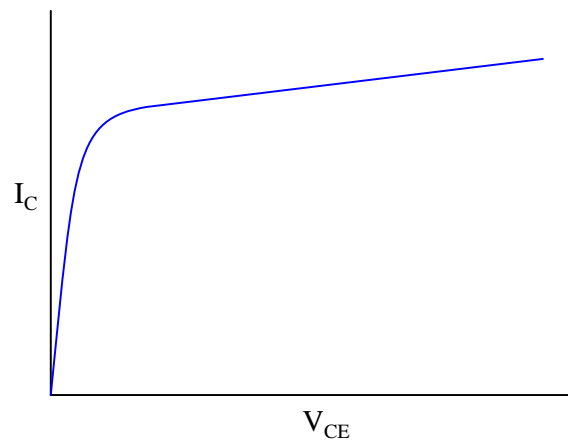Question 9

We know that graphs are nothing more than collections of individual points representing correlated data in a system. Here is a plot of a transistor's characteristic curve (for a single value of base current):



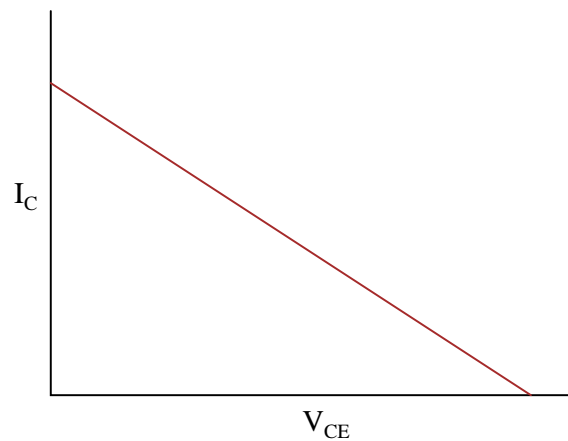And here is a plot of the "load line" for a transistor amplifier circuit:




For each of these graphs, pick a single point along the curve (or line) and describe what that single point represents, in real-life terms. What does any single point of data along either of these graphs *mean* in a transistor circuit?

If a transistor's characteristic curve is superimposed with a load line on the same graph, what is the significance of those two plots' intersection?

file 00945

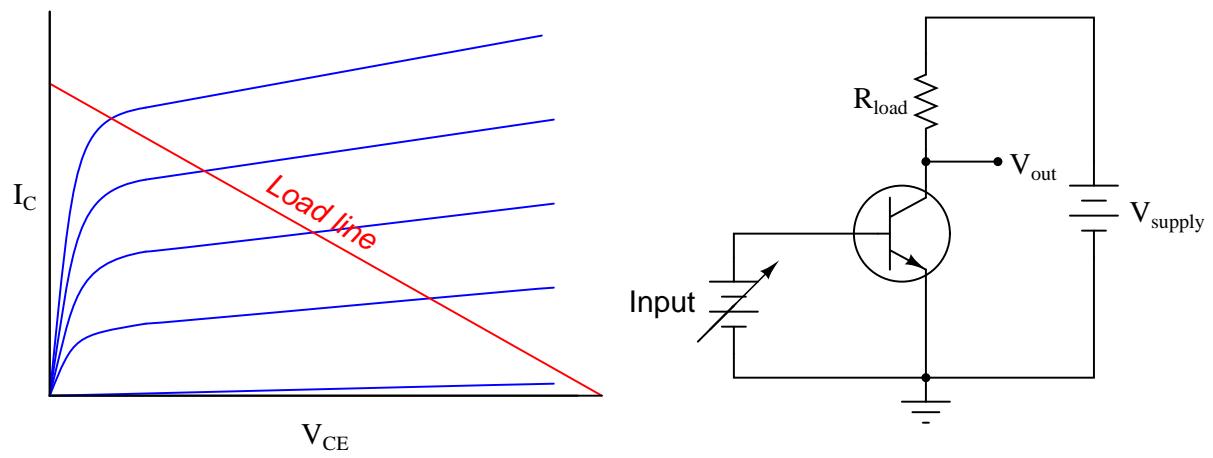Question 10

Describe what a *load line* is, as it appears superimposed on this graph of characteristic transistor curves:




What exactly does the load line represent in the circuit?


file 01681

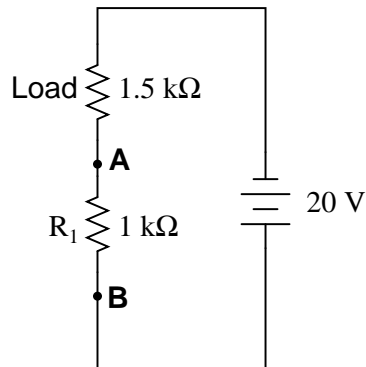Question 11


Load lines are useful tools for analyzing transistor amplifier circuits, but they may be hard to understand at first. To help you understand what "load lines" are useful for and how they are determined, I will apply one to this simple two-resistor circuit:



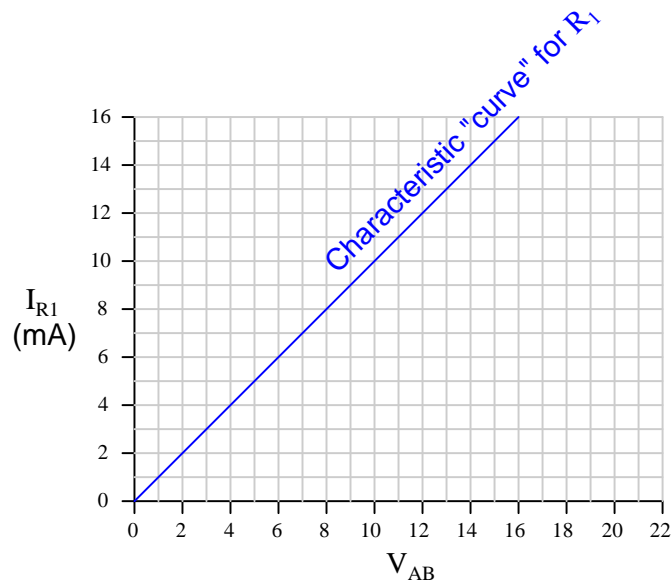We will have to plot a load line for this simple two-resistor circuit along with the "characteristic curve" for resistor R_1 in order to see the benefit of a load line. Load lines really only have meaning when superimposed with other plots. First, the characteristic curve for R_1 , defined as the voltage/current relationship between terminals **A** and **B**:



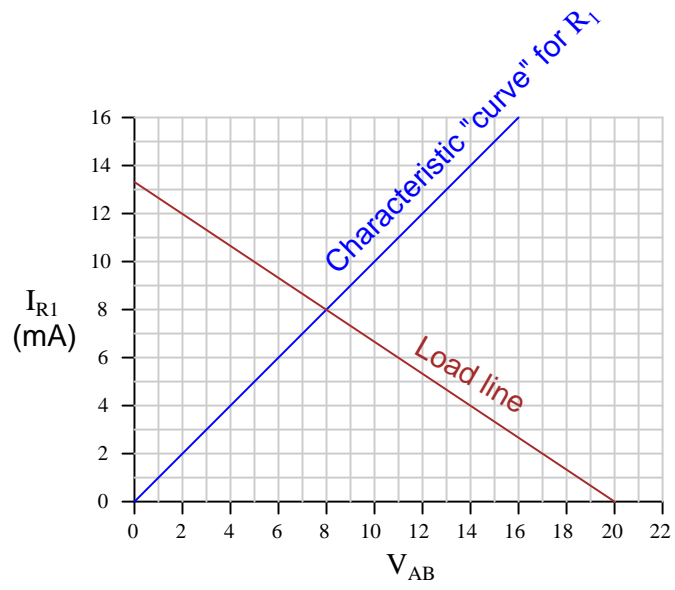Next, I will plot the load line as defined by the 1.5 kΩ load resistor. This "load line" expresses the voltage available between the same two terminals (V_{AB}) as a function of the load current, to account for voltage dropped across the load:




At what value of current (I_{R1}) do the two lines intersect? Explain what is significant about this value of current.


file 00953

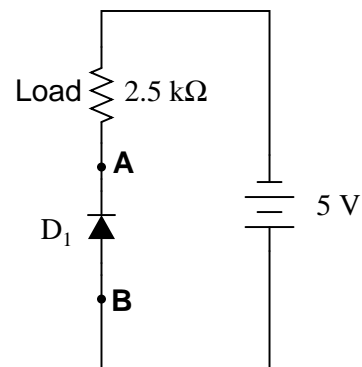Question 12

Load lines are useful tools for analyzing transistor amplifier circuits, but they may be applied to other types of circuits as well. Take for instance this diode-resistor circuit:



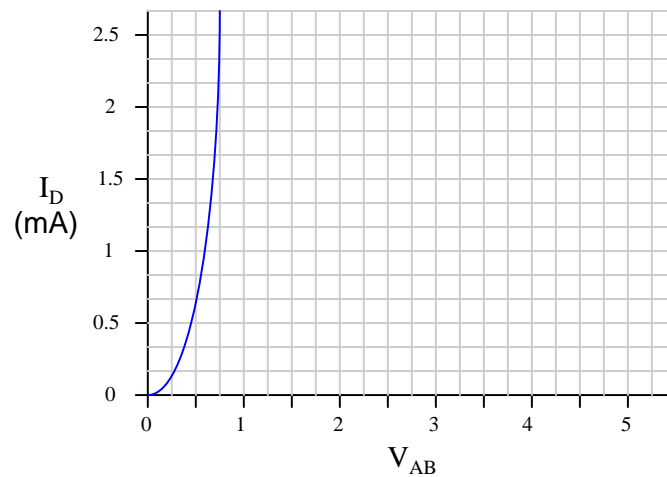
The diode's characteristic curve is already plotted on the following graph. Your task is to plot the load line for the circuit on the same graph, and note where the two lines intersect:




What is the practical significance of these two plots' intersection?
[file 00954](#)

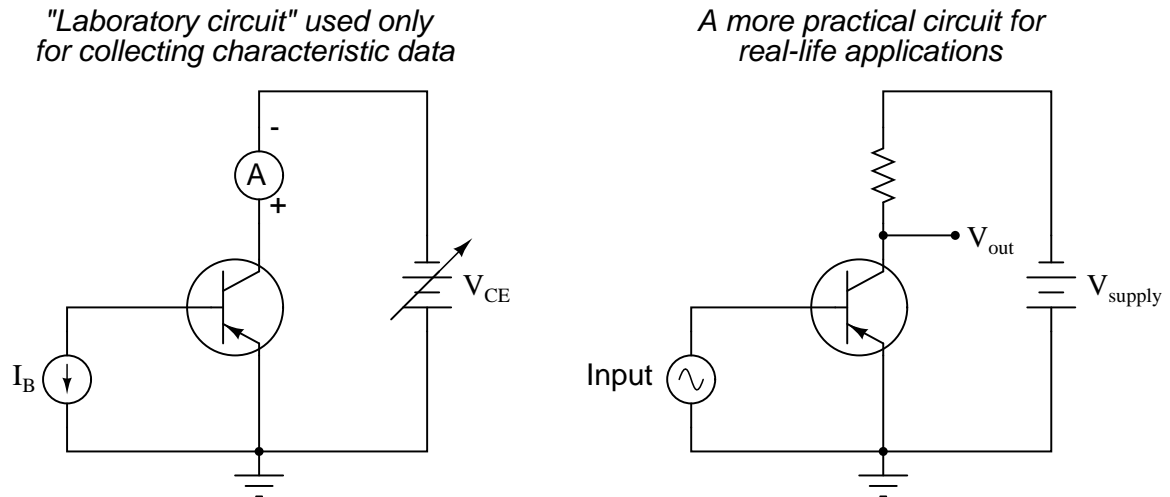Question 13

Though the characteristic curves for a transistor are usually generated in a circuit where base current is constant and the collector-emitter voltage (V_{CE}) is varied, this is usually not how transistor amplifier circuits are constructed. Typically, the base current varies with the input signal, and the collector power supply is a fixed-voltage source:





The presence of a load resistor in the circuit adds another dynamic to the circuit's behavior. Explain what happens to the transistor's collector-emitter voltage (V_{CE}) as the collector current increases (dropping more battery voltage across the load resistor), and qualitatively plot this *load line* on the same type of graph used for plotting transistor curves:

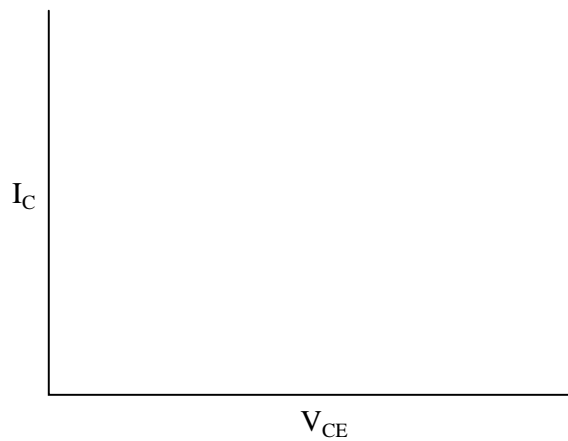

file 00943

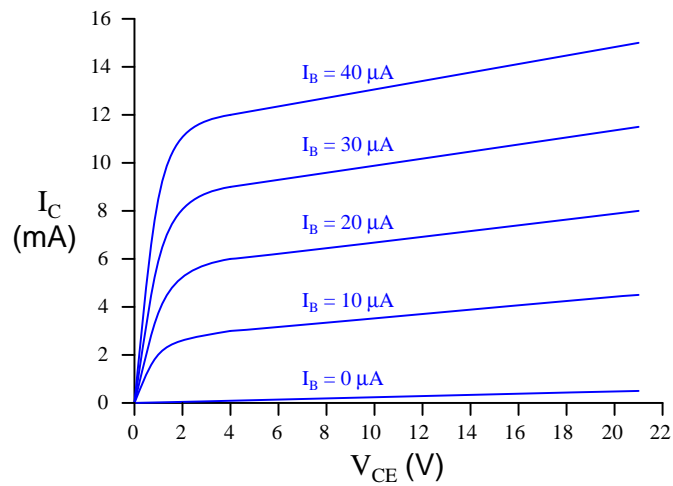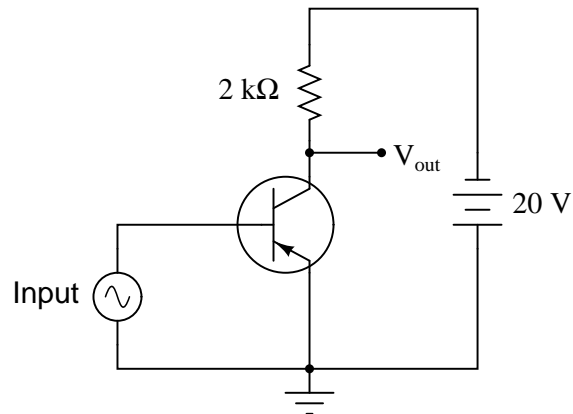Question 14

Calculate and superimpose the *load line* for this circuit on top of the transistor's characteristic curves:





Then, determine the amount of collector current in the circuit at the following base current values:

- $I_B = 10 \mu A$
- $I_B = 20 \mu A$
- $I_B = 30 \mu A$
- $I_B = 40 \mu A$

file 00944

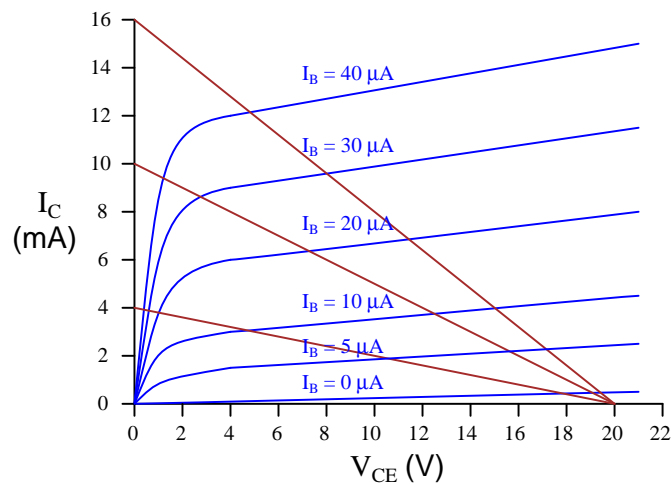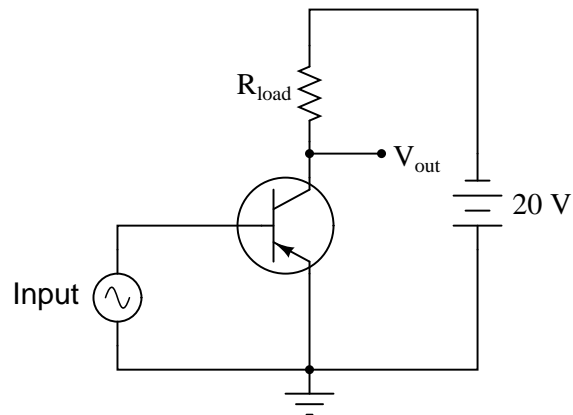Question 15

In this graph you will see three different load lines plotted, representing three different values of load resistance in the amplifier circuit:



Which one of the three load lines represents the largest value of load resistance (R_{load})? Which of the three load lines will result in the greatest amount of change in voltage drop across the transistor (ΔV_{CE}) for any given amount of base current change (ΔI_B)? What do these relationships indicate about the load resistor's effect on the amplifier circuit's *voltage gain*?

[file 00955](#)

Question 16


An important parameter of transistor amplifier circuits is the *Q point*, or *quiescent operating point*. The "Q point" of a transistor amplifier circuit will be a single point somewhere along its load line.

Describe what the "Q point" actually means for a transistor amplifier circuit, and how its value may be altered.


[file 00952](#)

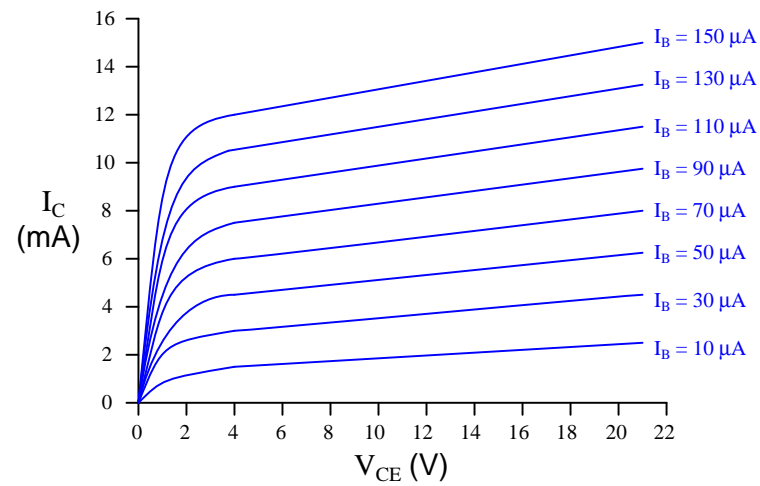Question 17

The following graph is a family of characteristic curves for a particular transistor:




Draw the load line and identify the Q-point on that load line for a common-collector amplifier circuit using this transistor:

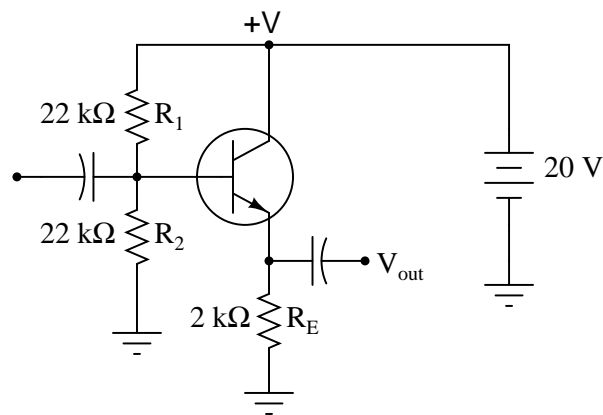


file 02244

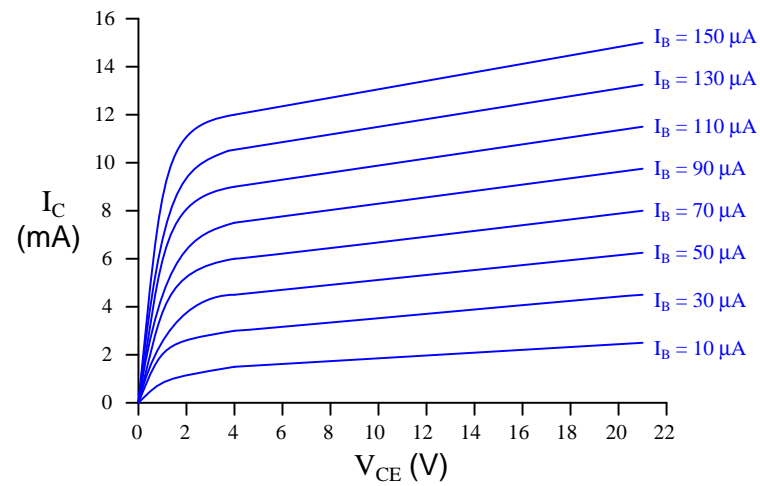Question 18

The following graph is a family of characteristic curves for a particular transistor:




Draw the load line and identify the Q-point on that load line for a common-emitter amplifier circuit using this transistor:

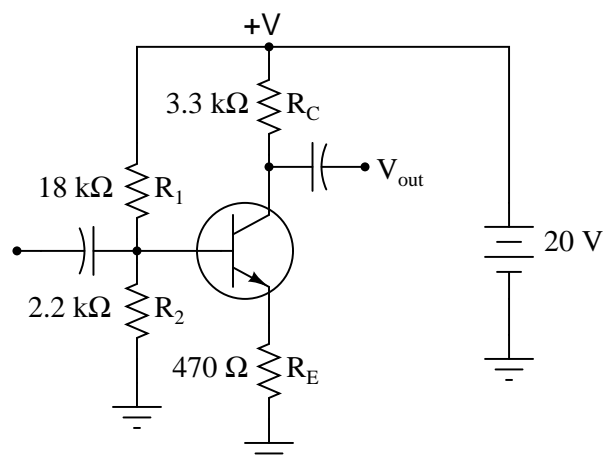


file 02245

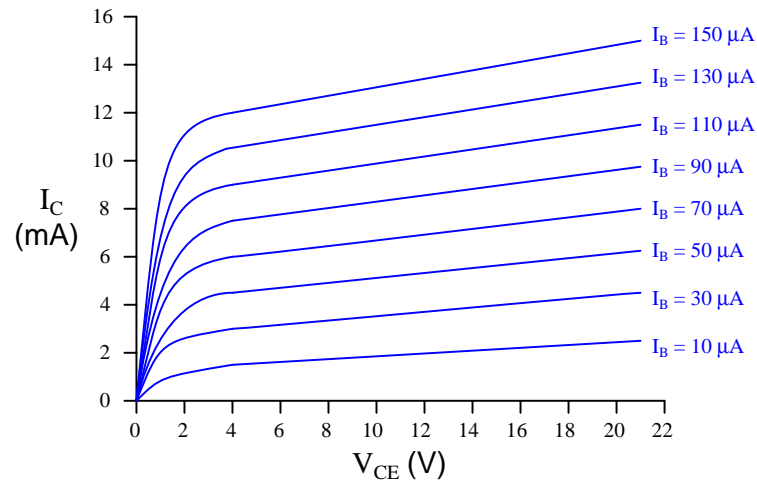Question 19

The following graph is a family of characteristic curves for a particular transistor:



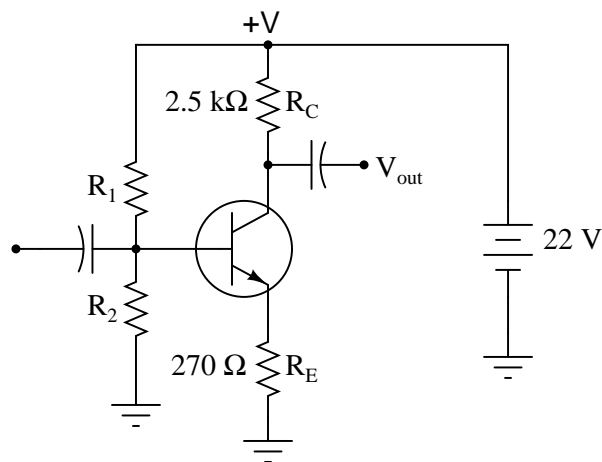Superimpose on that graph a load line for the following common-emitter amplifier circuit using the same transistor:



Also determine some bias resistor values (R_1 and R_2) that will cause the Q-point to rest approximately mid-way on the load line.

$R_1 =$ _____ $R_2 =$ _____
[file 02246](#)

Question 20

Find one or two real bipolar junction transistors and bring them with you to class for discussion. Identify as much information as you can about your transistors prior to discussion:

- Terminal identification (which terminal is base, emitter, collector)
- Continuous power rating
- Typical β

[file 01164](#)


Question 21

A common term used in semiconductor circuit engineering is *small signal analysis*. What, exactly, is "small signal" analysis, and how does it contrast with *large signal analysis*?

file 01680

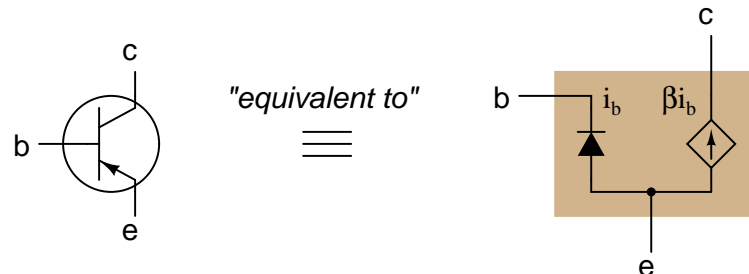
Question 22

Models of complex electronic components are useful for circuit analysis, because they allow us to express the approximate behavior of the device in terms of ideal components with relatively simple mathematical behaviors. Transistors are a good example of components frequently modeled for the sake of amplifier circuit analysis:




It must be understood that models are never *perfect* replicas of the real thing. At some point, all models fail to precisely emulate the thing being modeled. The only real concern is how accurate we want our approximation to be: which characteristics of the component most concern us, and which do not.

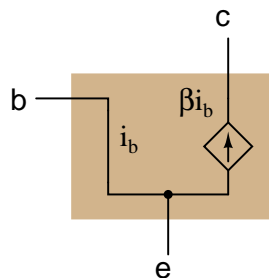For example, when analyzing the response of transistor amplifier circuits to small AC signals, it is often assumed that the transistor will be "biased" by a DC signal such that the base-emitter diode is always conducting. If this is the case, and all we are concerned with is how the transistor responds to *AC* signals, we may safely eliminate the diode junction from our transistor model:




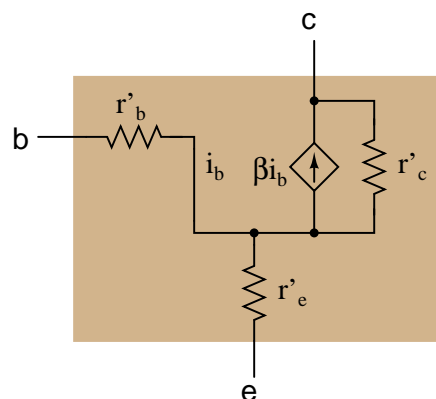However, even with the 0.7 volt (nominal) DC voltage drop absent from the model, there is still some impedance that an AC signal will encounter as it flows through the transistor. In fact, several distinct impedances exist within the transistor itself, customarily symbolized by resistors and lower-case r' designators:



From the perspective of an AC current passing through the base-emitter junction of the transistor, explain why the following transistor models are equivalent:

Equivalent transistor models

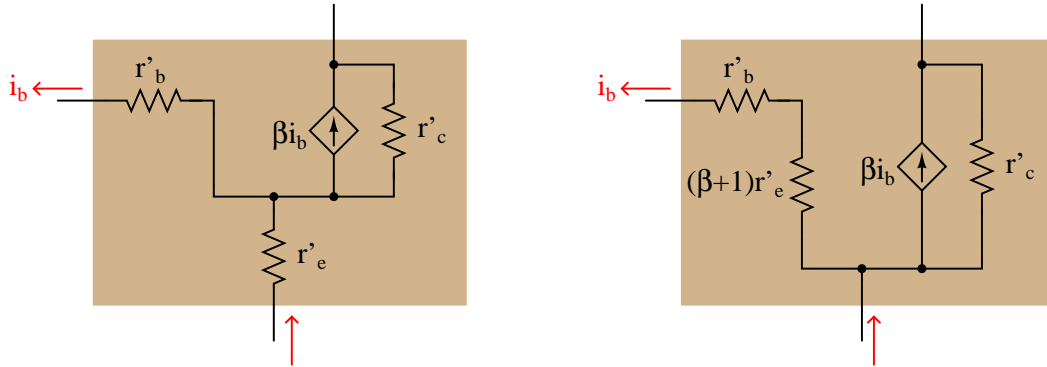

file 02239

Don't just sit there! Build something!!

Learning to mathematically analyze circuits requires much study and practice. Typically, students practice by working through lots of sample problems and checking their answers against those provided by the textbook or the instructor. While this is good, there is a much better way.

You will learn much more by actually *building and analyzing real circuits*, letting your test equipment provide the "answers" instead of a book or another person. For successful circuit-building exercises, follow these steps:

1. Carefully measure and record all component values prior to circuit construction, choosing resistor values high enough to make damage to any active components unlikely.
2. Draw the schematic diagram for the circuit to be analyzed.
3. Carefully build this circuit on a breadboard or other convenient medium.
4. Check the accuracy of the circuit's construction, following each wire to each connection point, and verifying these elements one-by-one on the diagram.
5. Mathematically analyze the circuit, solving for all voltage and current values.
6. Carefully measure all voltages and currents, to verify the accuracy of your analysis.
7. If there are any substantial errors (greater than a few percent), carefully check your circuit's construction against the diagram, then carefully re-calculate the values and re-measure.

When students are first learning about semiconductor devices, and are most likely to damage them by making improper connections in their circuits, I recommend they experiment with large, high-wattage components (1N4001 rectifying diodes, TO-220 or TO-3 case power transistors, etc.), and using dry-cell battery power sources rather than a benchtop power supply. This decreases the likelihood of component damage.


As usual, avoid very high and very low resistor values, to avoid measurement errors caused by meter "loading" (on the high end) and to avoid transistor burnout (on the low end). I recommend resistors between 1 k Ω and 100 k Ω .

One way you can save time and reduce the possibility of error is to begin with a very simple circuit and incrementally add components to increase its complexity after each analysis, rather than building a whole new circuit for each practice problem. Another time-saving technique is to re-use the same components in a variety of different circuit configurations. This way, you won't have to measure any component's value more than once.


file 00505

Answers

Answer 1

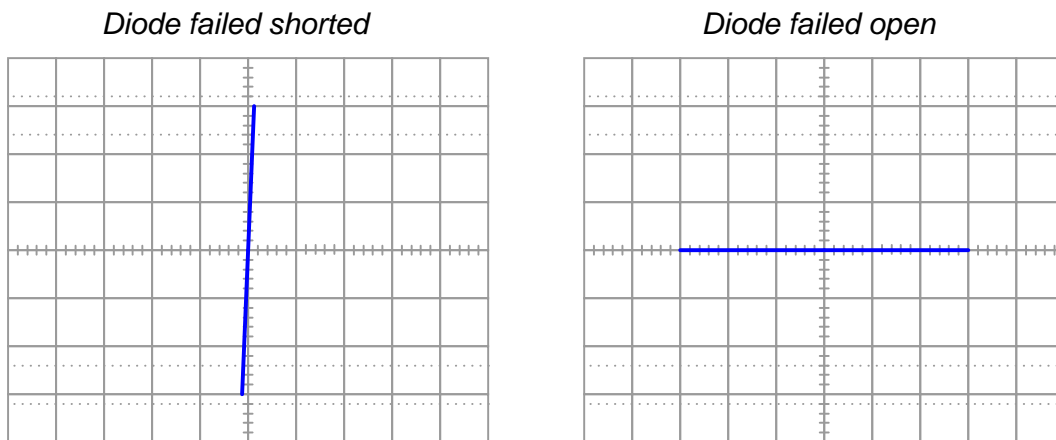

Answer 2

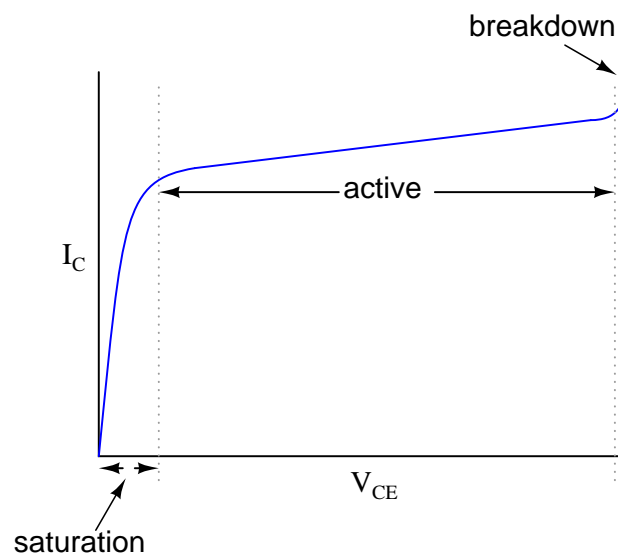

The transistor's best current-regulation behavior occurs in its "active" region.

Follow-up question: what might the characteristic curves look like for a transistor that is failed *shorted* between its collector and emitter terminals? What about the curves for a transistor that is failed *open*?

Answer 3

In the active mode, a transistor "throttles" current somewhere between being fully off and fully on.

Answer 4

The collector current is (for the most part) directly proportional to base current while in the "active" region.

Answer 5

$$I_C \approx 4.75 \text{ mA}$$

Follow-up question: how much will the collector current rise if the voltage source increases to 35 volts?

Answer 6

The action of tossing flower petals into the air is analogous to base current injecting charge carriers into the base region of a transistor. The drifting of those tossed petals by the wind is analogous to the sweeping of charge carriers across the base and into the collector by V_{CE} . Like the number of flower petals drifting, the amount of collector current does not depend much on the strength of V_{CE} (the strength of the wind), but rather on the rate of charge carriers injected (the number of petals tossed upward per second).

Answer 7

Because the BJT is a minority carrier device, the vast majority of collector current is the result of charge carriers injected from the emitter into the base region. Since this rate of charge carrier injection is a function of base-emitter junction excitation, base current (or more properly, base-to-emitter voltage) primarily determines collector current with collector-to-emitter voltage playing a relatively minor role.

Answer 8

Sit down before you read this, and brace yourself for the hard truth: bipolar junction transistors are technically *not* current-controlled devices. You were sitting down, right? Good.

Follow-up question: if BJTs are not controlled by base current, then what *are* they controlled by? Express this in the form of an equation if possible. Hint: research the "diode equation" for clues.

Answer 9


For a transistor's characteristic curve, one point of data represents the amount of current that will go through the collector terminal for a given amount of base current, and a given amount of collector-emitter voltage drop.

For a load line, one point of data represents the amount of collector-emitter voltage available to the transistor for a given amount of collector current.

The intersection of a characteristic curve and a load line represents the one collector current (and corresponding V_{CE} voltage drop) that will "satisfy" all components' conditions.

Answer 10

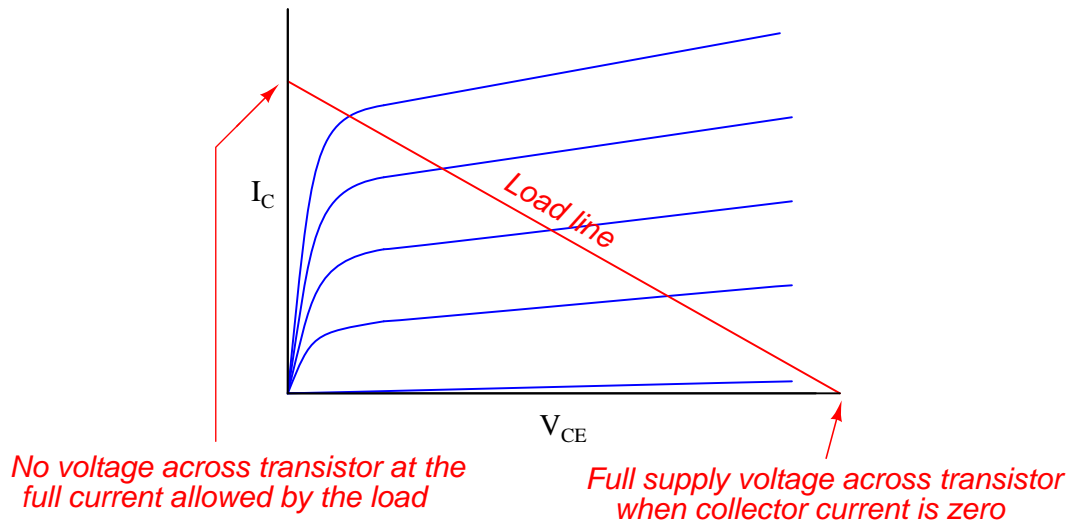A *load line* is a plot showing the amount of collector-emitter voltage available to the transistor (V_{CE}) for any given collector current:



Follow-up question: why are load lines always straight, and not bent as the transistor characteristic curves are? What is it that ensures load line plots will always be linear functions?


Answer 11

$I_R = 8 \text{ mA}$ is the same value of current you would calculate if you had analyzed this circuit as a simple series resistor network.

Follow-up question: you might be wondering, "what is the point of plotting a 'characteristic curve' and a 'load line' in such a simple circuit, if all we had to do to solve for current was add the two resistances and divide that total resistance value into the total voltage?" Well, to be honest, there is no point in analyzing such a simple circuit in this manner, except to illustrate *how* load lines work. My follow-up question to you is this: where would plotting a load line actually be helpful in analyzing circuit behavior? Can you think of any modifications to this two-resistor circuit that would require load line analysis in order to solve for current?

Answer 12

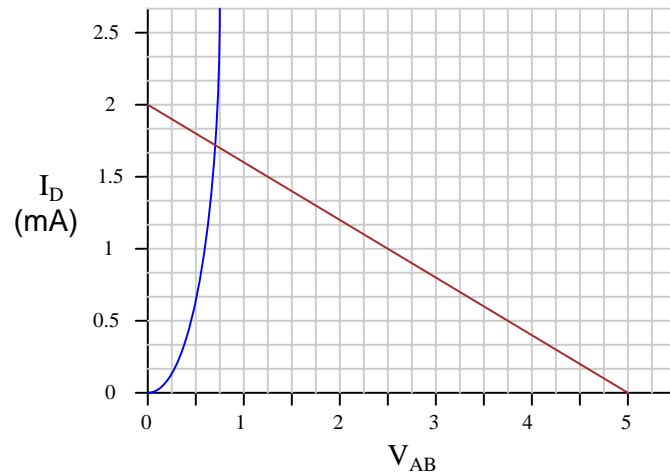The two lines intersect at a current of approximately 1.72 mA:




Follow-up question: explain why the use of a load line greatly simplifies the determination of circuit current in such a diode-resistor circuit.



Challenge question: suppose the resistor value were increased from 2.5 k Ω to 10 k Ω . What difference would this make in the load line plot, and in the intersection point between the two plots?

Answer 13

Because there are no numbers along the axes of this graph, the best you can do is plot the general slope of the line, from upper-left to lower-right:

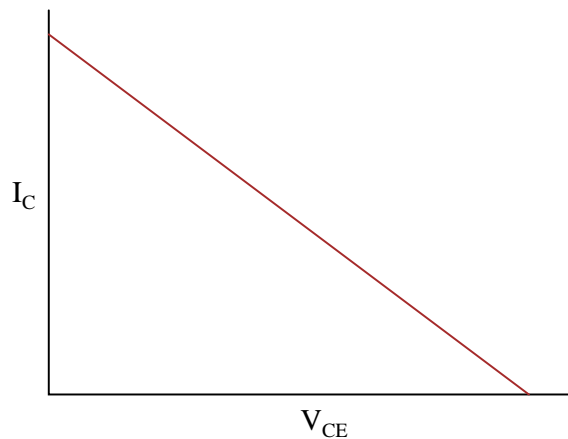

Answer 14

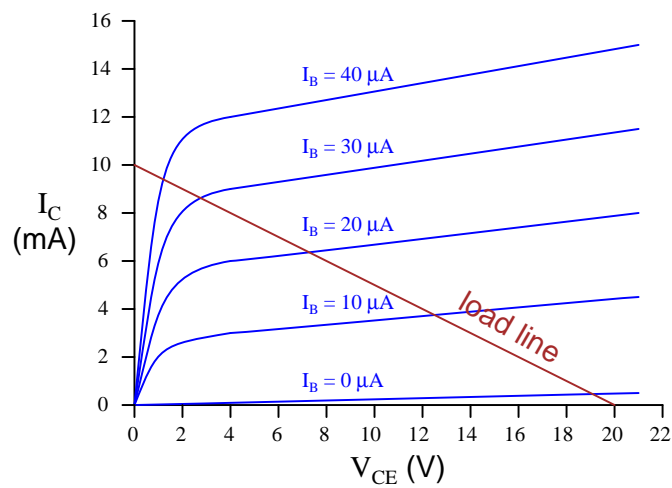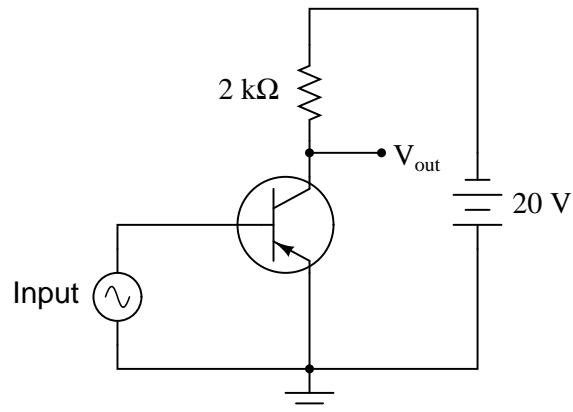

- $I_B = 10 \mu A$; $I_C = 3.75 \text{ mA}$
- $I_B = 20 \mu A$; $I_C = 6.25 \text{ mA}$
- $I_B = 30 \mu A$; $I_C = 8.5 \text{ mA}$
- $I_B = 40 \mu A$; $I_C = 9.5 \text{ mA}$


Answer 15

The load line closest to horizontal represents the largest value of load resistance, and it also represents the condition in which V_{CE} will vary the most for any given amount of base current (input signal) change.

Answer 16


The "Q point" for a transistor amplifier circuit is the point along its operating region in a "quiescent" condition: when there is no input signal being amplified.

Answer 17

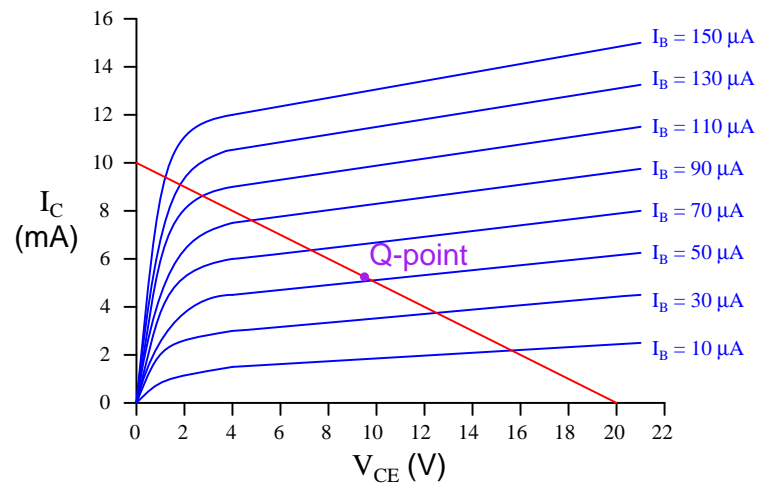


Follow-up question: the position of this circuit's Q-point is approximately mid-way along the load line. Would you say this is indicative of an amplifier biased for Class A operation, or for some other class of operation? Explain your answer.

Answer 18

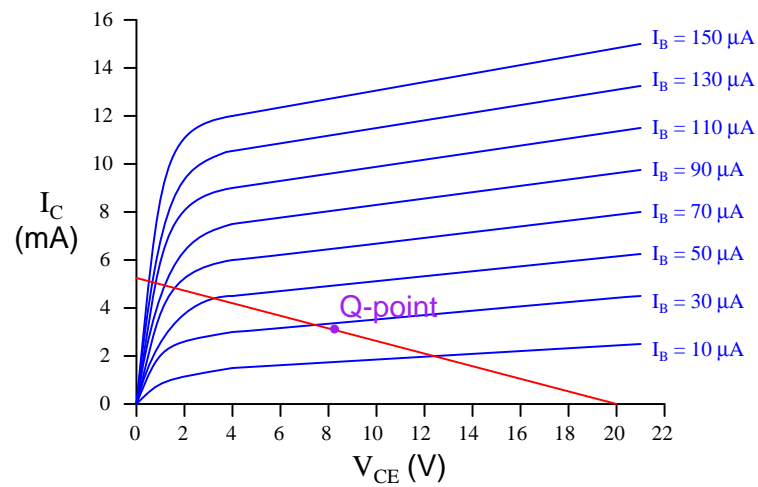

Follow-up question: determine what would happen to the Q-point if resistor R_2 (the $2.2 \text{ k}\Omega$ biasing resistor) were to fail open.

Answer 19

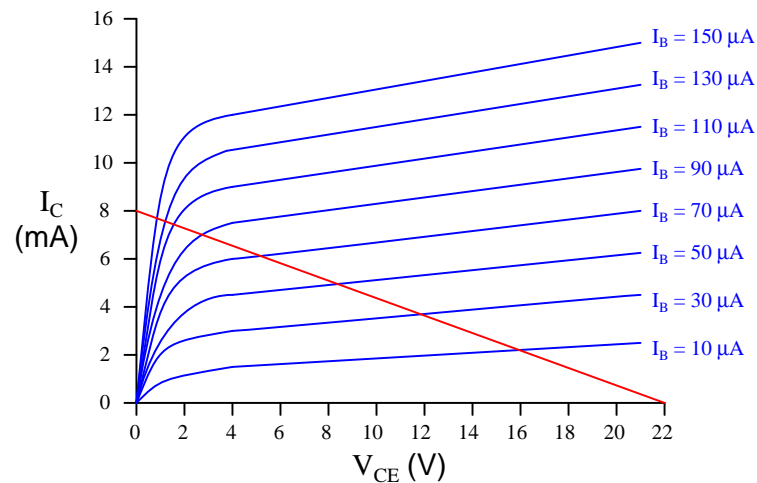

There are several pairs of resistor values that will work adequately to position the Q-point at the center of the load line. I leave this as an exercise for you to work through and discuss with your classmates!

Follow-up question: determine what would happen to the Q-point if resistor R_2 (the 2.2 k Ω biasing resistor) were to fail open.

Answer 20

If possible, find a manufacturer's datasheet for your components (or at least a datasheet for a similar component) to discuss with your classmates. Be prepared to *prove* the terminal identifications of your transistors in class, by using a multimeter!

Answer 21

Small signal analysis is where the signals are presumed to be small enough in magnitude that the active device(s) should respond in a nearly linear manner. *Large signal analysis* is where the signals are presumed to be large enough that component nonlinearities become significant.

Follow-up question: why would engineers bother with two modes of analysis instead of just one (large signal), where the components' true (nonlinear) behavior is taken into account? Explain this in terms of network theorems and other mathematical "tools" available to engineers for circuit analysis.

Answer 22

These two models are equivalent because a given current (i_b) will cause the exact same amount of voltage drop between base and emitter ($v = i_r$):

$$v = i_b r'_b + (i_b + \beta i_b) r'_e \quad \text{Left-hand model}$$

$$v = i_b [r'_b + (\beta + 1) r'_e] \quad \text{Right-hand model}$$

The mathematical equivalence of these two expressions may be shown by factoring i_b from all the terms in the left-hand model equation.

Answer 23

Let the electrons themselves give you the answers to your own "practice problems"!

Notes

Notes 1

Characteristic curves are not the easiest concept for some students to grasp, but they are incredibly informative. Not only can they illustrate the electrical behavior of a nonlinear device, but they can also be used to diagnose otherwise hard-to-measure faults. Letting students figure out what shorted and open curves look like is a good way to open their minds to this diagnostic tool, and to the nature of characteristic curves in general.

Although it is far from obvious, one of the oscilloscope channels will have to be "inverted" in order for the characteristic curve to appear in the correct quadrant(s) of the display. Most dual-trace oscilloscopes have a "channel invert" function that works well for this purpose. If engaging the channel invert function on the oscilloscope flips the wrong axis, you may reverse the connections of the test device to the curve tracer circuit, flipping both axes simultaneously. Between reversing device connections and reversing one channel of the oscilloscope, you can get the curve to plot any way you want it to!

Notes 2

Ask your students what a perfect current-regulating curve would look like. How does this perfect curve compare with the characteristic curve shown in this question for a typical transistor?

A word of caution is in order: I do not recommend that a test circuit such as the one shown in the question be built for collecting curve data. If the transistor dissipates power for any substantial amount of time, it will heat up and its curves will change dramatically. Real transistor curves are generated by a piece of test equipment called a "curve tracer," which sweeps the collector-emitter voltage and steps the base current very rapidly (fast enough to "paint" all curves on an oscilloscope screen before the phosphor stops glowing).

Notes 3

Help your students contrast active transistor operation with what they know of transistors as switching elements (either saturated or cut off). Ask them to explain what is unique about transistor behavior in the active region that is not exhibited in any other region (i.e. the transistor's behavior with regard to collector current and collector-emitter voltage).

Notes 4

Ask your students what the characteristic curves would look like for a *perfect* transistor: one that was a perfect regulator of collector current over the full range of collector-emitter voltage.

Notes 5

This question is nothing more than an exercise in interpreting characteristic curves.

Notes 6

This is one of my better analogies for explaining BJT operation, especially for illustrating the why I_C is almost independent of V_{CE} . It also helps to explain reverse recovery time for transistors: imagine how long it takes the air to clear of tossed flower petals after you stop tossing them, analogous to latent charge carriers having to be swept out of the base region by V_{CE} after base current stops.

Notes 7

The current-regulating nature of a BJT is made more understandable by analyzing an energy band diagram of the transistor in active mode.

Notes 8

For discussion purposes, you might want to show your students this equation, accurate over a wide range of operating conditions for base-emitter voltages in excess of 100 mV:

$$I_C = I_{ES} \left(e^{V_{BE}/V_T} - 1 \right)$$

This equation is nonlinear: increases in V_{BE} do not produce proportional increases in I_C . It is therefore much easier to think of BJT operation in terms of base and collector *currents*, the relationship between those two variables being more linear. Except when it isn't, of course. Such is the tradeoff between simplicity and accuracy. In an effort to make things simpler, we often end up making them *wrong*.

It should be noted here that although bipolar junction transistors aren't really current-controlled devices, they still may be considered to be (approximately) current-*controlling* devices. This is an important distinction that is easily lost in questions such as this when basic assumptions are challenged.

Notes 9

Discuss this question thoroughly with your students. So many students of electronics learn to plot load lines for amplifier circuits without ever really understanding *why* they must do so. Load line plots are very useful tools in amplifier circuit analysis, but the meaning of each curve/line must be well understood before it becomes useful as an instrument of understanding.

Ask your students which of the two types of graphs (characteristic curves, or load lines) represents a component's natural, or "free", behavior, and which one represents the bounded conditions within a particular circuit.

Notes 10

It is very important for students to grasp the ontological nature of load lines (i.e. *what they are*) if they are to use them frequently in transistor circuit analysis. This, sadly, is something often not grasped by students when they begin to study transistor circuits, and I place the blame squarely on textbooks (and instructors) who don't spend enough time introducing the concept.

My favorite way of teaching students about load lines is to have them plot load lines for non-transistor circuits, such as voltage dividers (with one of two resistors labeled as the "load," and the other resistor made variable) and diode-resistor circuits.

Notes 11

While this approach to circuit analysis may seem silly – using load lines to calculate the current in a two-resistor circuit – it demonstrates the principle of load lines in a context that should be obvious to students at this point in their study. Discuss with your students how the two lines are obtained (one for resistor R_1 and the other plotting the voltage available to R_1 based on the total source voltage and the load resistor's value).

Also, discuss the significance of the two line intersecting. Mathematically, what does the intersection of two graphs mean? What do the coordinate values of the intersection point represent in a system of simultaneous functions? How does this principle relate to an electronic circuit?

Notes 12

While this approach to circuit analysis may seem silly – using load lines to calculate the current in a diode-resistor circuit – it demonstrates the principle of load lines in a context that should be obvious to students at this point in their study. Discuss with your students how the load line is obtained for this circuit, and why it is straight while the diode's characteristic curve is not.

Also, discuss the significance of the two line intersecting. Mathematically, what does the intersection of two graphs mean? What do the coordinate values of the intersection point represent in a system of simultaneous functions? How does this principle relate to an electronic circuit?

Notes 13

Ask your student why this plot is straight, and not curved like the transistor's characteristic function.

Notes 14

It would be good to point out something here: superimposing a linear function on a set of nonlinear functions and looking for the intersection points allows us to solve for multiple variables in a nonlinear mathematical system. Normally, only *linear* systems of equations are considered "solvable" without resorting to very time-consuming arithmetic computations, but here we have a powerful (graphical) tool for approximating the values of variables in a nonlinear system. Since approximations are the best we can hope for in transistor circuits anyway, this is good enough!

Notes 15

This question challenges students to relate load resistor values to load lines, and both to the practical measure of voltage gain in a simple amplifier circuit. As an illustration, ask the students to analyze changes in the circuit for an input signal that varies between $5\ \mu\text{A}$ and $10\ \mu\text{A}$ for the three different load resistor values. The difference in ΔV_{CE} should be very evident!

Notes 16

Q points are very important in the design process of transistor amplifiers, but again students often seem to fail to grasp the actual meaning of the concept. Ask your students to explain how the load line formed by the load resistance, and characteristic curves of the transistor, describe all the possible operating conditions of collector current and V_{CE} for that amplifier circuit. Then discuss how the status of that circuit is defined *at any single point in time* along those graphs (by a line, a curve, or a point?).

Notes 17

The purpose of this question is to get students to relate their existing knowledge of common-collector circuit DC analysis to the concept of load lines and Q-points. Ask your students to share their analysis techniques with the whole class.

Notes 18

The purpose of this question is to get students to relate their existing knowledge of common-emitter circuit DC analysis to the concept of load lines and Q-points. Ask your students to share their analysis techniques with the whole class.

Notes 19

This is a very practical question, as technicians and engineers alike need to choose proper biasing so their amplifier circuits will operate in the intended class (A, in this case). There is more than one proper answer for the resistor values, so be sure to have your students share their solutions with the whole class so that many options may be explored.

Notes 20

The purpose of this question is to get students to kinesthetically interact with the subject matter. It may seem silly to have students engage in a "show and tell" exercise, but I have found that activities such as this greatly help some students. For those learners who are kinesthetic in nature, it is a great help to actually *touch* real components while they're learning about their function. Of course, this question also provides an excellent opportunity for them to practice interpreting component markings, use a multimeter, access datasheets, etc.

Notes 21

When researching engineering textbooks and other resources, these terms are quite often used without introduction, leaving many beginning students confused.

Notes 22

The purpose of this question is to introduce students to the concept of BJT modeling, and also to familiarize them with some of the symbols and expressions commonly used in these models (as well as a bit of DC resistor network theory and algebra review, of course!).

Notes 23

It has been my experience that students require much practice with circuit analysis to become proficient. To this end, instructors usually provide their students with lots of practice problems to work through, and provide answers for students to check their work against. While this approach makes students proficient in circuit theory, it fails to fully educate them.

Students don't just need mathematical practice. They also need real, hands-on practice building circuits and using test equipment. So, I suggest the following alternative approach: students should *build* their own "practice problems" with real components, and try to mathematically predict the various voltage and current values. This way, the mathematical theory "comes alive," and students gain practical proficiency they wouldn't gain merely by solving equations.

Another reason for following this method of practice is to teach students *scientific method*: the process of testing a hypothesis (in this case, mathematical predictions) by performing a real experiment. Students will also develop real troubleshooting skills as they occasionally make circuit construction errors.

Spend a few moments of time with your class to review some of the "rules" for building circuits before they begin. Discuss these issues with your students in the same Socratic manner you would normally discuss the worksheet questions, rather than simply telling them what they should and should not do. I never cease to be amazed at how poorly students grasp instructions when presented in a typical lecture (instructor monologue) format!

A note to those instructors who may complain about the "wasted" time required to have students build real circuits instead of just mathematically analyzing theoretical circuits:

What is the purpose of students taking your course?

If your students will be working with real circuits, then they should learn on real circuits whenever possible. If your goal is to educate theoretical physicists, then stick with abstract analysis, by all means! But most of us plan for our students to do something in the real world with the education we give them. The "wasted" time spent building real circuits will pay huge dividends when it comes time for them to apply their knowledge to practical problems.

Furthermore, having students build their own practice problems teaches them how to perform *primary research*, thus empowering them to continue their electrical/electronics education autonomously.

In most sciences, realistic experiments are much more difficult and expensive to set up than electrical circuits. Nuclear physics, biology, geology, and chemistry professors would just love to be able to have their students apply advanced mathematics to real experiments posing no safety hazard and costing less than a textbook. They can't, but you can. Exploit the convenience inherent to your science, and *get those students of yours practicing their math on lots of real circuits!*